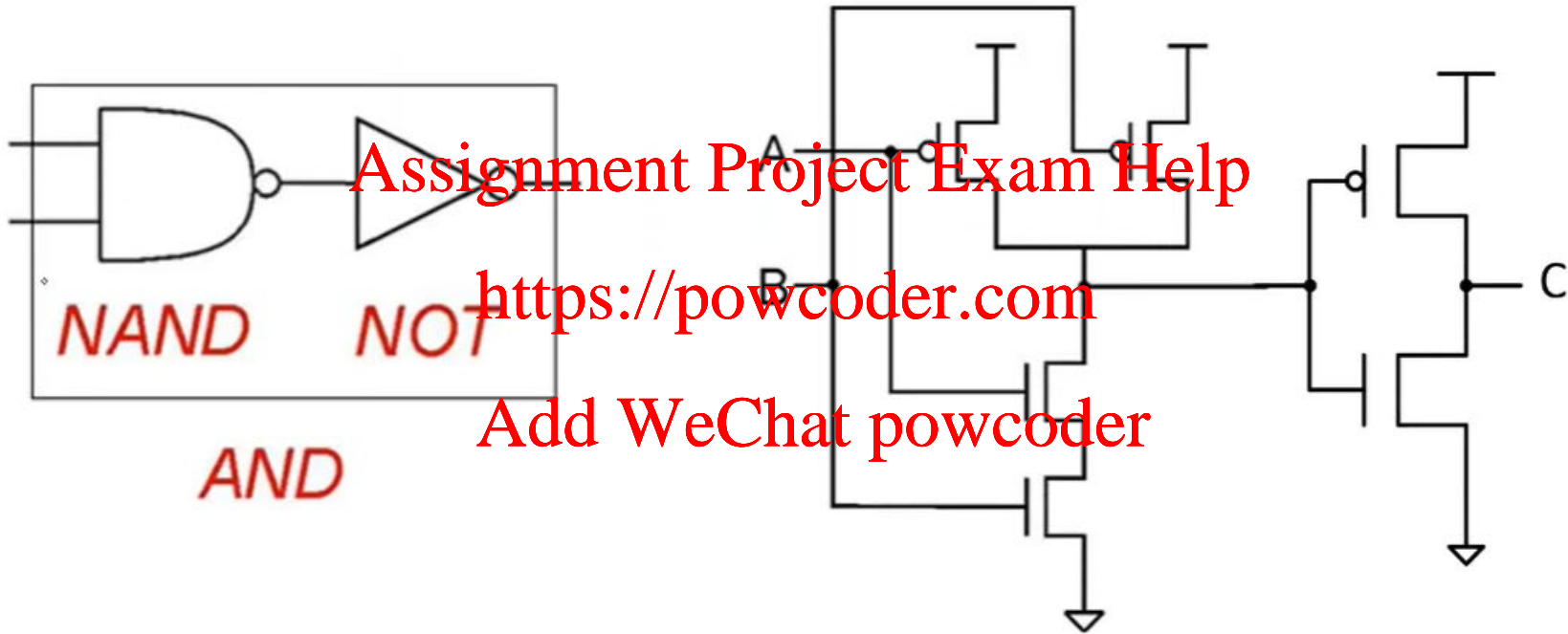



Assignment Project Exam Help

Digital Logic: Boolean Algebra and Gates
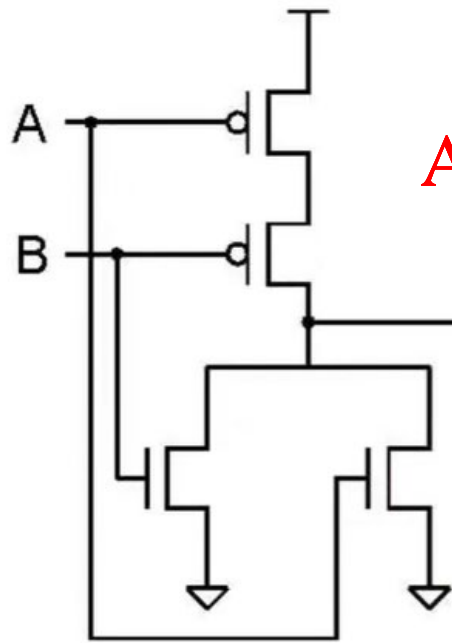
<https://powcoder.com>
Add WeChat powcoder









Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

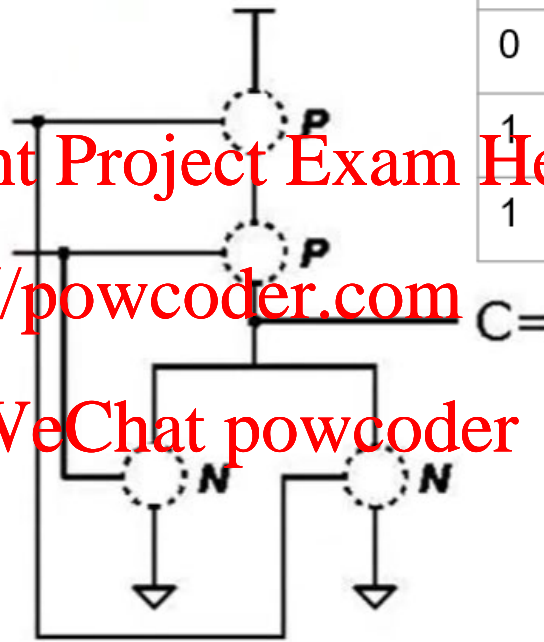


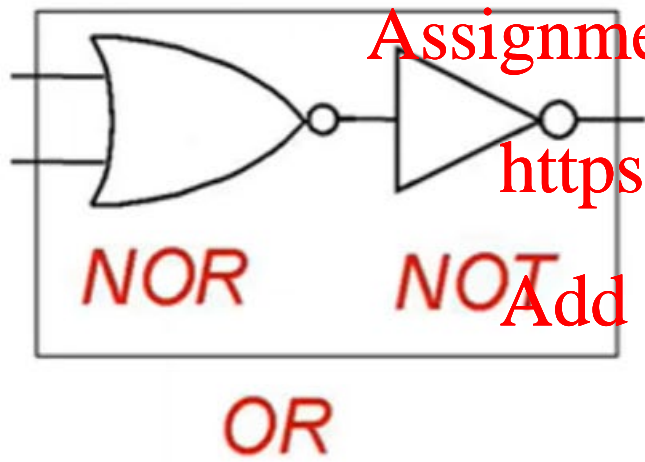


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

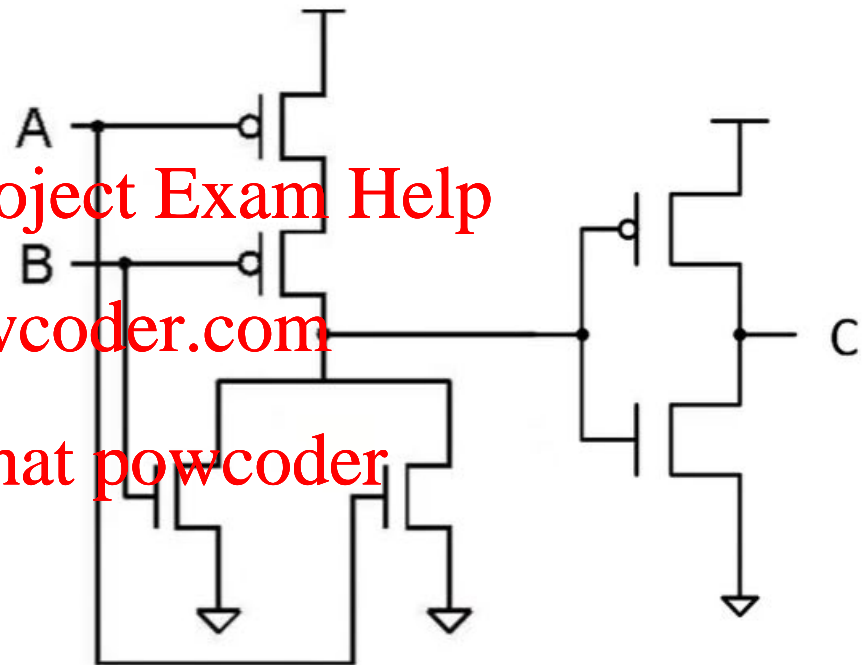

A general CMOS circuit

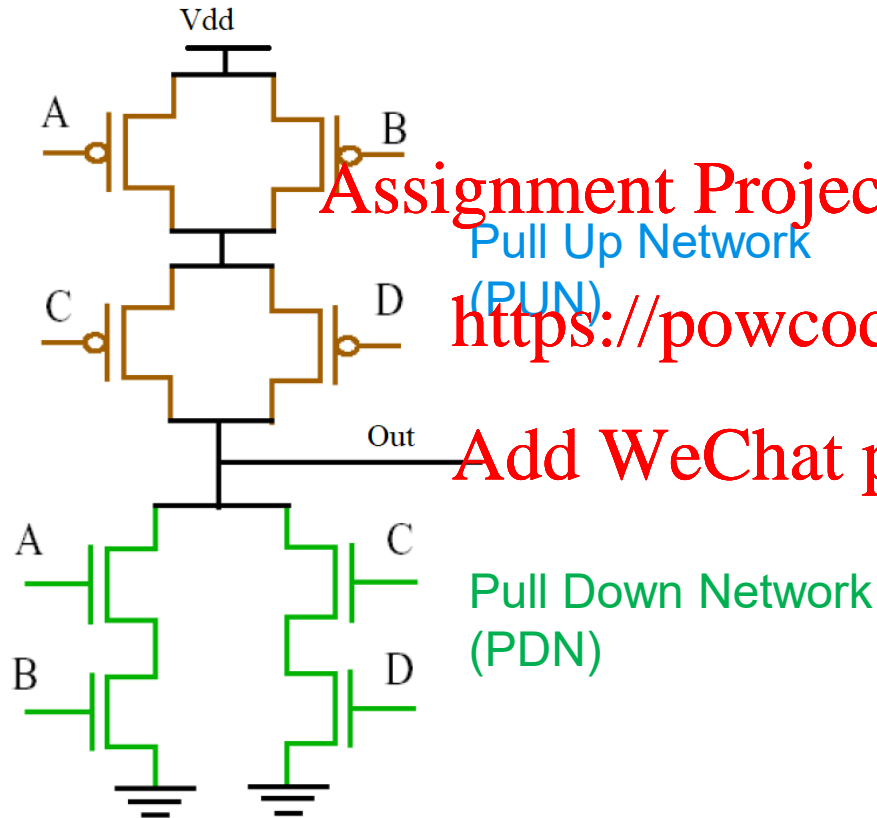

Q. How to determine Out without solving for entire truth table???

A. Follow Output path through either the PUN (towards Vdd) or the PDN (towards gnd)

PDN approach: Under what conditions does Out have a direct path to gnd??


Out = 0, (when A AND B ON)
OR (when C AND D ON)

$$\text{Out} = (AB + CD)'$$



Combinational Logic

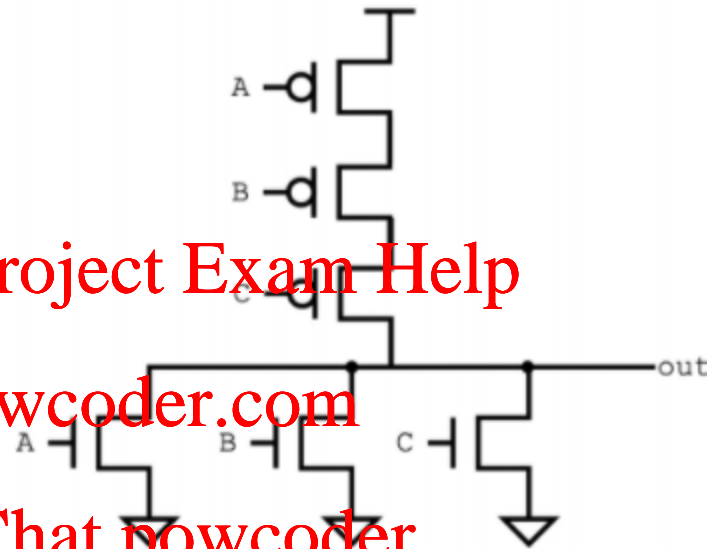7. The following CMOS diagram represents which logic gate?



- ☐ A. NAND
- ☐ B. NOR
- ☐ C. AND
- ☐ D. OR
- ☐ E. Answer not listed.



Axioms of Boolean Algebra (CMPE 100!)

- **Algebra** : study of mathematical symbols and the rules for manipulating these symbols
- Different types of algebra exists depending on what mathematical space you are working with ; e.g. real algebra, vector algebra, linear algebra, Boolean algebra
- The three important elements of algebra: **symbols, rules, operators, constants**
- We are already pretty familiar with the rules of real algebra, i.e. working with real numbers e.g. x, y, z, k are real numbers: $x(y+z-k) = xy +xz - xk$
- **Above example used distributive law and “plus”, “subtract”, “multiply” operators.**
- **Boolean algebra is the only algebra understood by a computer. The computer physically solves problems in Boolean algebra which are based on high level problems (in various types of algebra)**
- **Two constants: 1,0; Three fundamental operators: AND (&), OR(+), NOT**



Axioms of Boolean Algebra (CMPE 100!)

- $0 \cdot 0 = 0$

- $1 + 1 = 1$

- $1 \cdot 1 = 1$

- $0 + 0 = 0$

- $0 \cdot 1 = 1 \cdot 0 = 0$

- $1 + 0 = 0 + 1 = 1$

- if $x = 0$ then $x = 1$

- if $x = 1$ then $x' = 0$

Let's have a closer look at what exactly those transistors were computing in the previous slides!

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Single-Variable Theorems (CMPE 100!)

- $x \cdot 0 = 0$

- $x + 1 = 1$

- $x \cdot 1 = x$

- $x + 0 = x$

- $x \cdot x = x$

- $x + x = x$

- $x \cdot x' = 0$

- $x + x' = 1$

- $(x')' = x$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Properties of Boolean Algebra (CMPE 100!)

■ Commutative

$$\blacklozenge x \cdot y = y \cdot x$$

$$\blacklozenge x + y = y + x$$

■ Associative

$$\blacklozenge x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

$$\blacklozenge x + (y + z) = (x + y) + z$$

■ Distributive

$$\blacklozenge x \cdot (y + z) = x \cdot y + x \cdot z$$

$$\blacklozenge x + y \cdot z = (x + y) \cdot (x + z)$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder




Properties of Boolean Algebra (CMPE 100!)

■ Absorption

$$\blacklozenge x + x \cdot y = x$$

$$\blacklozenge x \cdot (x + y) = x$$

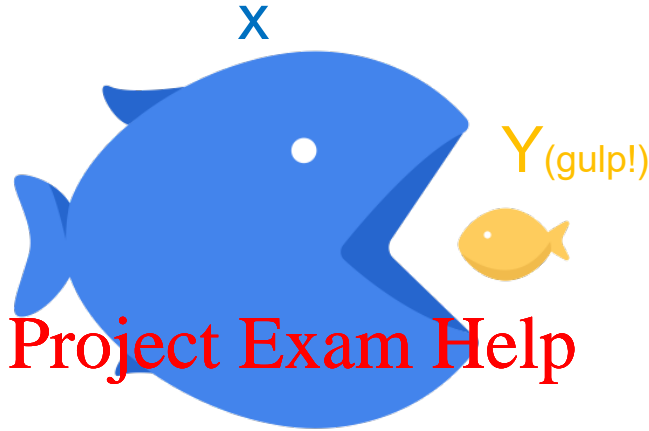

Assignment Project Exam Help

■ Combining

$$\blacklozenge x \cdot y + x \cdot y' = x$$

$$\blacklozenge (x + y) \cdot (x + y') = x$$

<https://powcoder.com>

Add WeChat powcoder



Properties of Boolean Algebra (CMPE 100!)

■ De Morgan's Laws

$$\blacklozenge (x \cdot y)' = x' + y'$$

$$\blacklozenge (x + y)' = x'y'$$

Assignment Project Exam Help

■ Other

<https://powcoder.com>


$$\blacklozenge x + x' \cdot y = x + y$$

Add WeChat powcoder

$$\blacklozenge x \cdot (x' + y) = x \cdot y$$



Basic Logic Gates

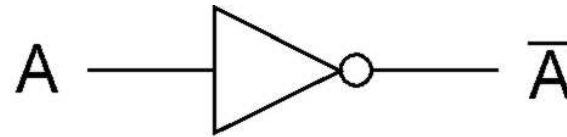


NOT




Assignment Project Exam Help

<https://powcoder.com>


OR Add WeChat powcoder **NOR**

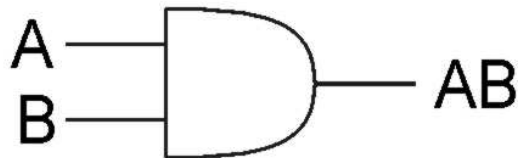

AND

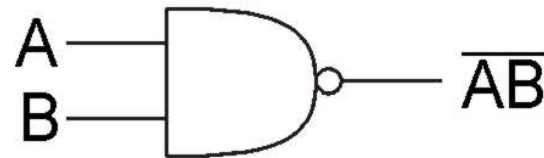


NAND

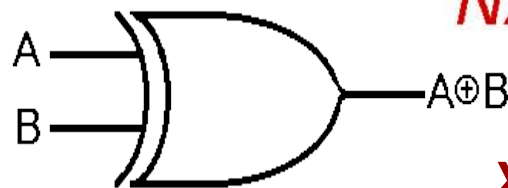

XOR



XOR gate

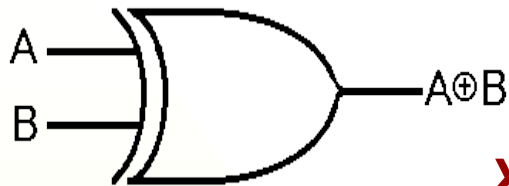

XOR

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

A	B	C	$A \oplus B \oplus C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

- Output is $a(XOR)b = a'b + ab'$ (for 2 operands)
- In general, we say output is
 - ◆ 1 if odd number of inputs are 1
 - ◆ 0 if even number of inputs are 1

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

- Output is $a(XOR)b = a'b + ab'$ (for 2 operands)
- In general, we say output is
 - ◆ 1 if odd number of inputs are 1
 - ◆ 0 if even number of inputs are 1

odd no. of inputs are 1, therefore output is 1



XOR gate as a “programmable” inverter (NOT gate)

A	B	Z ($A \oplus B$)
0	0	0
0	1	1
1	0	1
1	1	0

→ When $A=0$, $Z=B$


→ When $A=1$, $Z=\overline{B}$

Assignment Project Exam Help

<https://powcoder.com>

- Thus, we can “program” Z to either be inverse of B, or simply be equal to B, depending on the value of A

Add WeChat powcoder

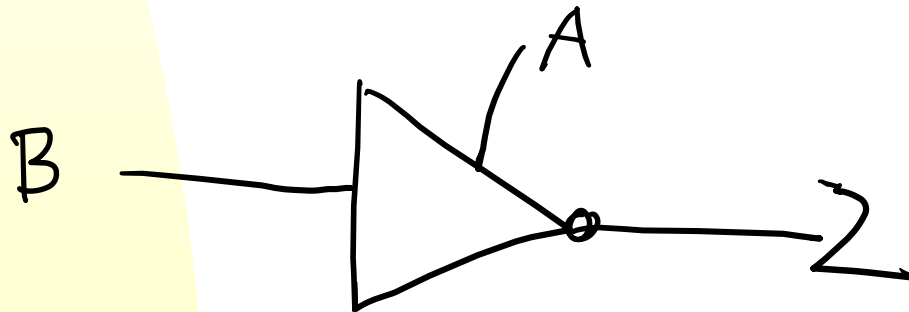

- Above is an alternative symbol for XOR gate as a programmable inverter. But in general, we will stick to the normal XOR gate symbol

