

# Digital Logic: Boolean Algebra and Gates (contd..)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# n-to- $2^n$ Decoder

- $n$  inputs,  $2^n$  outputs
  - ◆ exactly one output is 1 for each possible input pattern
- Uses:
  - ◆ Convert memory or register address to a control line
  - ◆ Convert an opcode to one of  $n$  control lines
  - ◆ We will get to this in the MIPS material

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

# Two-to-Four Decoder

TRUTH TABLE:

A	B	$Y_0$	$Y_1$	$Y_2$	$Y_3$
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

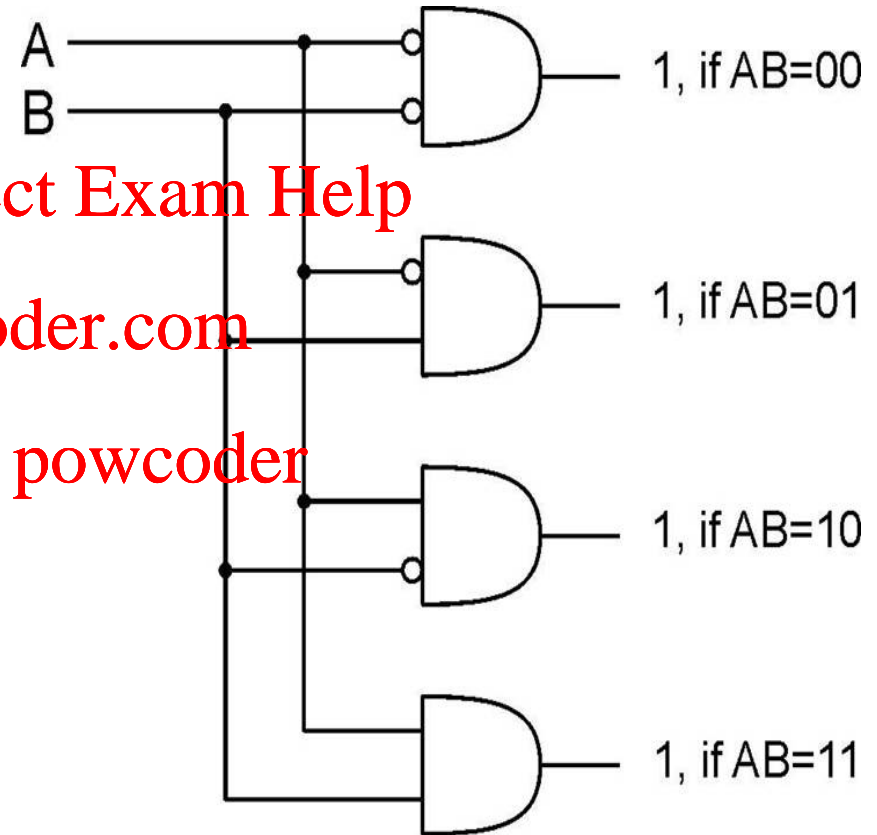

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Three-to-Eight Decoder

$$[ 2^3 = 8 ]$$

	A	B	C	$Y_0$	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$
$R_0$	0	0	0								
$R_1$	0	0	1								
$R_2$	0	1	0								
$R_3$	0	1	1								
$R_4$	1	0	0								
$R_5$	1	0	1								
$R_6$	1	1	0								
$R_7$	1	1	1								

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# How to decode for 6 output lines?

- How many input lines do we need?

	A	B	C	$Y_0$	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$
$R_0$	0	0	0	<b>Assignment Project Exam Help</b>  <a href="https://powcoder.com">https://powcoder.com</a>  Add WeChat powcoder							
$R_1$	0	0	1								
$R_2$	0	1	0								
$R_3$	0	1	1								
$R_4$	1	0	0								
$R_5$	1	0	1								
$R_6$	1	1	0								
$R_7$	1	1	1								

# Time for some...

- We currently use decimal system in daily life (deci=10 digits, 0-9)

- We know.. <https://powcoder.com>

$$1+0=1$$

$$1+1=2; 1+2=3; 1+3=4...$$

$$1+8=9;$$

- What is  $1+9=??$



# Binary Addition and Half-Adder

- $0 + 0 = 0$

- $0 + 1 = 1$

- $1 + 0 = 1$

- $1 + 1 = 10$

- A half-adder can add 2 bits and produces a sum and carry signal

- ◆ Sum =  $A \oplus B$

- ◆ Carry =  $AB$

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


# One-Bit Full Adder

A	B	$C_{in}$	$C_{out}$	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

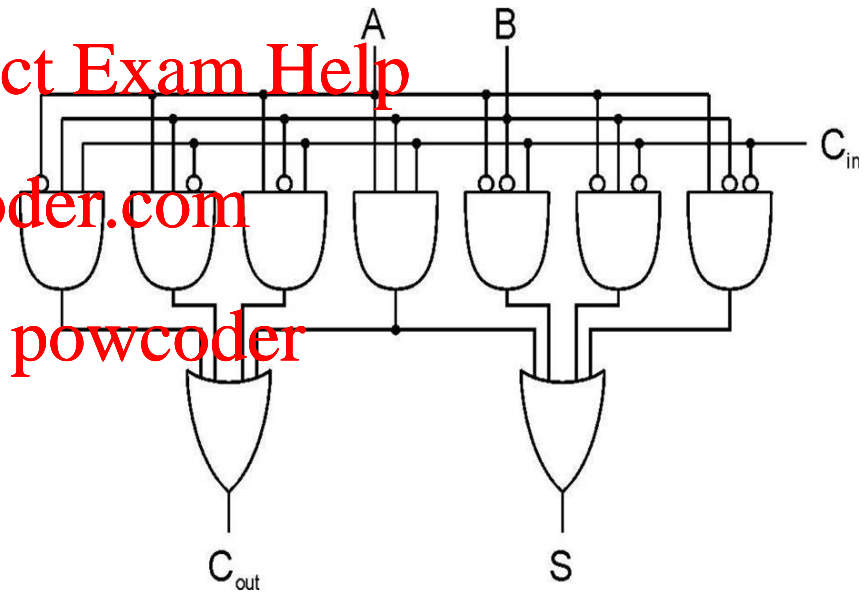



# Four-Bit Full Adder

Ripple-carry adder

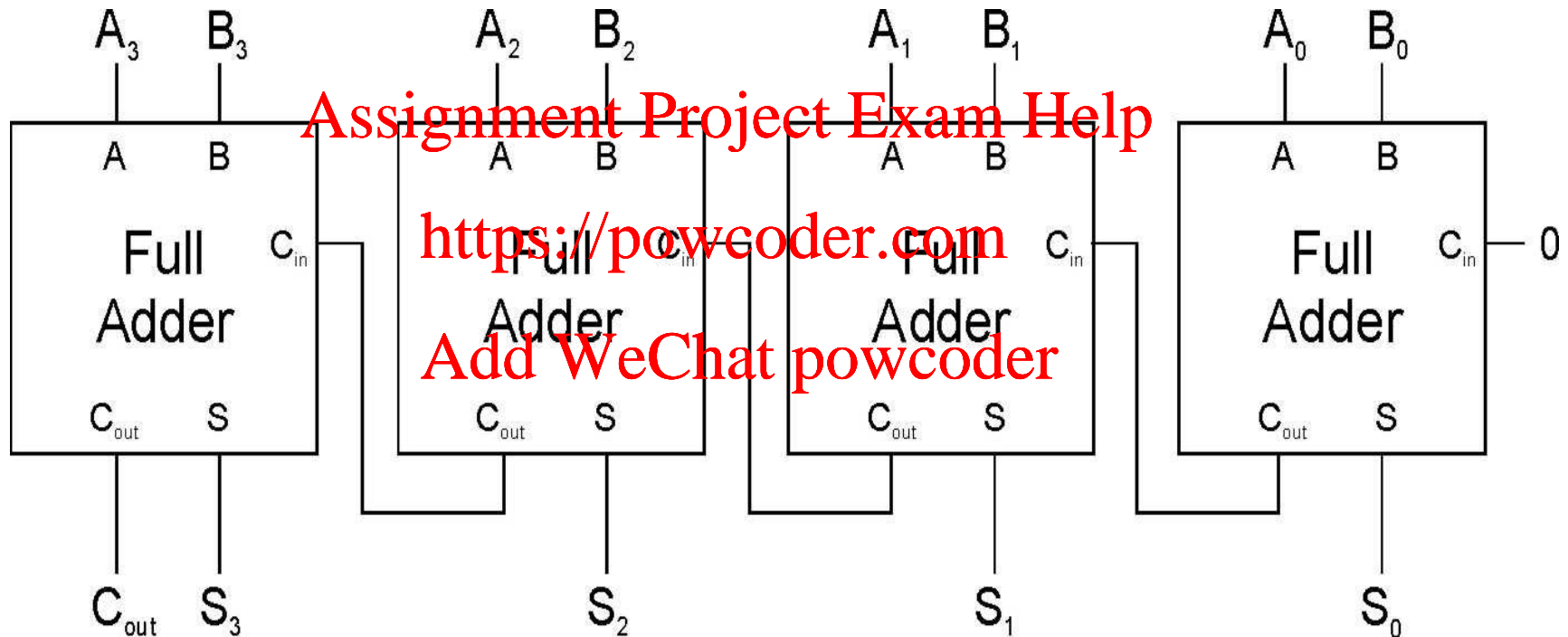

# Masking

- Want to look only at certain bits of a binary word
- Use a mask to remove the uninteresting bits
- Example:
  - ◆ Two values: 01001101 and 01001001
  - ◆ If we want to see bit 3 from right, we AND it with 00000100 to get
    - ★ 00000100 and 00000000, respectively.

# Logic Minimization (CSE 100!)

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Start with SOP:

$$A'B'C' + A'B'C + AB'C' + ABC'$$

Factor A' and A out:

$$A'(B'C' + B'C) + A(B'C' + BC')$$

Factor B and C' out:

$$A'(B(C' + C)) + A(C'(B' + B))$$

Use identity that  $C' + C = 1$  and  $B' + B = 1$ :

$$A'B + AC'$$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Building functions from logic gates

- Combinational Logic Circuit
  - ◆ Output depends only on the current inputs
  - ◆ Stateless (memoryless)
- Sequential Logic Circuit
  - ◆ Output depends on the sequence of inputs (past and present)
  - ◆ Stores information (state) from past inputs

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

# Sequential Circuits and Memory

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder