 


Digital Logic: Boolean Algebra and Gates (contd.)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder




**HW: Please go through Participation
activities on Zybooks before doing
Challenge activities!**

Assignment Project Exam Help

<https://powcoder.com>

[Add WeChat powcoder](#)

 

XOR gate as a “programmable” inverter (NOT gate)

A	B	Z ($A \oplus B$)
0	0	0
0	1	1
1	0	1
1	1	0

→ When $A=0$, $Z=B$


→ When $A=1$, $Z=\bar{B}$

Assignment Project Exam Help


<https://powcoder.com>

- Thus, we can “program” Z to either be inverse of B, or simply be equal to B, depending on the value of A

Add WeChat powcoder

 

 - Above is an alternative symbol for XOR gate as a programmable inverter. But in general, we will stick to the normal XOR gate symbol




Sum of Products (SOP)

- How do you get from a truth table to a logic expression?
- Sum of products is standard way of synthesizing simple circuits
- Procedure:
 - 1. Find the rows with the '1' output
 - 2. Write the product-form expression for the inputs in that row (0=inverted, 1=normal)
 - 3. Combine the products in step 2 into a sum (OR the results of step 2)

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

Sum of Products

■ XOR Gate


A	B	Y
0	0	
0	1	
1	0	
1	1	

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

 1. Find the rows with the '1' output
2. Write the product-form expression for the inputs in that row (0=inverted, 1=normal)
3. Combine the products in step 2 into a sum (OR the results of step 2)



Product of Sums

 - Procedure:
 1. Find the rows with the '0' output
 2. Write the sum-form expression for the inputs in that row (0=normal, 1=inverted)
Assignment Project Exam Help
<https://powcoder.com>
 3. Combine the sums in step 2 into a product (AND the results of step 2)
- Note: we treat 0 and 1 reverse than for SoP
Add WeChat powcoder



Product of Sums


- XOR Gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

Examples of SoP and PoS

Find SOP

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Find Pos

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

 

Logical Completeness


Can implement ANY truth table AND, OR, and NOT!

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
		0	0
		1	0

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

 

1. AND combinations that yield a "1" in the truth table.

2. OR the results of the AND gates.

 3. Is not necessarily a minimal solution.



De Morgan's Laws


Two laws:

- ◆ $A' + B' = (AB)'$
- ◆ $A' B' = (A+B)'$

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

De Morgan's Laws

$$(A + B)' = A'B' \quad \text{conversely} \quad (AB)' = A' + B'$$


“Break the line, change the sign”

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

A	B	$A + B$	$\overline{A + B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0			1	1	1
0	1			1	0	0
1	0			0	1	0
1	1			0	0	0

 

De Morgan's Laws

$$(A + B)' = A'B' \quad \text{conversely} \quad (AB)' = A' + B'$$


“Break the line, change the sign”

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

A	B	AB	\overline{AB}	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$
0	0			1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

 

Even Simpler Logical Completeness


- Can implement ANY truth table NAND only!
 - ◆ Make NOT out of NAND?

Assignment Project Exam Help

- ◆ Make OR out of NAND? <https://powcoder.com>

Add WeChat powcoder

- ◆ Make AND out of NAND?


 


Two-Way Multiplexer

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

  

Two-Way Multiplexer

2-way multiplexer: the output is equal to one of the two inputs, based on a selector

S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder




Four-Way Multiplexer

- n -bit selector and 2^n inputs, one output
 - ◆ output equals one of the inputs, depending on selector
- “Four-to-one mux”


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

   


Multiple Bit Multiplexers (and Buses)

 

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


 


Two-to-Four Decoder

- n inputs, 2^n outputs
 - ◆ exactly one output is 1 for each possible input pattern

- Uses:

 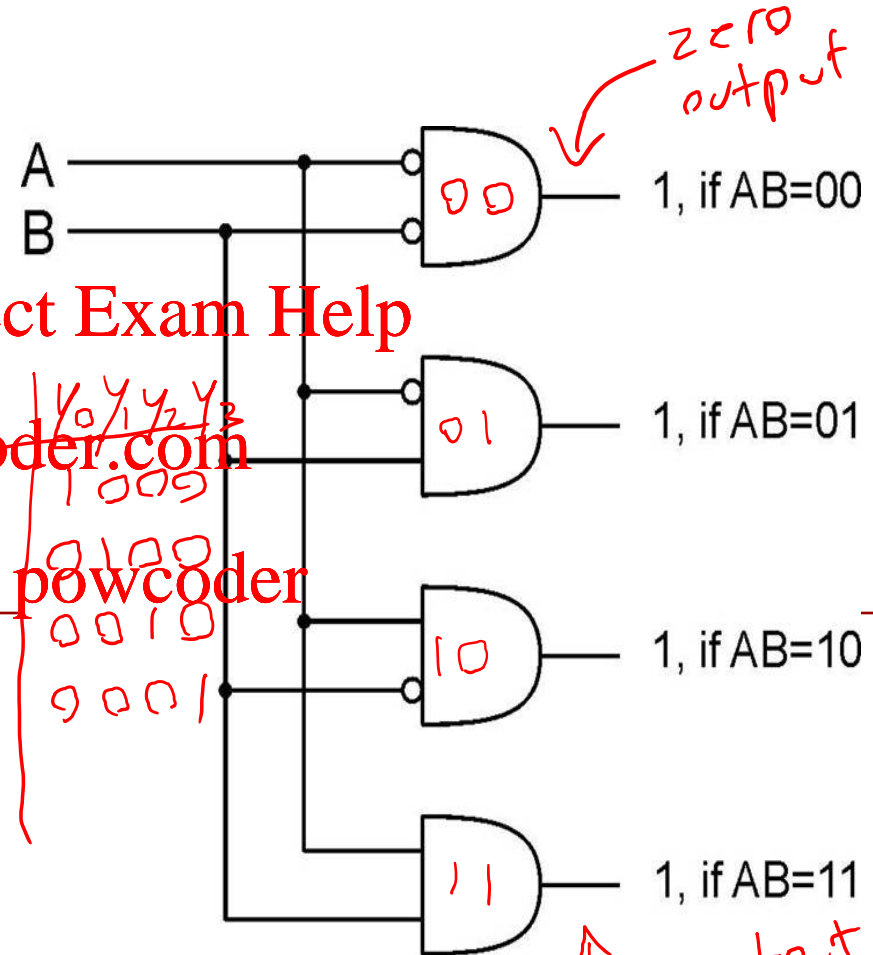- ◆ Convert memory or register address to a control line
- ◆ Convert an opcode to one of n control lines
- ◆ We will get to this in the MIPS material



Time for some...

- We currently use decimal system in daily life (deci=10 digits, 0-9)

- We know.. <https://powcoder.com>

$$1+0=1$$

$$1+1=2; 1+2=3; 1+3=4...$$


$$1+8=9;$$

- What is $1+9=?$?

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

Binary Addition and Half-Adder

- $0 + 0 = 0$

- $0 + 1 = 1$

- $1 + 0 = 1$

- $1 + 1 = 1$

- A half-adder can add 2 bits and produces a sum and carry signal

- ◆ Sum = $A \oplus B$


- ◆ Carry = AB

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Assignment Project Exam Help XOR

<https://powcoder.com>

Add WeChat powcoder

 



One-Bit Full Adder

A	B	C_{in}	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		

Assignment Project Exam Help



<https://powcoder.com>

Add WeChat powcoder

  

Four-Bit Full Adder

Ripple-carry adder

 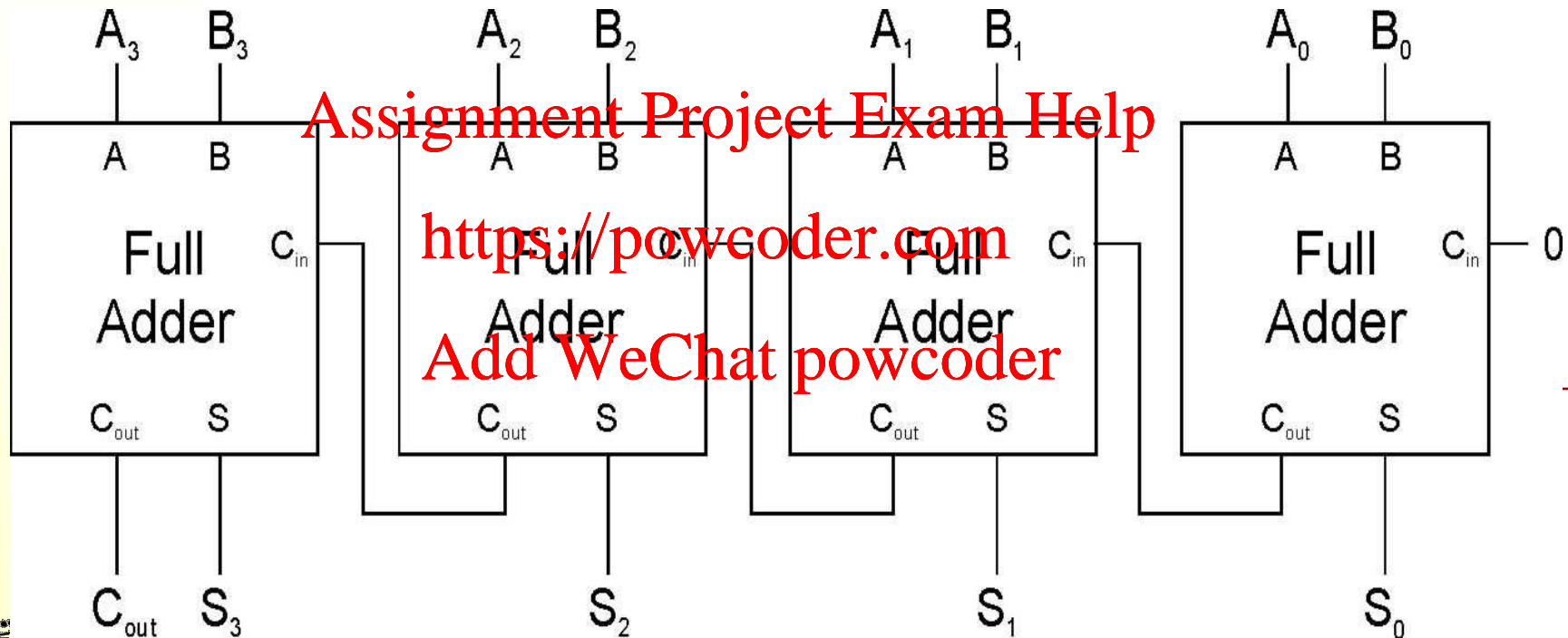


Masking

- Want to look only at certain bits of a binary word
- Use a mask to remove the uninteresting bits
- Example:
 - ◆ Two values: 01001101 and 01001001
 - ◆ If we want to see bit 3 from right, we AND it with 00000100 to get
 - ★ 00000100 and 00000000, respectively.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 


Building functions from logic gates

- Combinational Logic Circuit
 - ◆ Output depends only on the current inputs
 - ◆ Stateless (memoryless)
- Sequential Logic Circuit
 - ◆ Output depends on the sequence of inputs (past and present)
 - ◆ Stores information (state) from past inputs

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 


Sequential Circuits and Memory

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 

Combinational vs. Sequential

- Combinational circuit
 - ◆ Always gives the same output for a given set of inputs
 - ◆ Example: Adder always generates sum and carry, regardless of previous inputs
- Sequential circuit
 - ◆ Remembers previous input
 - ◆ Output depends on state and input

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Sequential Circuits

- Store information
- Output depends on stored information (state) plus input
 - ◆ So a given input might produce different outputs, depending on the stored information
- Example: ticket counter
 - ◆ Advances when you push the button
 - ◆ Output depends on previous state

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder




State Machine


The basic type of sequential circuit

- ◆ Combines combinational logic with storage
- ◆ “Remembers” state, and changes output (and state) based on inputs and current state

<https://powcoder.com>

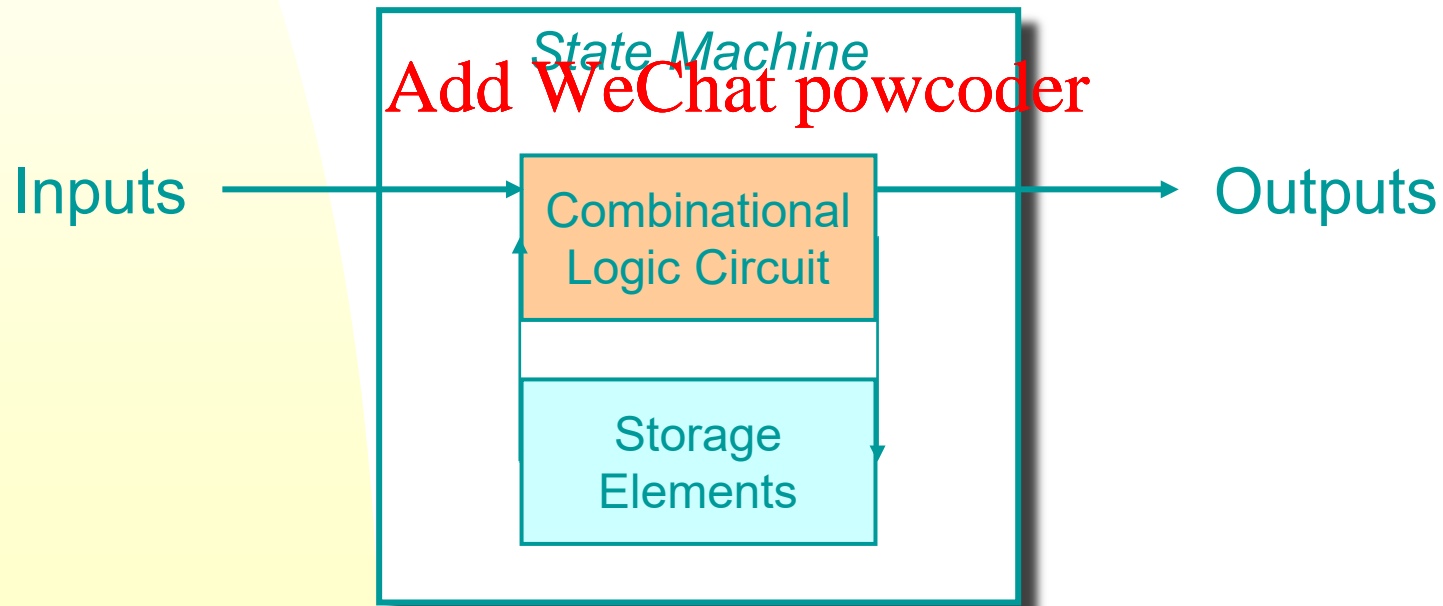

Example of State Machine: Traffic Light

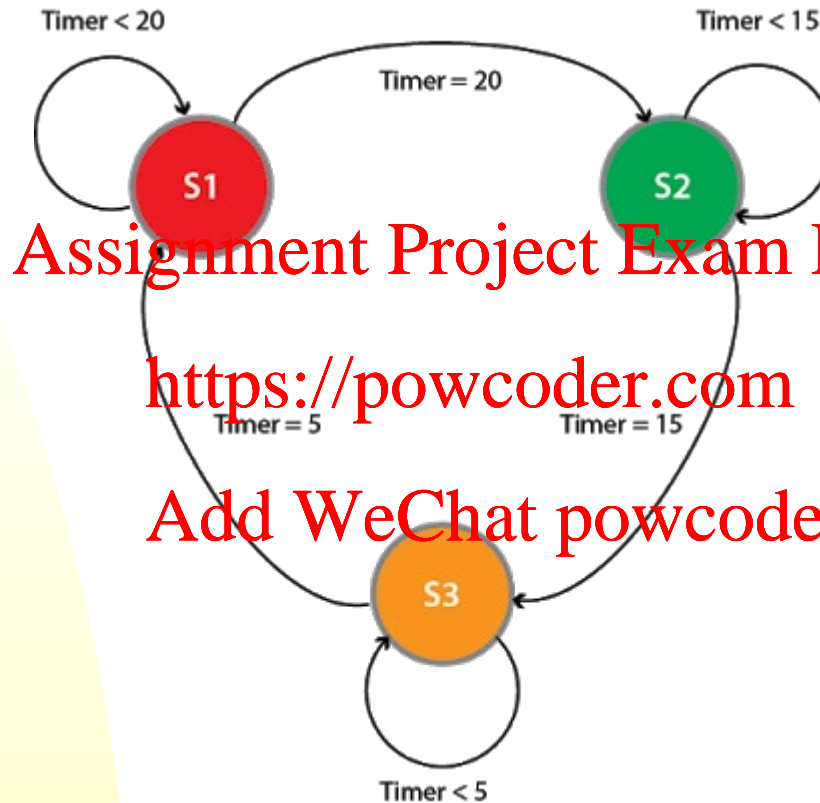


Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder




State Machine: Overview

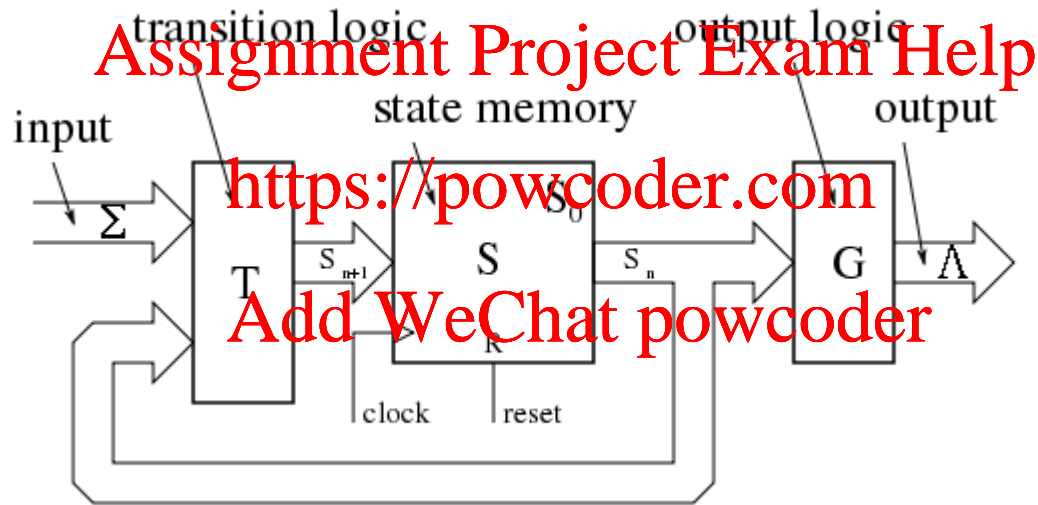

State Machine: Traffic Light

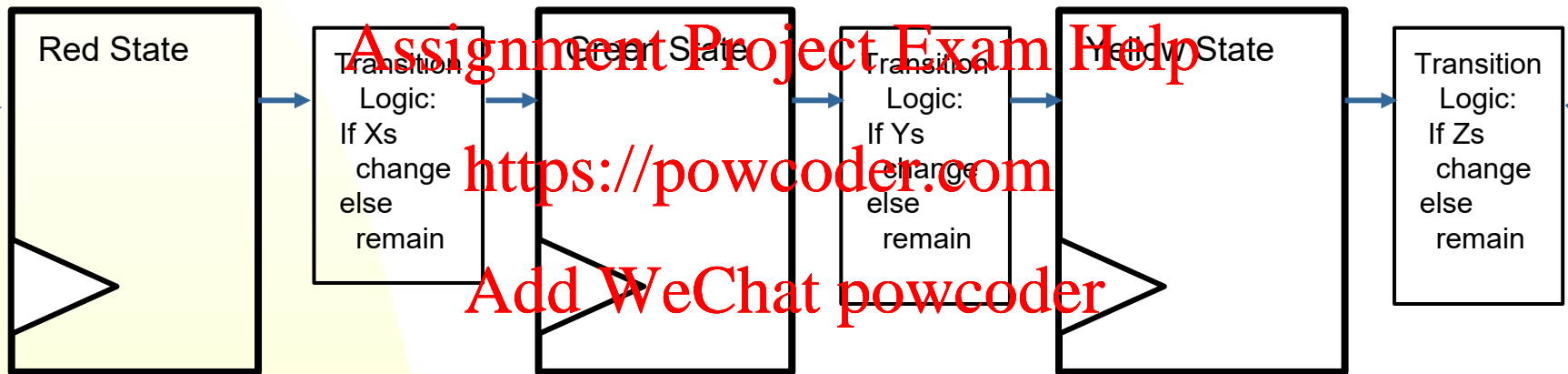


State Machine: Traffic Light

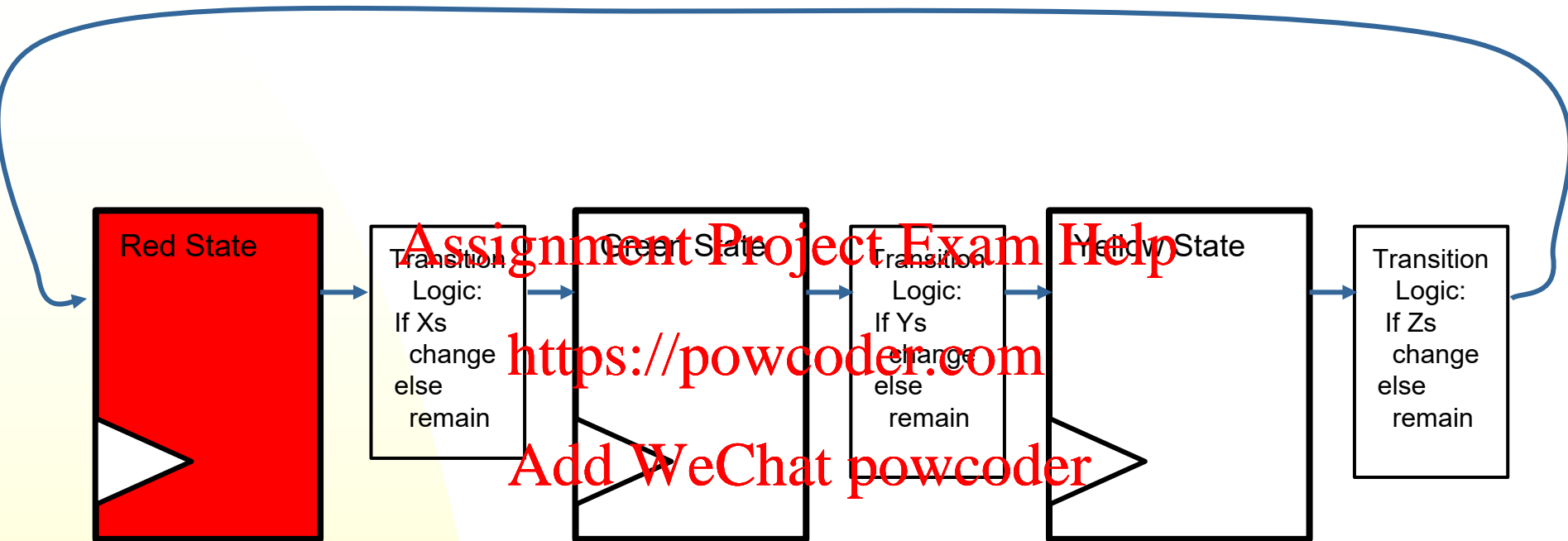

- Start off in default state Red




State Machine: Traffic Light

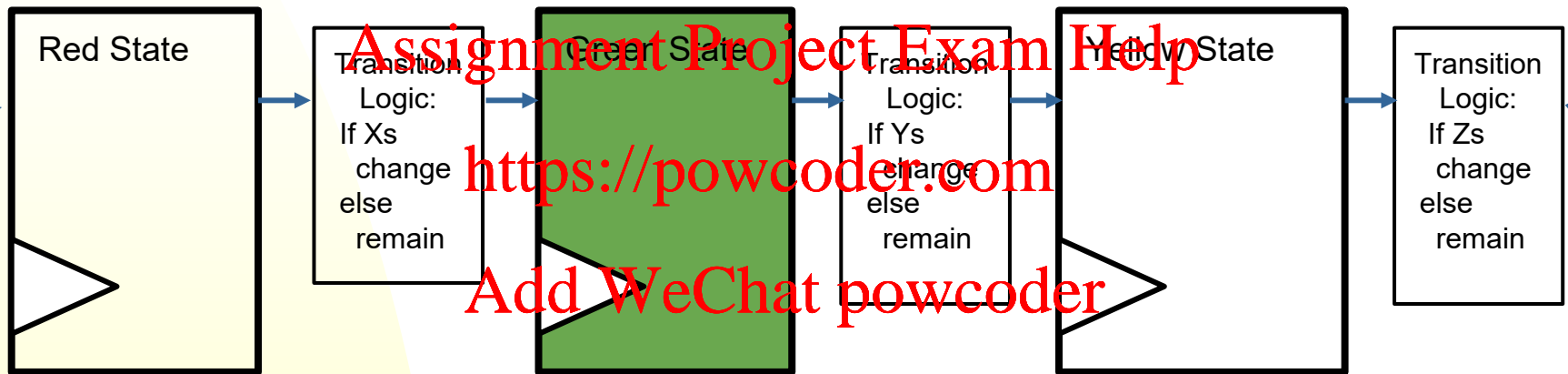

- After a specified time Xs switch to next state




State Machine: Traffic Light

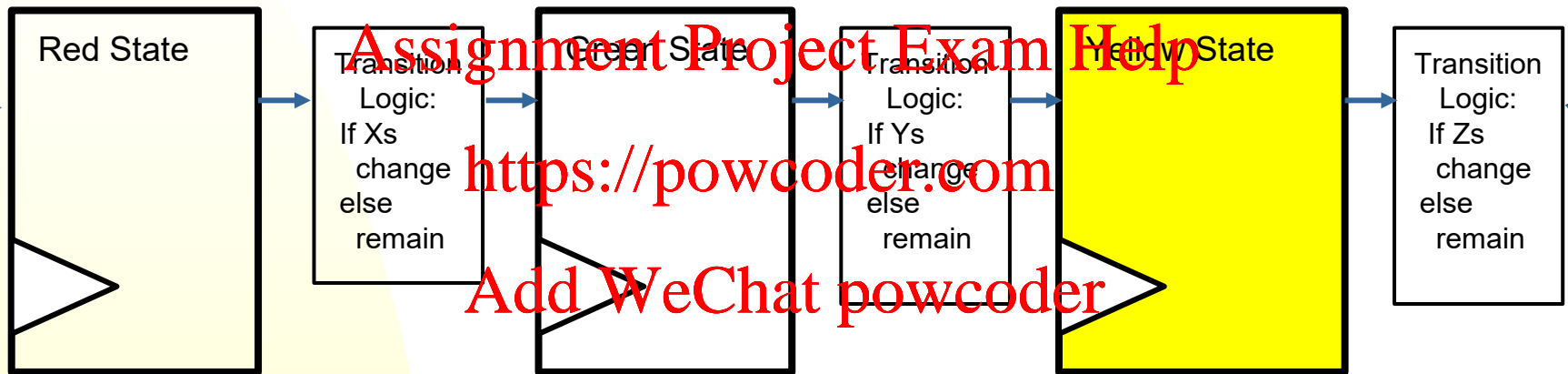

- After a specified time Ys switch to next state



State Machine: Traffic Light

 

- After a specified time Zs switch to next state which is Red.



D Flip-Flops

Memory device

- Can be positive triggered or negative triggered (by a clock usually abbreviated by clk)
- Different types e.g. RS, JK


Assignment Project Exam Help

<https://powcoder.com>

- Inputs/Outputs:

- ◆ D: input signal
- ◆ clk: Clock signal
- ◆ en: if 0 Q holds its value, if 1, Q becomes D at clk edge.
- ◆ rst: if 1 then Q becomes 0
- ◆ Q: output signal


Add WeChat powcoder

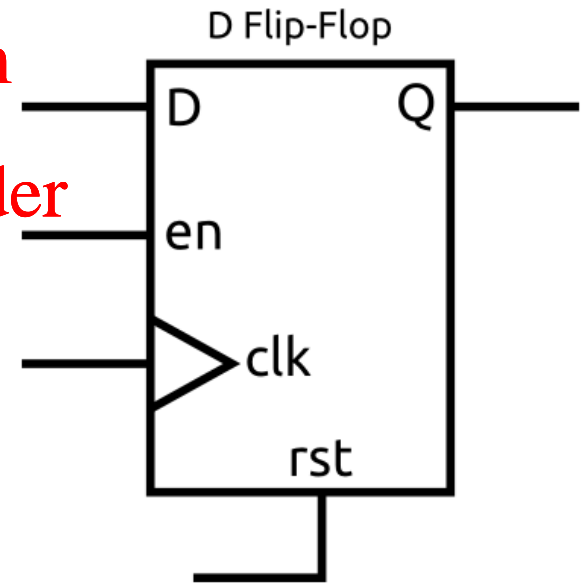

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge (0 -> 1).
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = 1/period


Assignment Project Exam Help

 

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge (0 -> 1).
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = 1/period


Assignment Project Exam Help

 

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$


Assignment Project Exam Help

 

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$


Assignment Project Exam Help

 

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$


Assignment Project Exam Help

 

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$


Assignment Project Exam Help

 

Setup and Hold Time


- Setup time: Time before clock edge where signal has to be stable
- Hold time: Time after clock edge where signal has to be stable

Assignment Project Exam Help

 


Latch

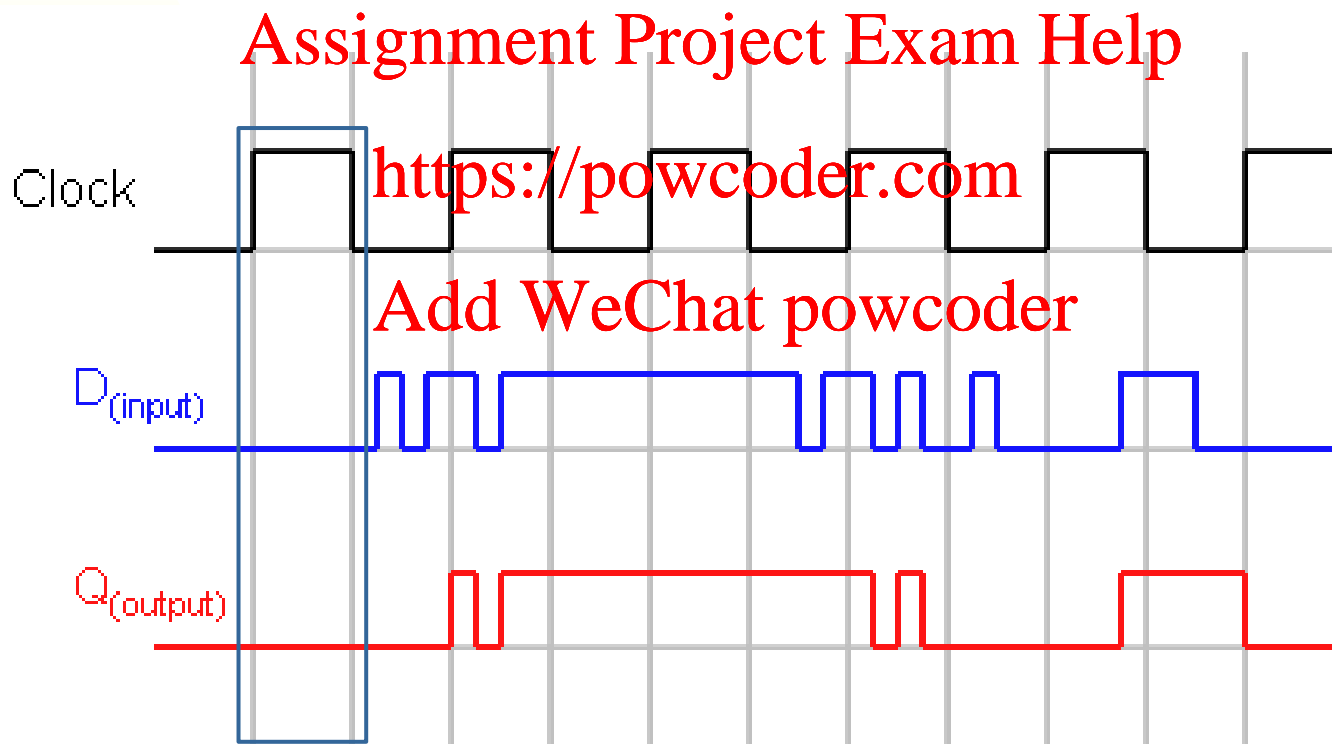- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

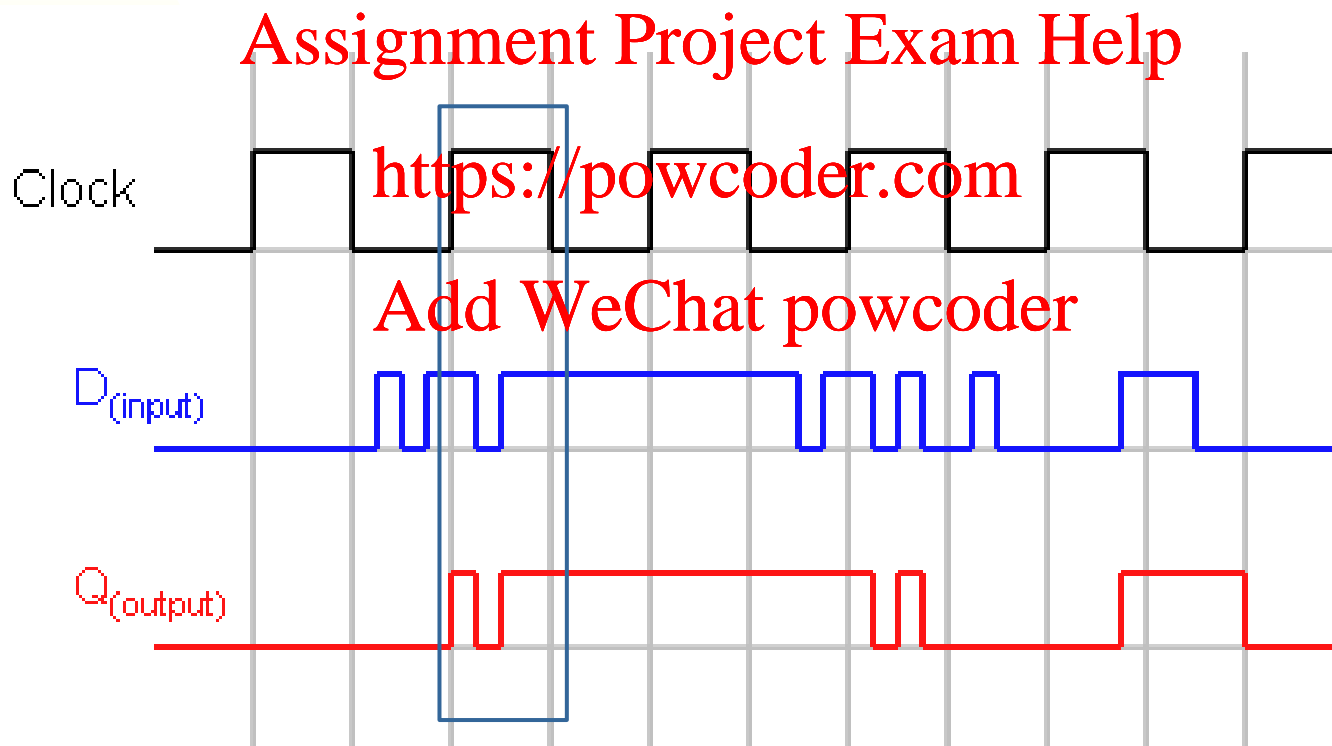- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

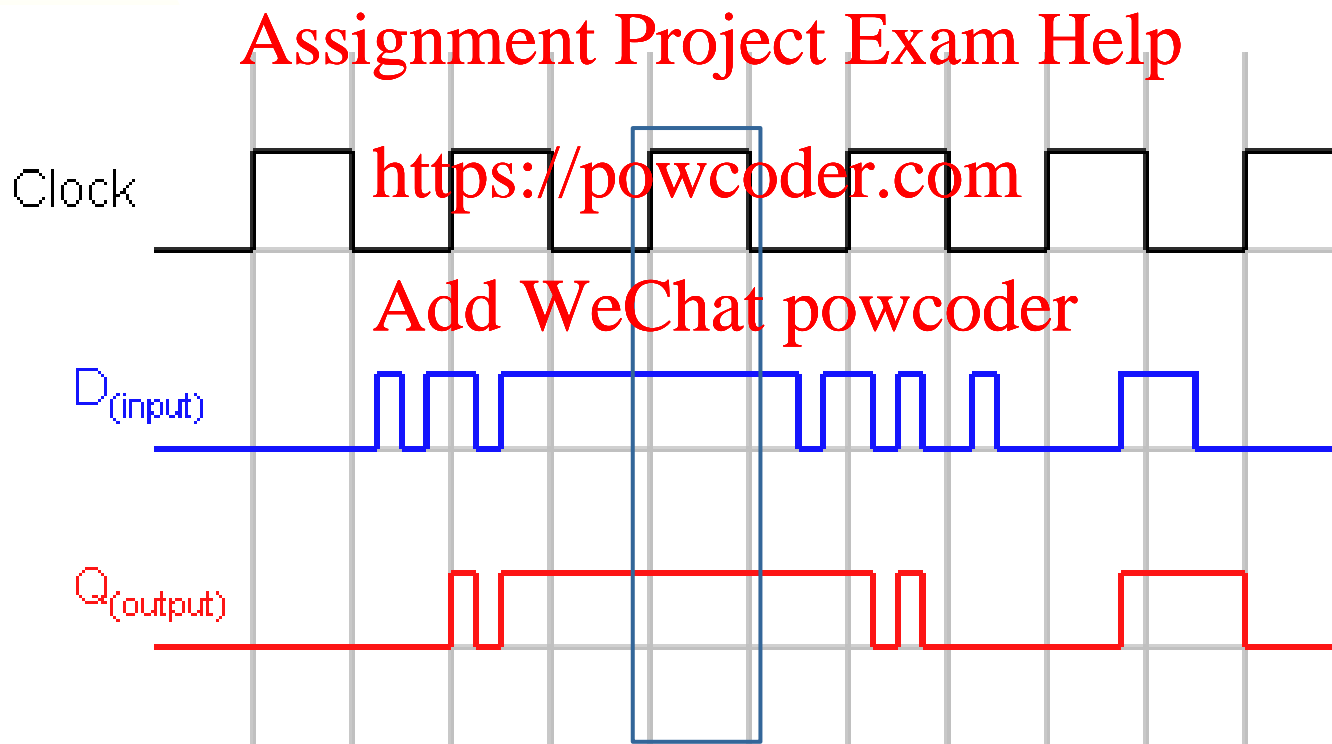- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

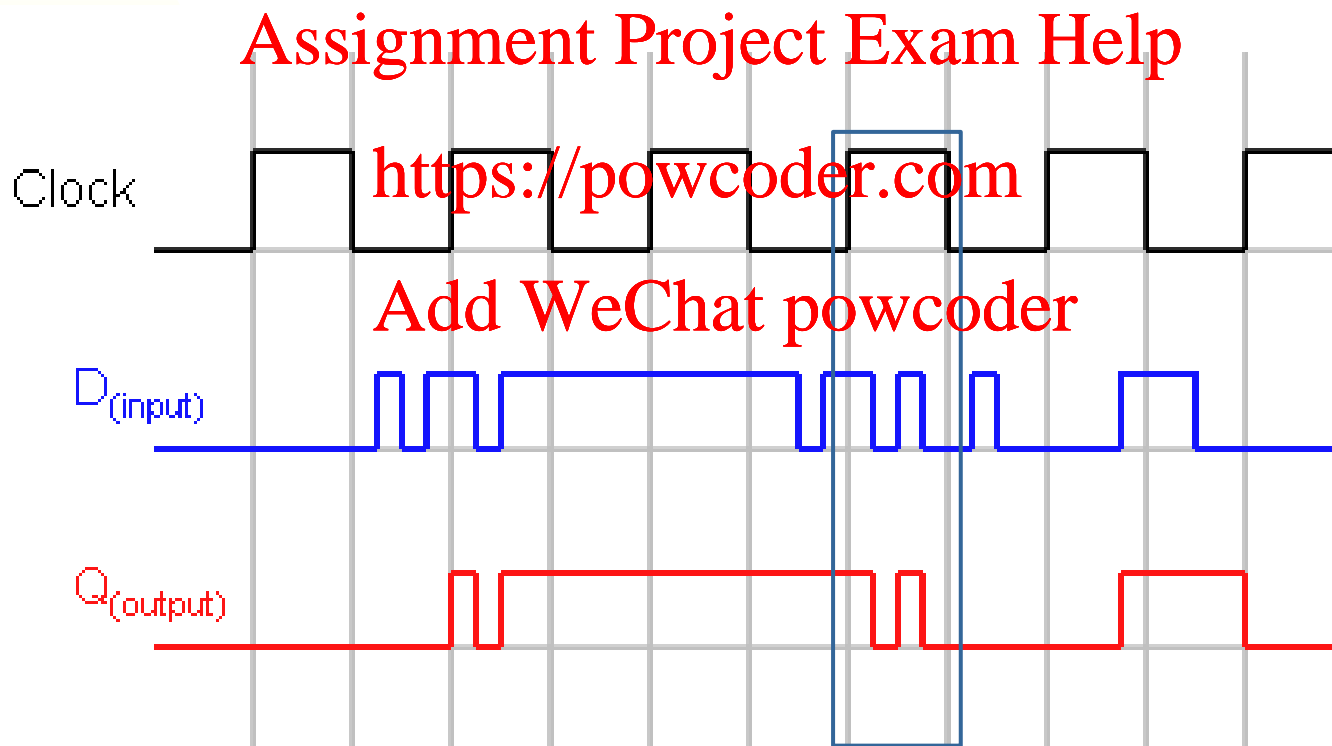- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

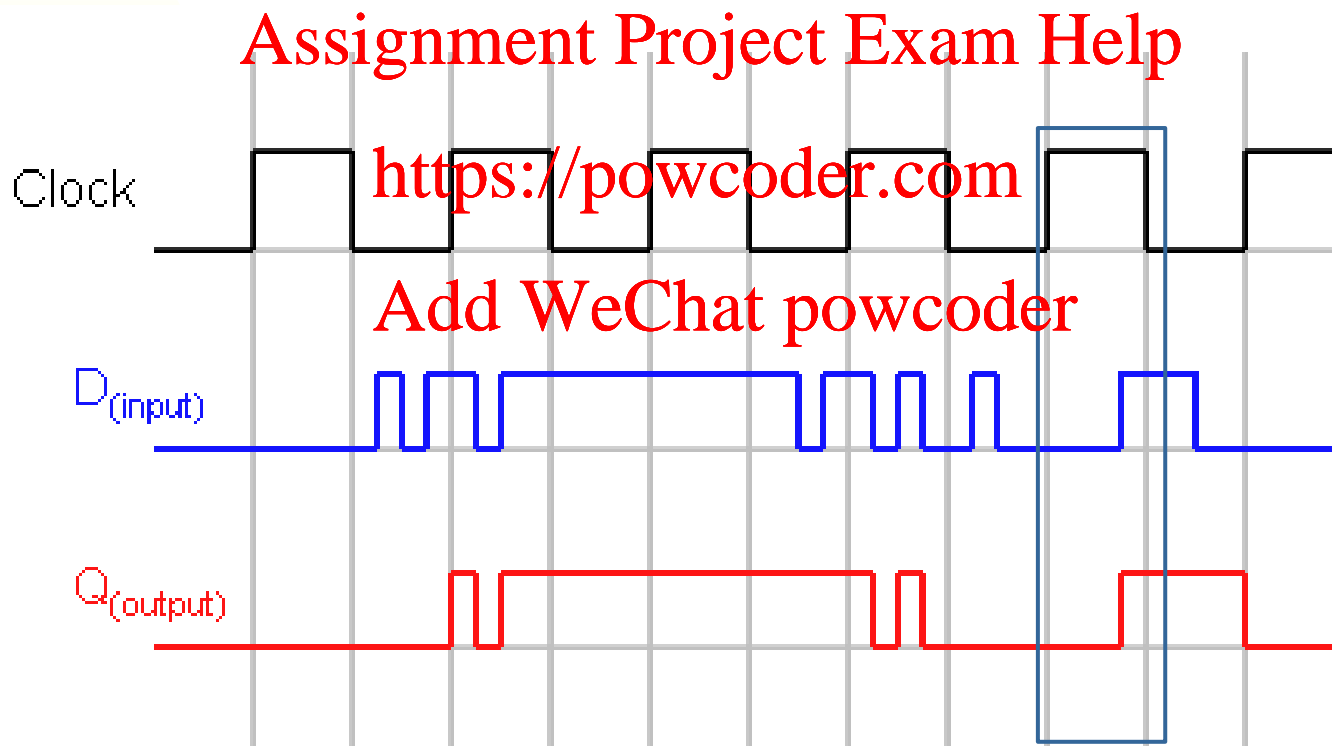- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

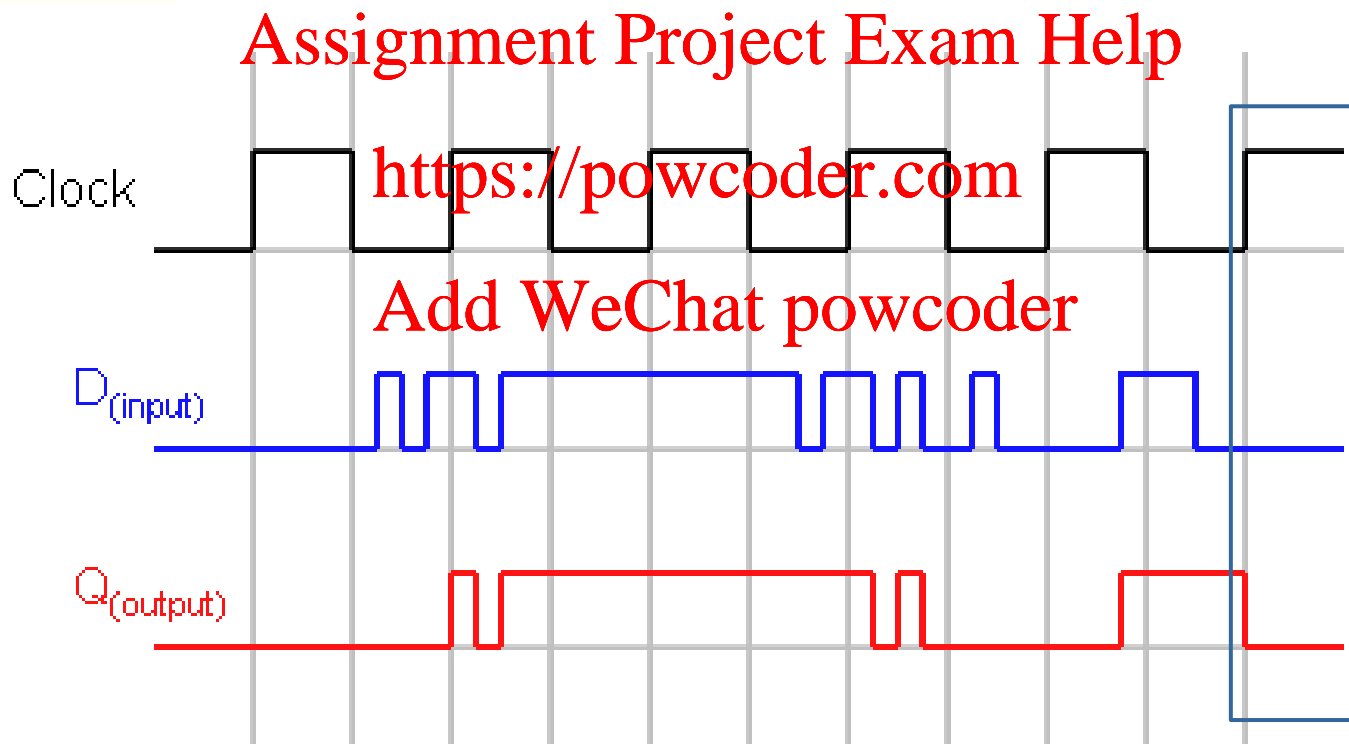- Output is equal to Input when clk is high.
- Stores last value when clk is low.





One way to make a Flip-Flop: Two Latches

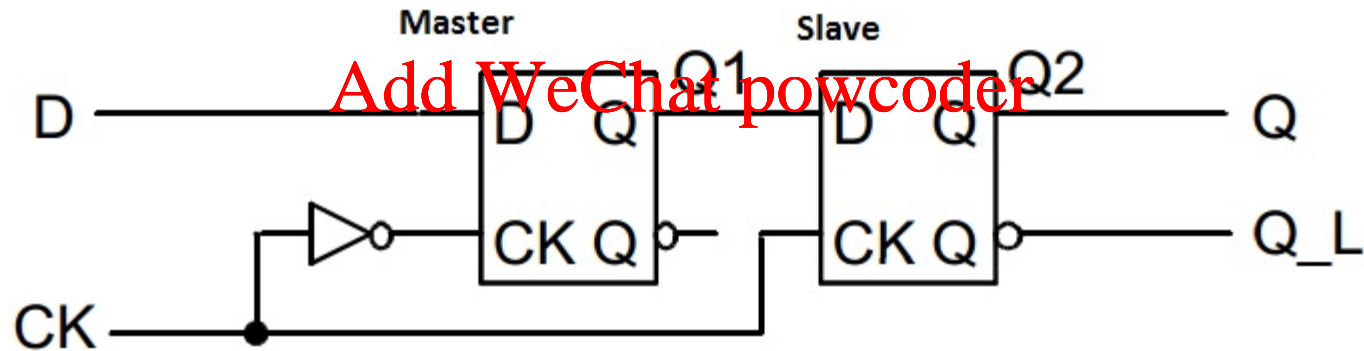- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since it's clk is low.





One way to make a Flip-Flop: Two Latches

 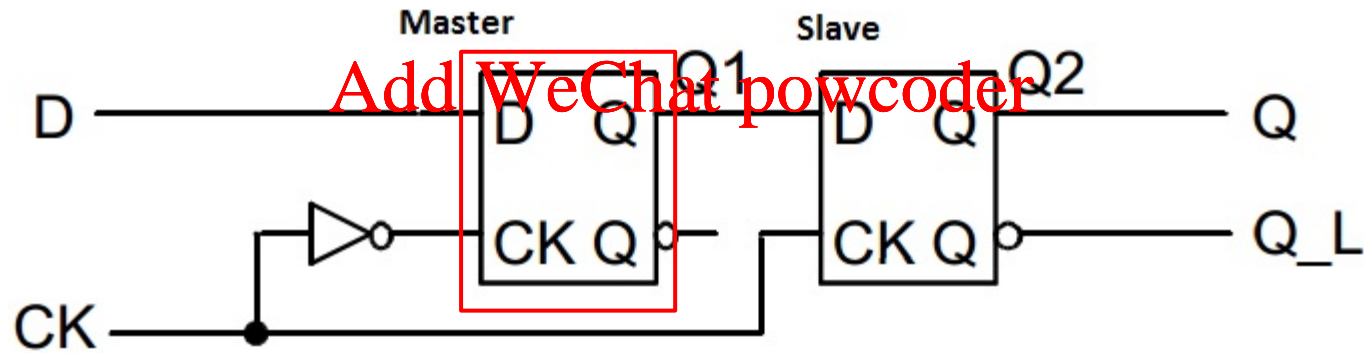- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since it's clk is low.





One way to make a Flip-Flop: Two Latches

 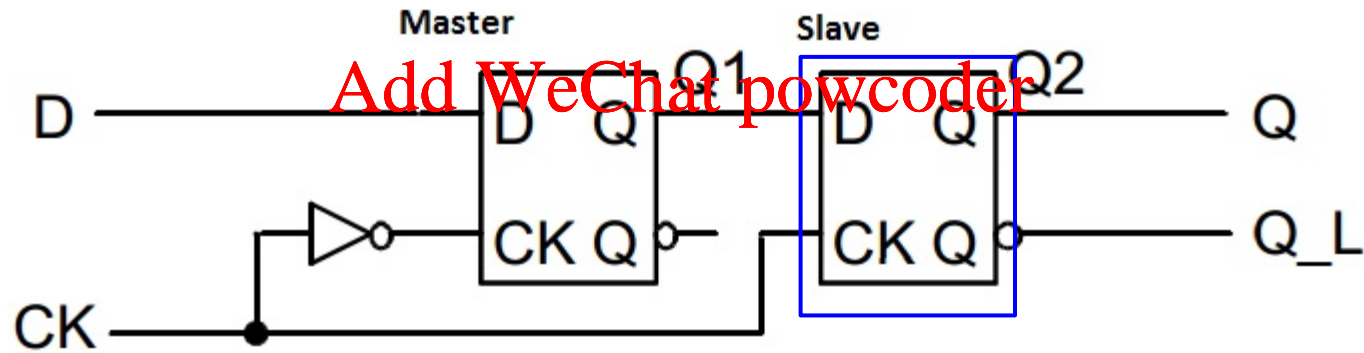- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since it's clk is low.





One way to make a Flip-Flop: Two Latches

 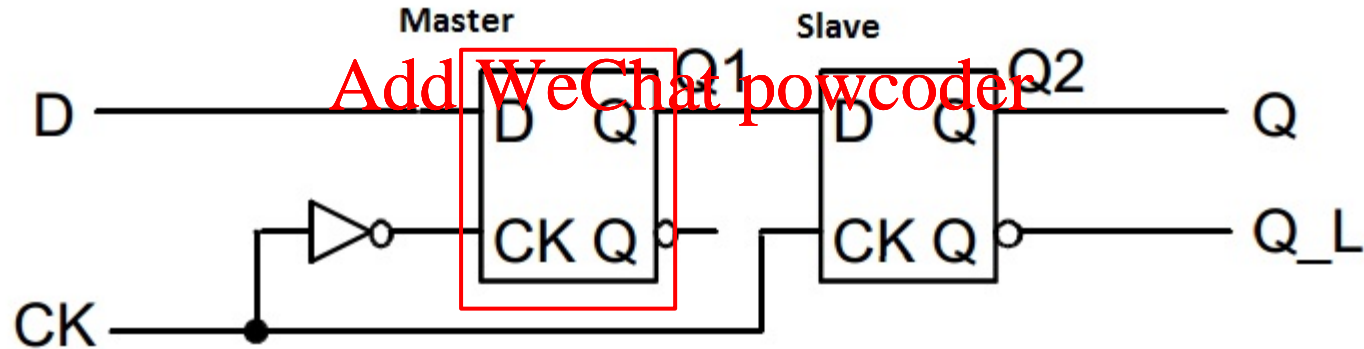- When clk transitions to high, slave captures last value of master which is now stored since its clk is low.
- When clk transitions to low, Master is open again but slave is closed, retaining value



One way to make a Flip-Flop: Two Latches

 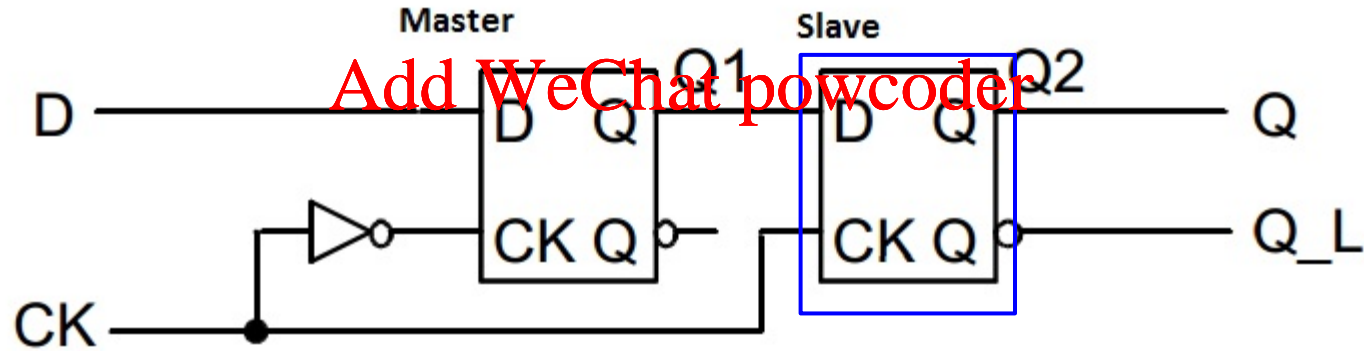- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since it's clk is low.



Reset-Set (RS) Latch – or \overline{SR}

- Two inputs: Set and Reset
- Set to 0 one of the two inputs at a time to store a value, S sets, R clears
- The transition to 00 generates an undefined output

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state



R-S Latch

 


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



R-S Latch Nor Gates

 


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Four SR Latch States: $S' 0, R' 0$

 

SR latch operation		
\bar{S}	\bar{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Four SR Latch States: $S' 0, R' 1$

 

SR latch operation		
\bar{S}	\bar{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Four SR Latch States: $S' 1, R' 0$

 

SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



 Four SR Latch States: $S' = 1, R' = 1$ Memory



SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

$Q = 1, Q' = 0$



 Four SR Latch States: $S' = 1, R' = 1$ Memory



SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

$Q = 1, Q' = 0$



 Four SR Latch States: $S' = 1, R' = 1$ Memory



SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

$Q = 0, Q' = 1$



 Four SR Latch States: $S' = 1, R' = 1$ Memory



SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

$Q = 0, Q' = 1$



D Latch

 

$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

E/clk	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state



D Latch

 

$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state


Assignment Project Exam Help
<https://powcoder.com>

Add WeChat powcoder

E/clk	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state
0	1	1	1	Q	Q'	Keep state



D Latch

 

$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

E/clock	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state
0	1	1	1	Q	Q'	Keep state
1	0	0	1	0	1	$D = Q$



D Latch

 

$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

E/clk	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state
0	1	1	1	Q	Q'	Keep state
1	0	0	1	0	1	$D = Q$
1	1	1	0	1	0	$D = Q$




Register

- A register stores a multi-bit value
- Common WE which latches the n-bit value


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

 


Other types of memory...

 

Assignment Project Exam Help

SRAM


(on-chip usually)

 

DRAM

(off-chip usually)

Add WeChat powcoder

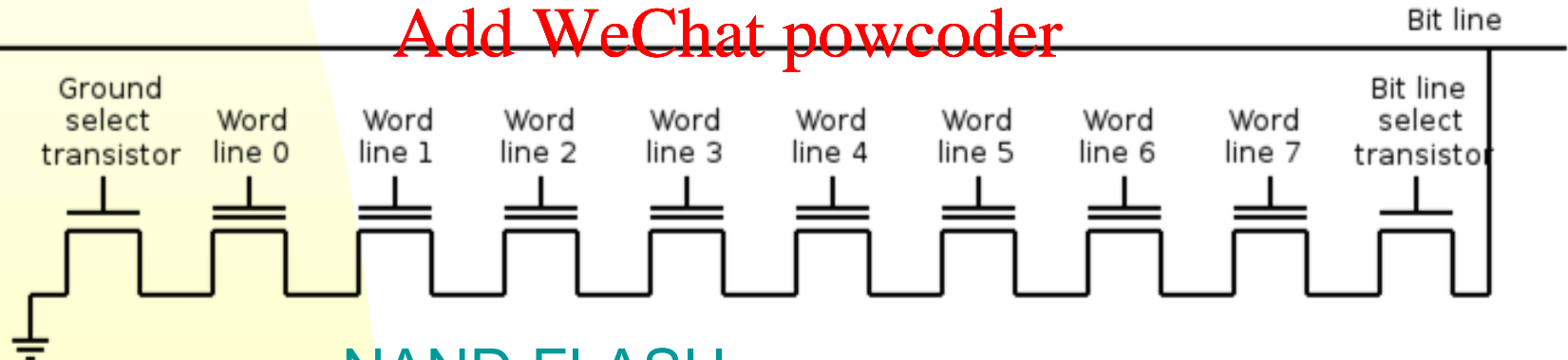

NAND FLASH

(on or off-chip, non-volatile)



Memory

Now that we know how to store bits,
we can build a memory – a logical $k \times m$ array of stored bits.

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder


Address Space:

number of locations
(usually a power of 2)


$k = 2^n$
locations

Addressability:

 
number of bits per location
(e.g., byte-addressable)




$2^2 \times 3$ Memory

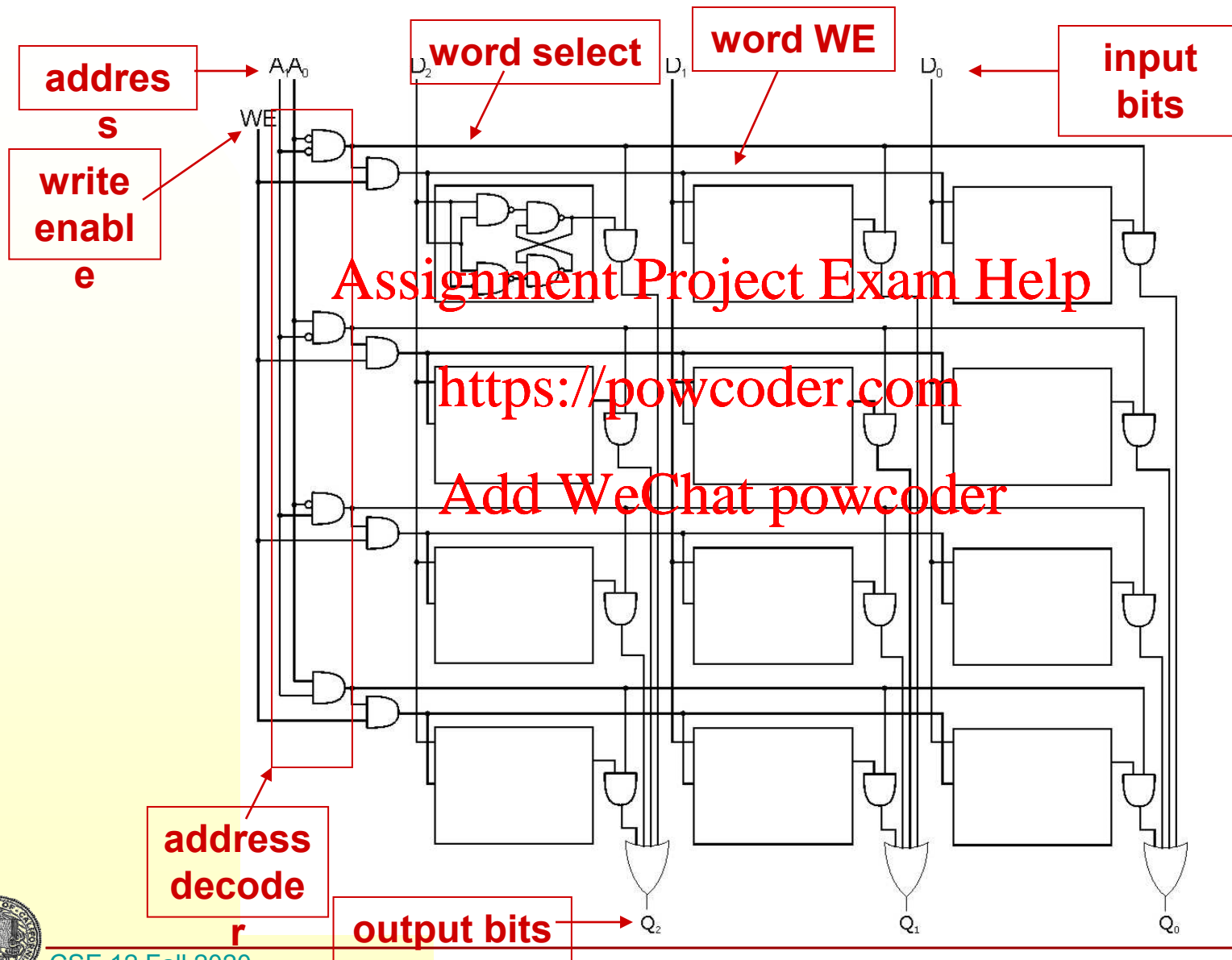

Let's Build a Computer

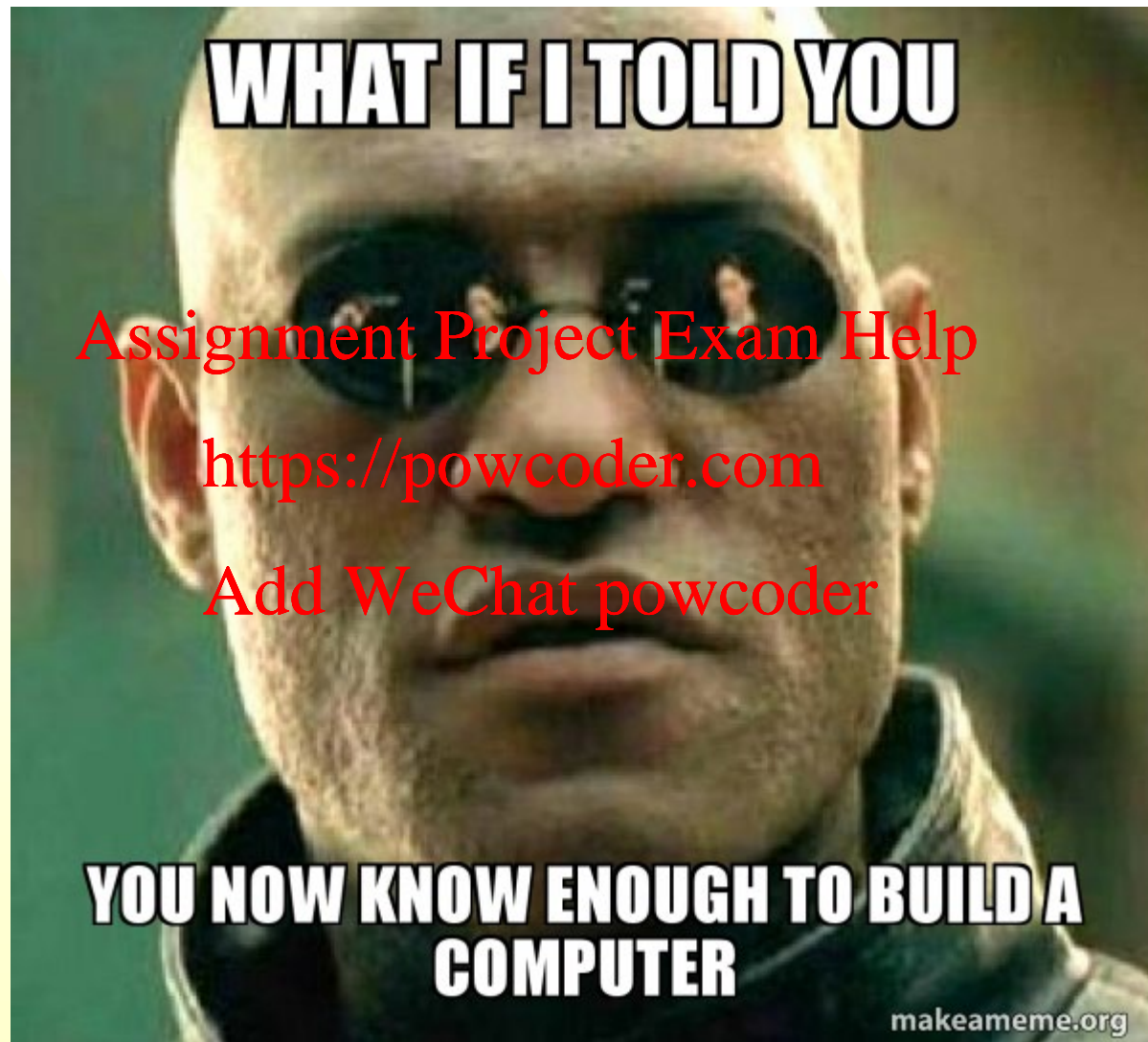

Example of State Machine: Traffic Light

 


Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder




State Machine: Overview

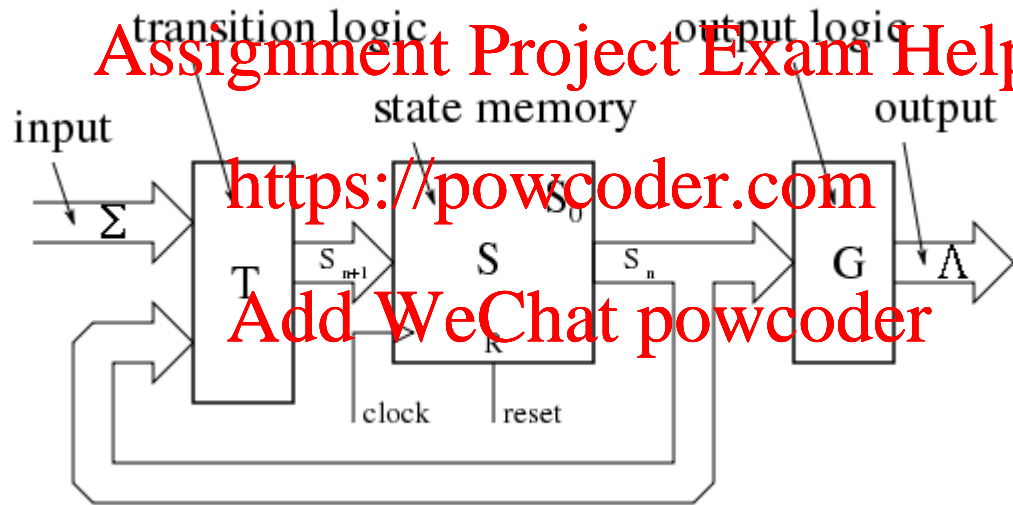

State Machine: Traffic Light

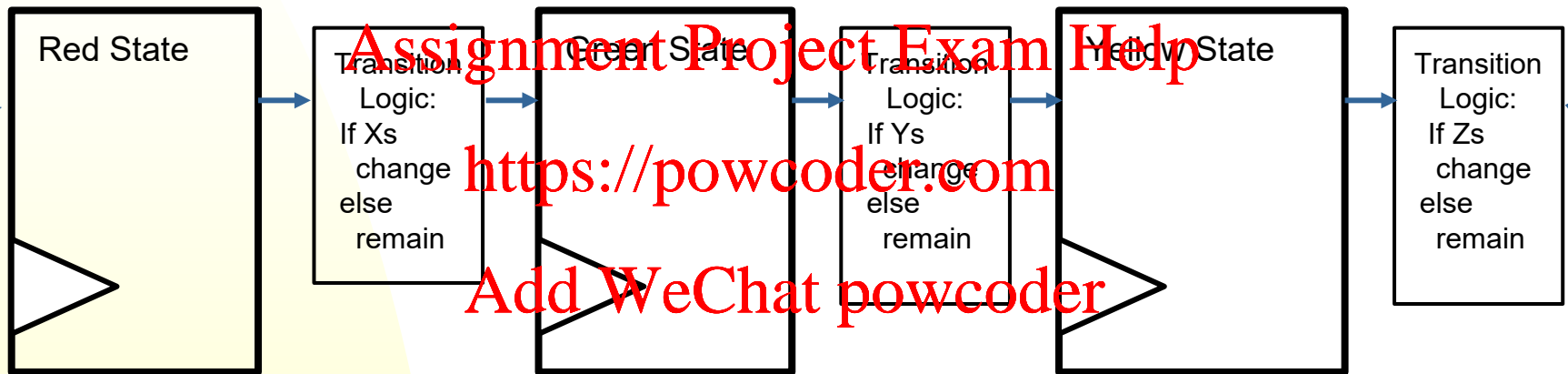


State Machine: Traffic Light

 

- Start off in default state Red




State Machine: Traffic Light

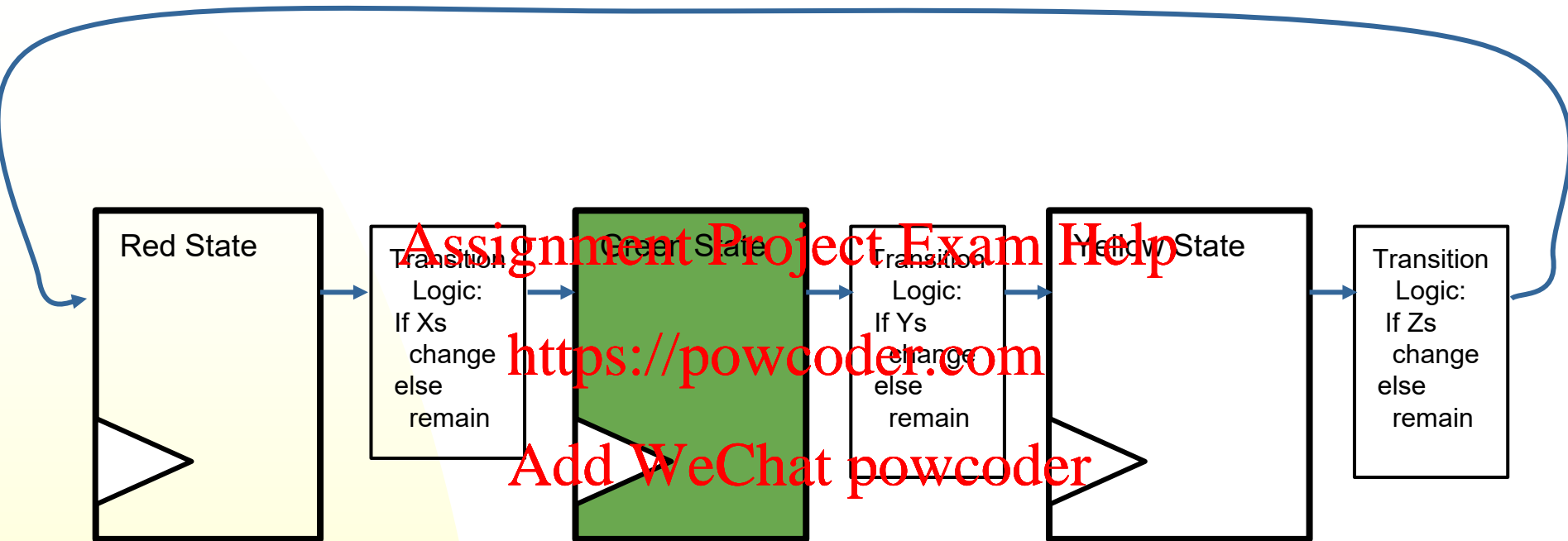

- After a specified time Xs switch to next state




State Machine: Traffic Light

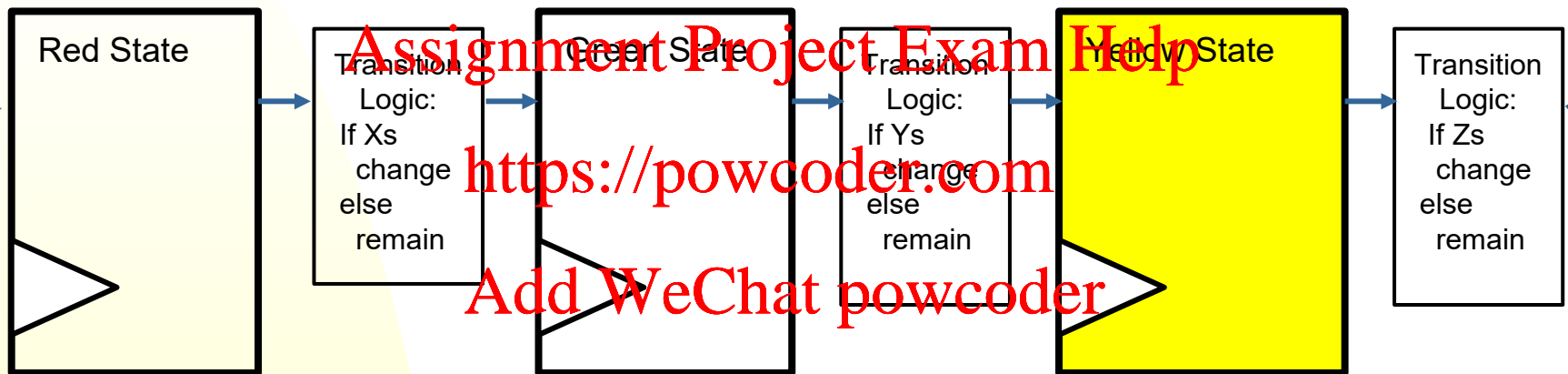

- After a specified time Ys switch to next state




State Machine: Traffic Light

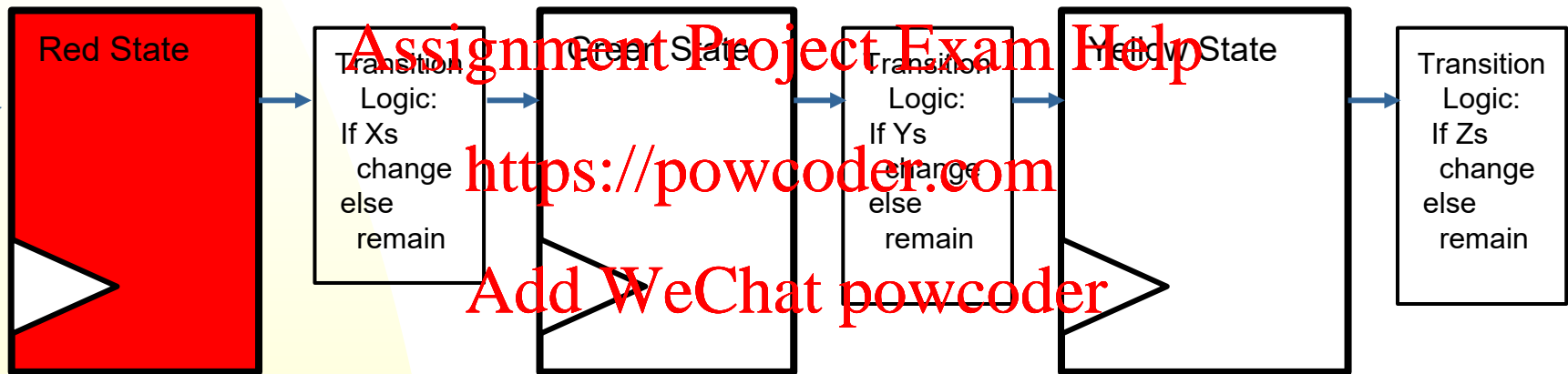

- After a specified time Zs switch to next state which is Red.



Basic Computer

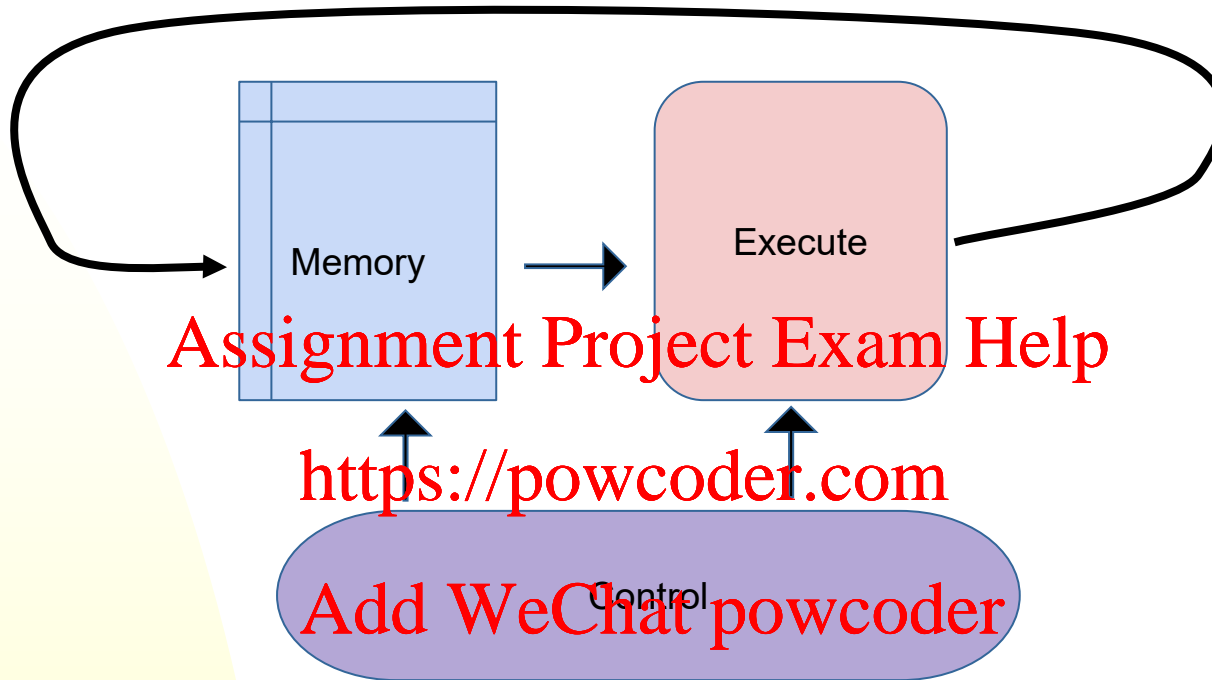

Memory: Could be Flip Flops, SRAM/DRAM, Flash etc

Execute: Combinational Logic (Adder, Shifter, Rotation etc)

Control: Finite State Machine (combination of sequential and combinational logic circuits)



