
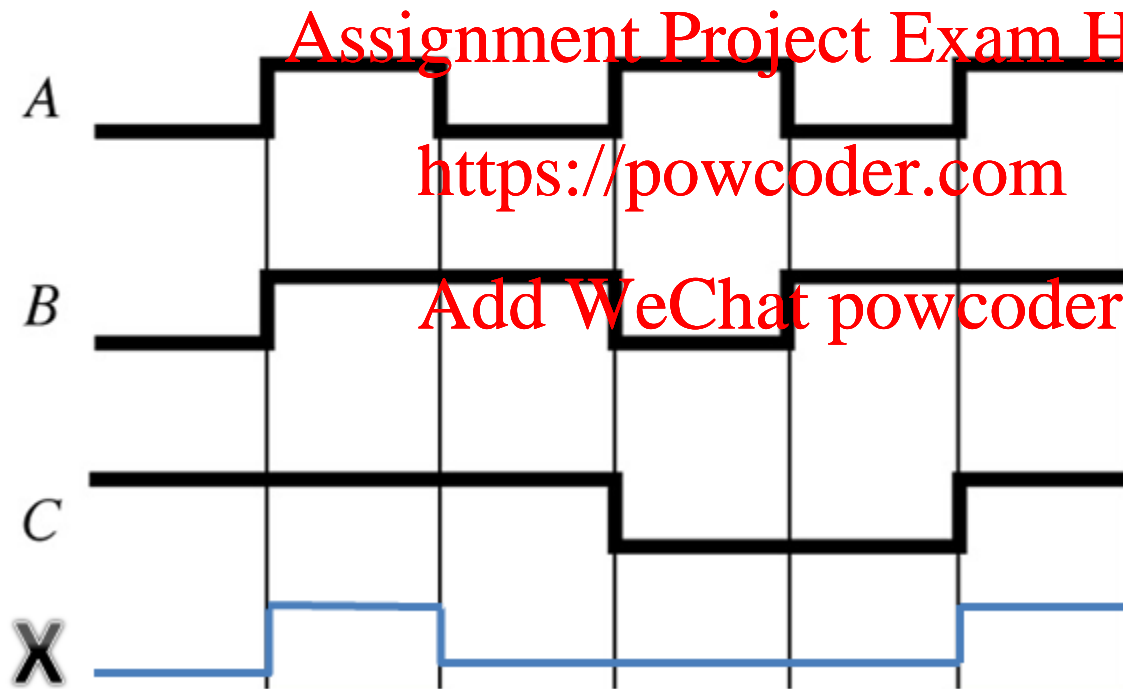


On wave diagrams

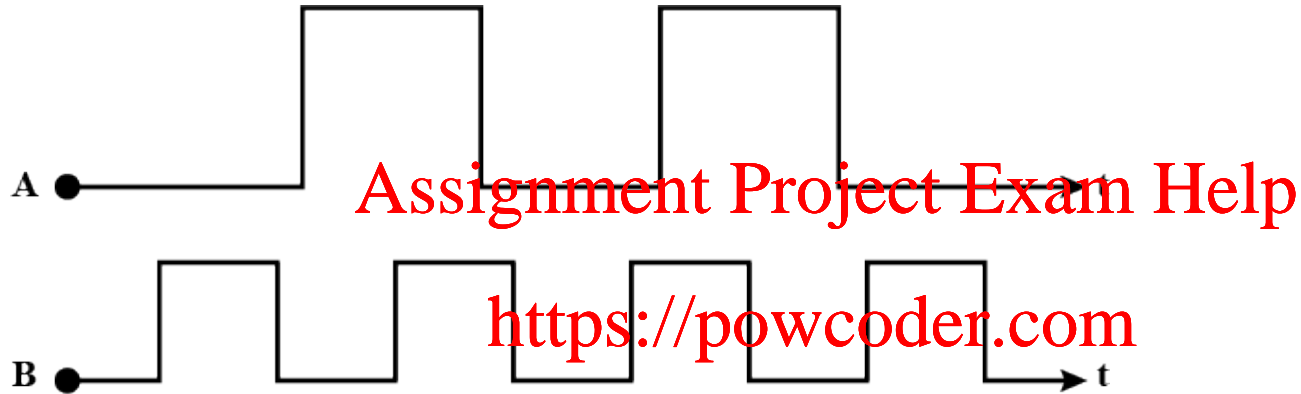


On wave diagrams

$$Y = A \text{ OR } B$$



Add WeChat powcoder


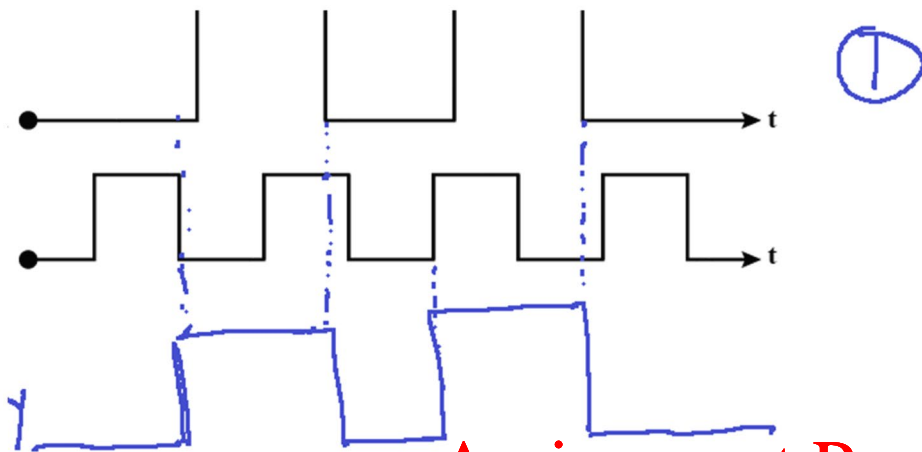
What will be the waveform of output Y
(Class Poll)



Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

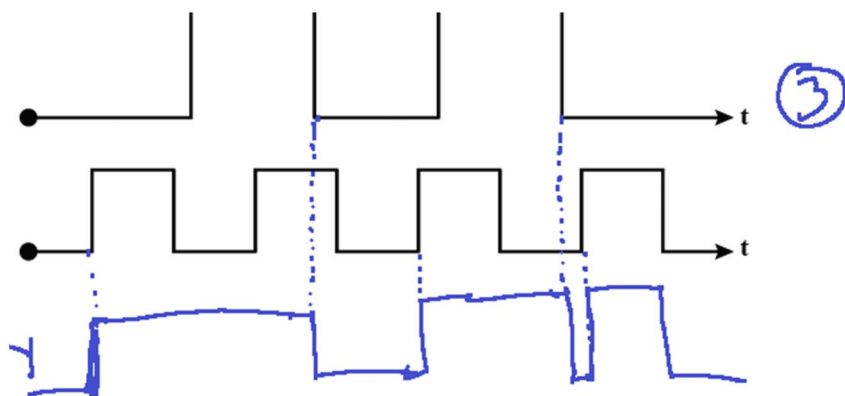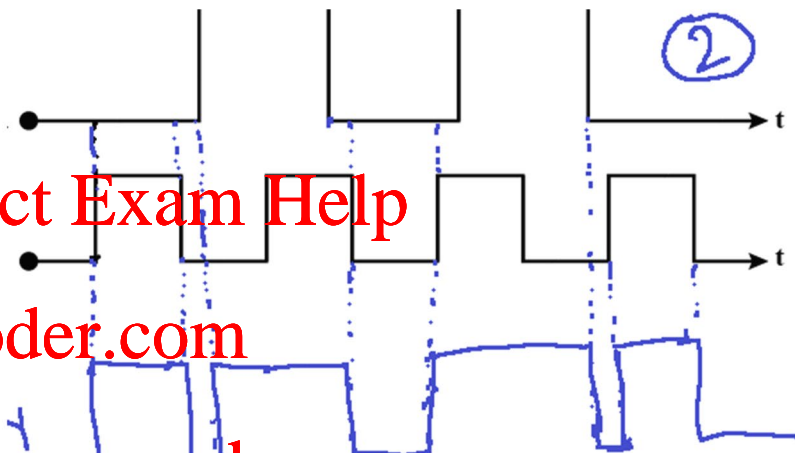

Sequential Circuits and Memory

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Combinational vs. Sequential

- Combinational circuit
 - ◆ Always gives the same output for a given set of inputs
 - ◆ Example: Adder always generates sum and carry, regardless of previous inputs
- Sequential circuit
 - ◆ Remembers previous input
 - ◆ Output depends on state and input

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Sequential Circuits

- Store information
- Output depends on stored information (state) plus input
 - ◆ So a given input might produce different outputs, depending on the stored information
- Example: ticket counter
 - ◆ Advances when you push the button
 - ◆ Output depends on previous state

Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder

State Machine


The basic type of sequential circuit

- ◆ Combines combinational logic with storage
- ◆ “Remembers” state, and changes output (and state) based on inputs and current state

<https://powcoder.com>

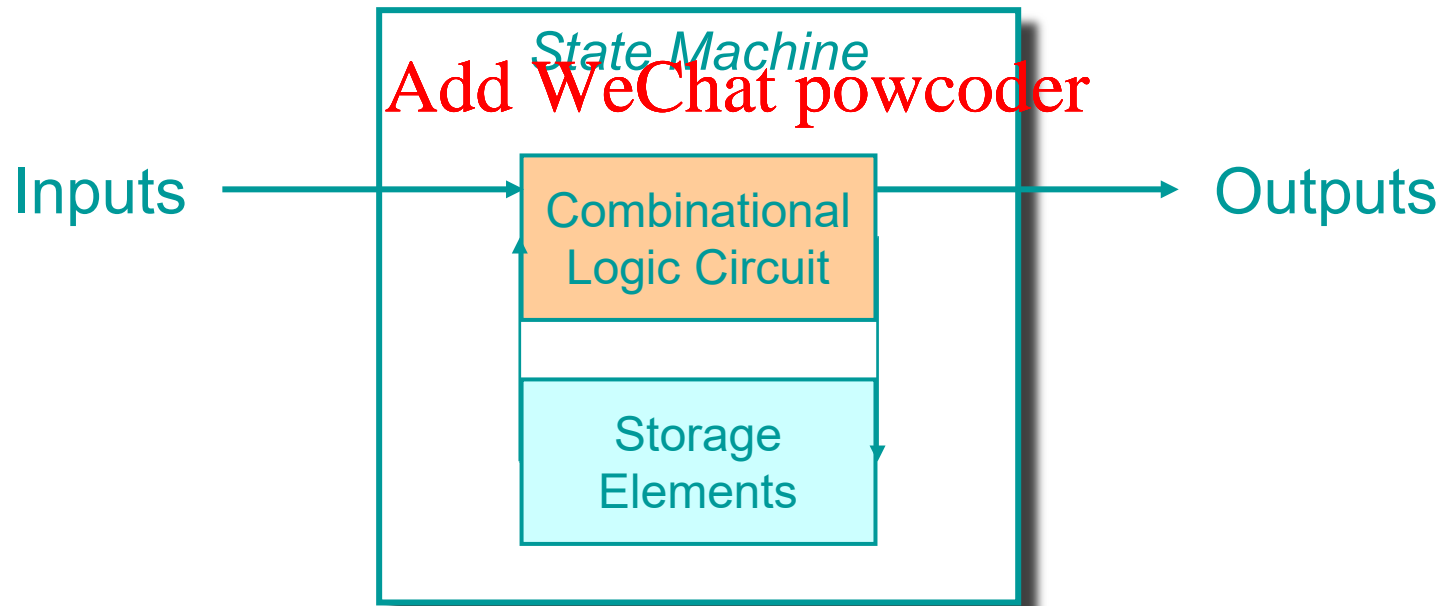

Example of State Machine: Traffic Light

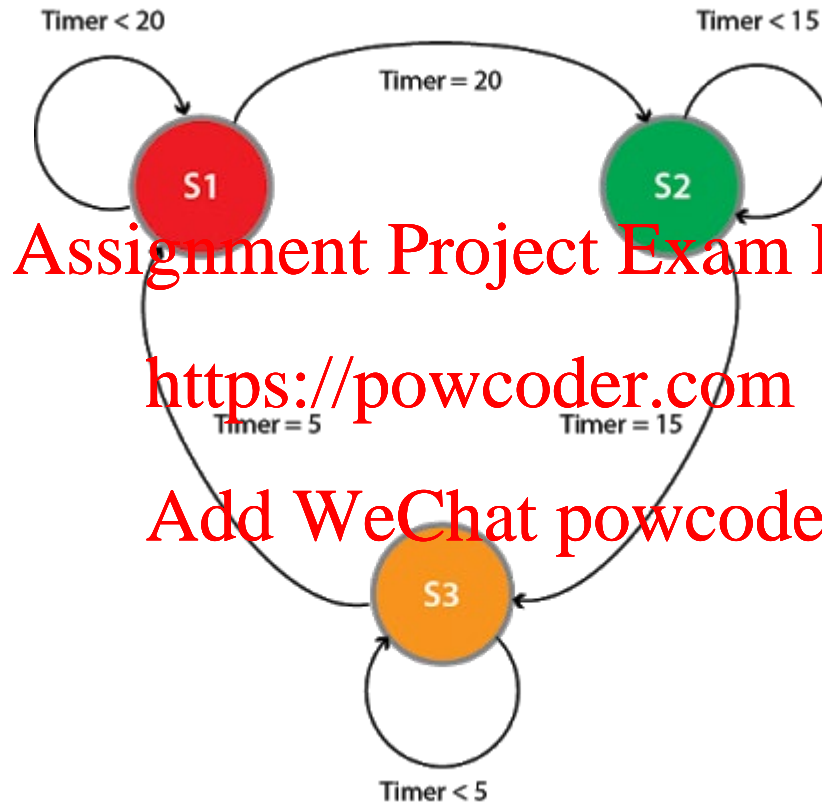


Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder


State Machine: Overview

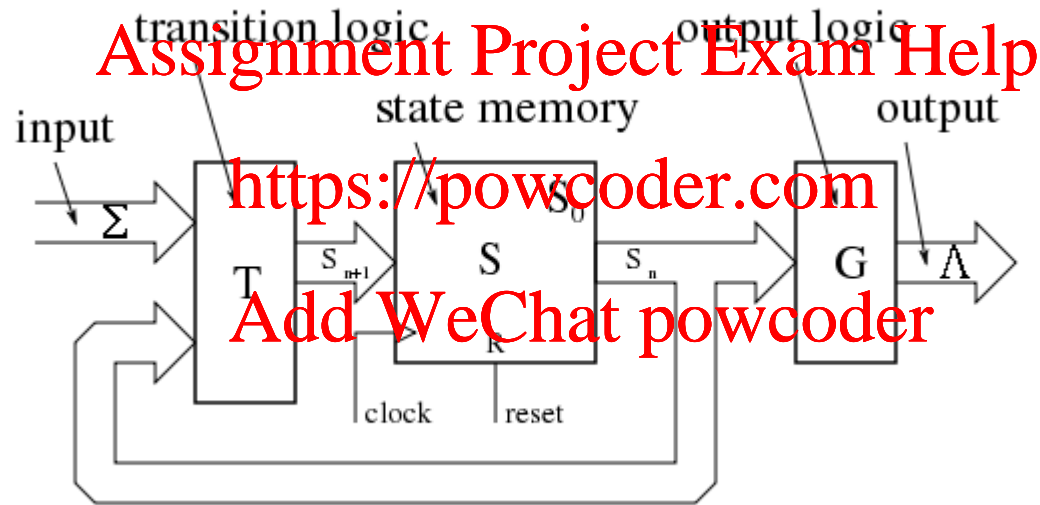

State Machine: Traffic Light

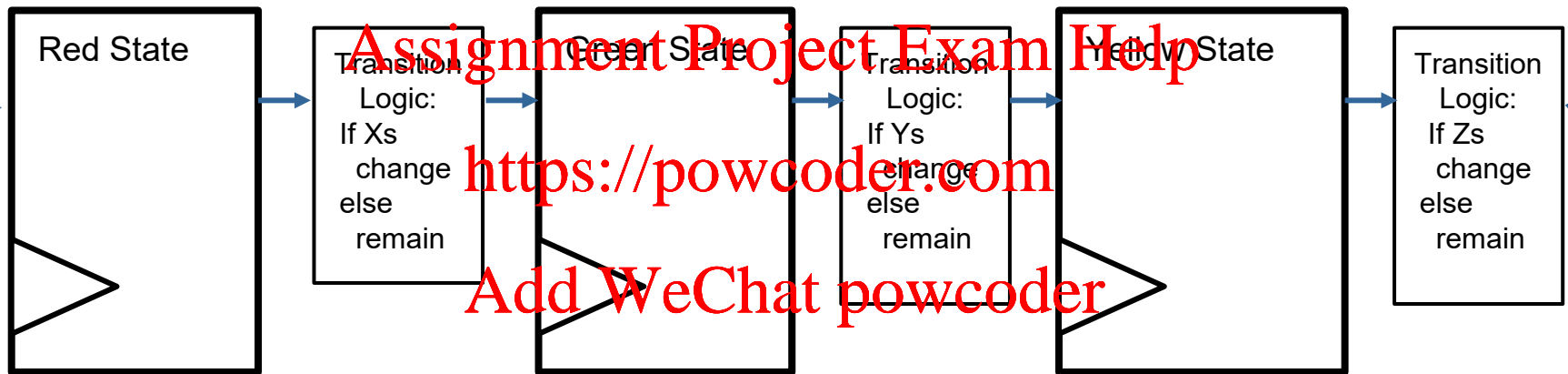


State Machine: Traffic Light

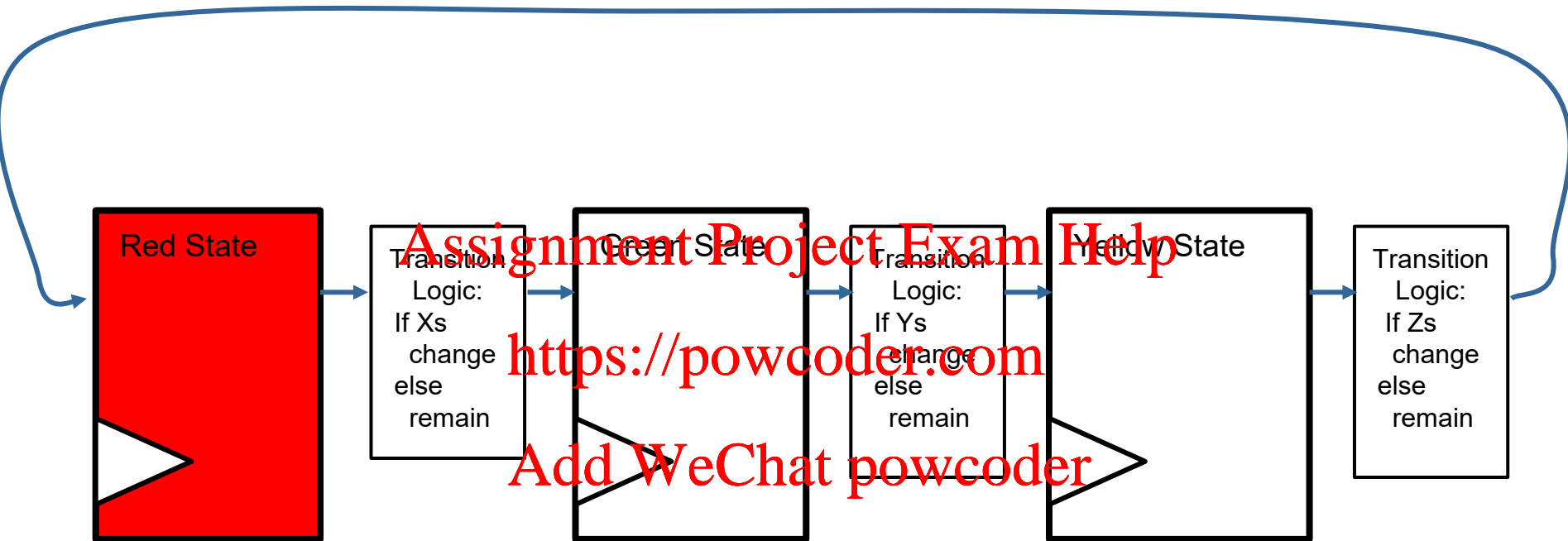


- Start off in default state Red

State Machine: Traffic Light

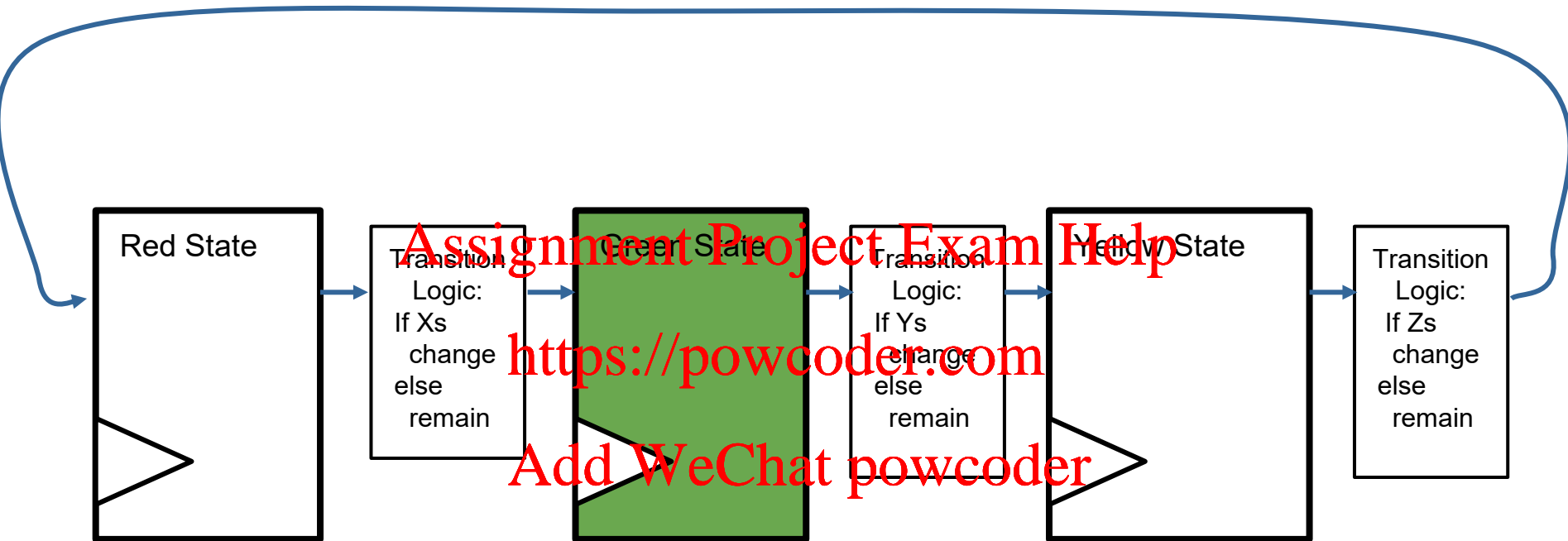


- After a specified time Xs switch to next state

State Machine: Traffic Light

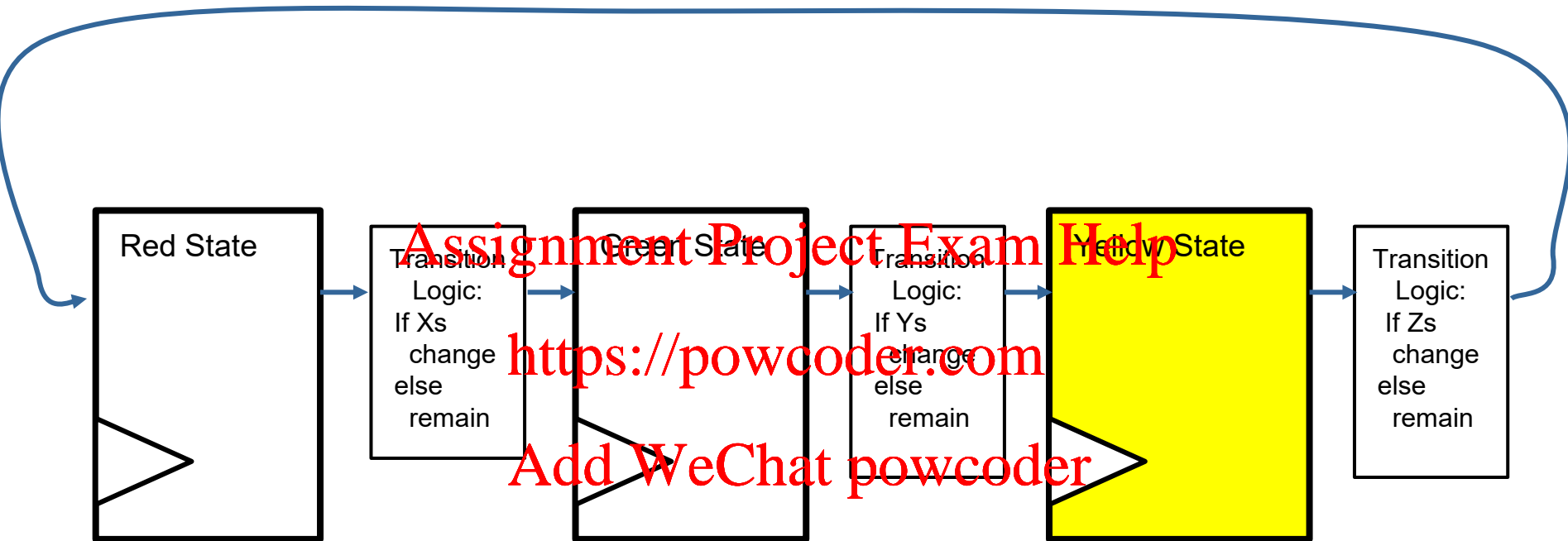

- After a specified time Ys switch to next state

State Machine: Traffic Light

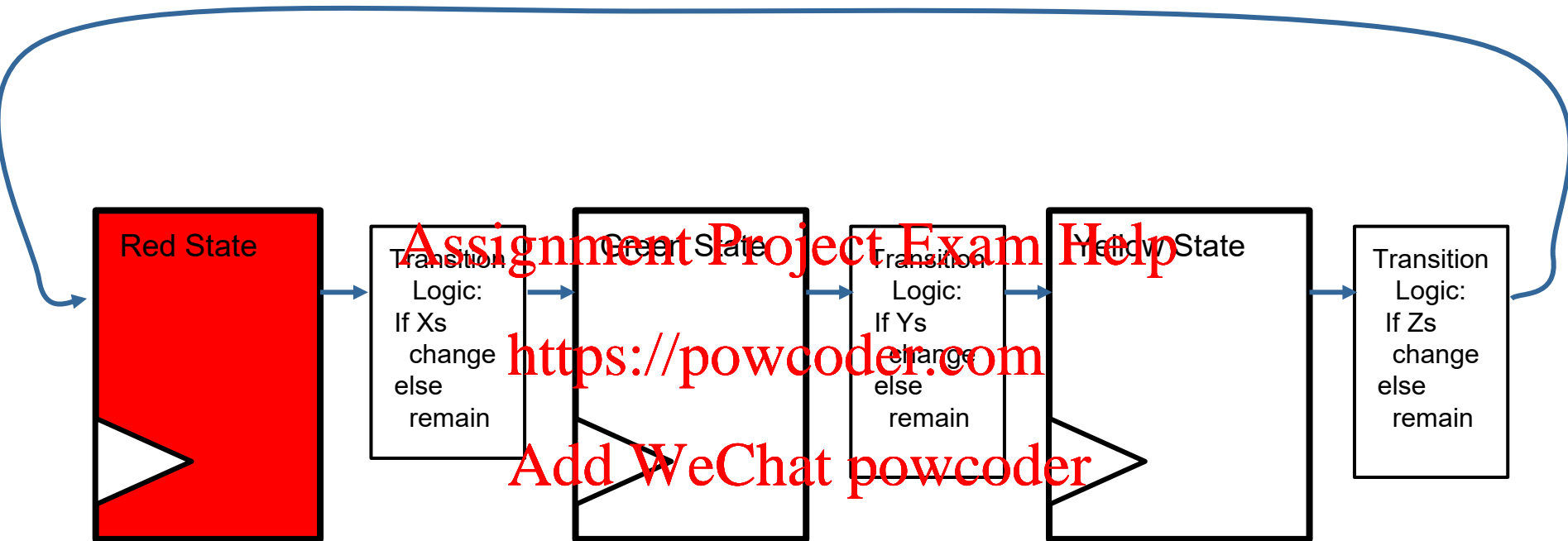


- After a specified time Zs switch to next state which is Red.

Latch


- Output is equal to Input when clk is high.
- Level sensitive
- Stores last value when clk is low.

Assignment Project Exam Help

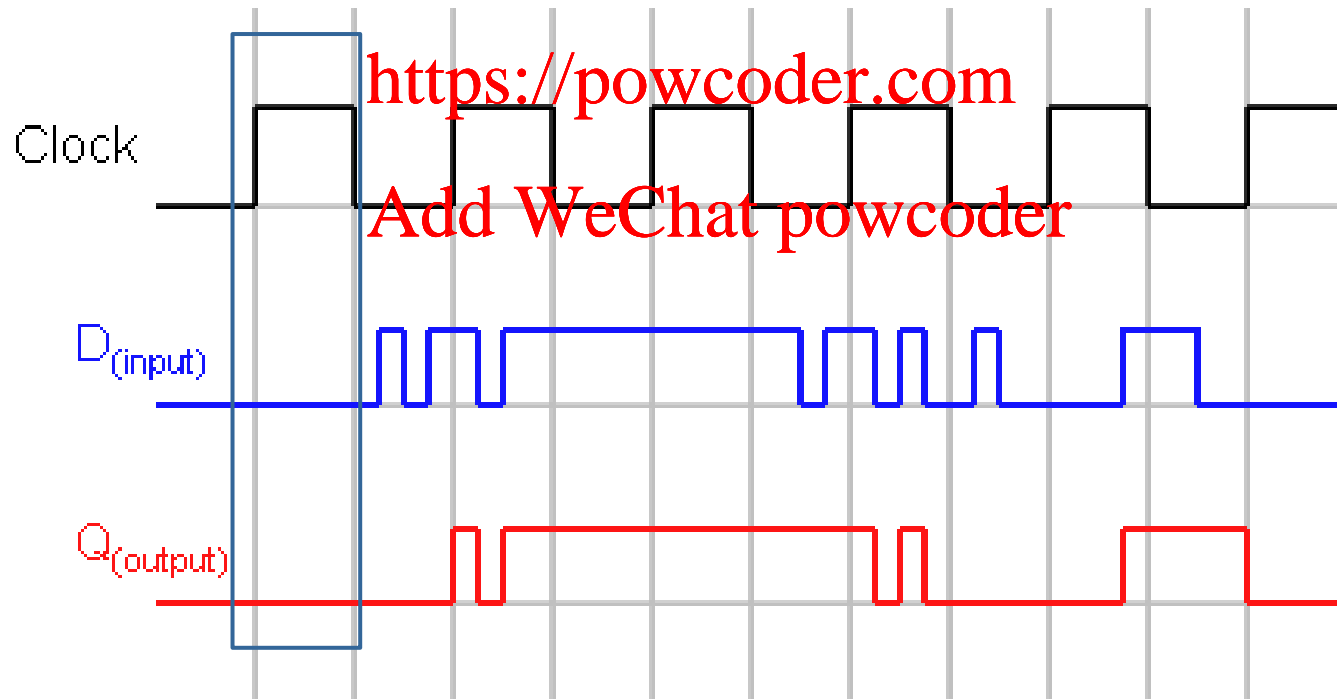


Latch

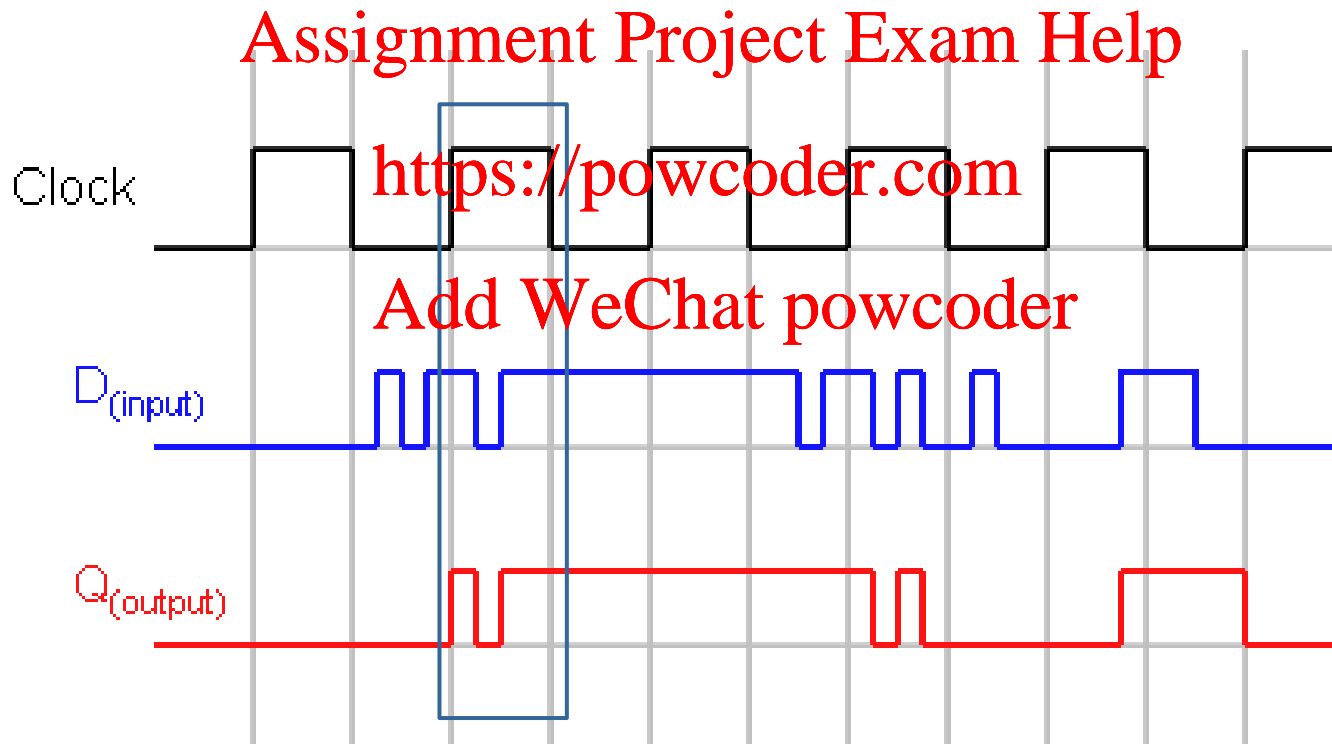- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

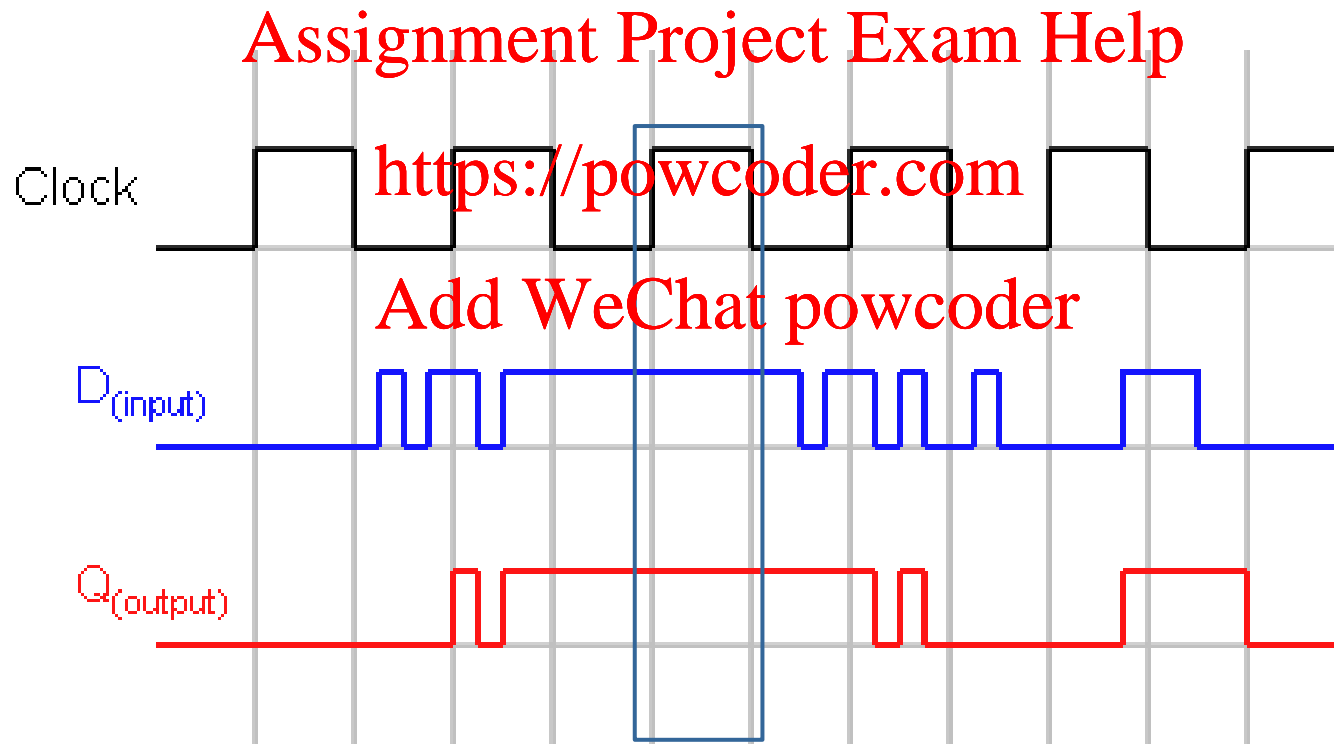- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

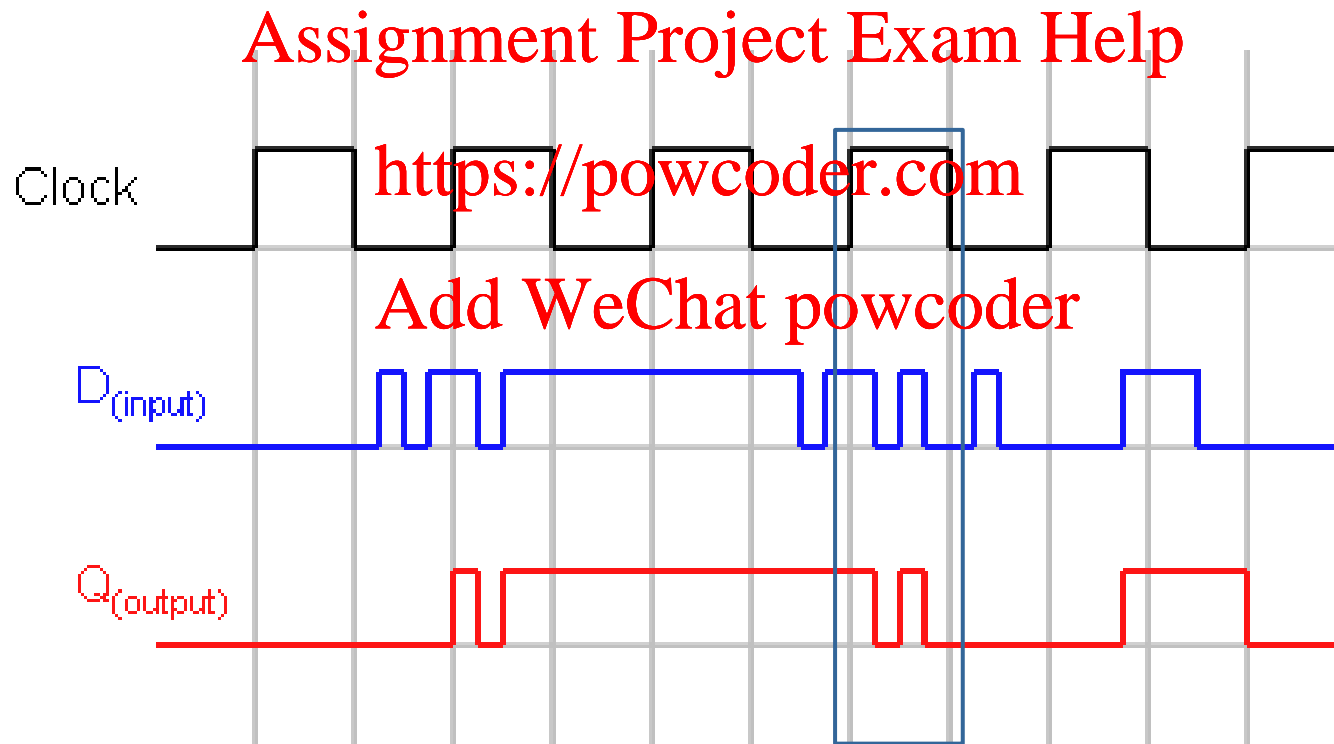- Output is equal to Input when clk is high.
- Stores last value when clk is low.




Latch

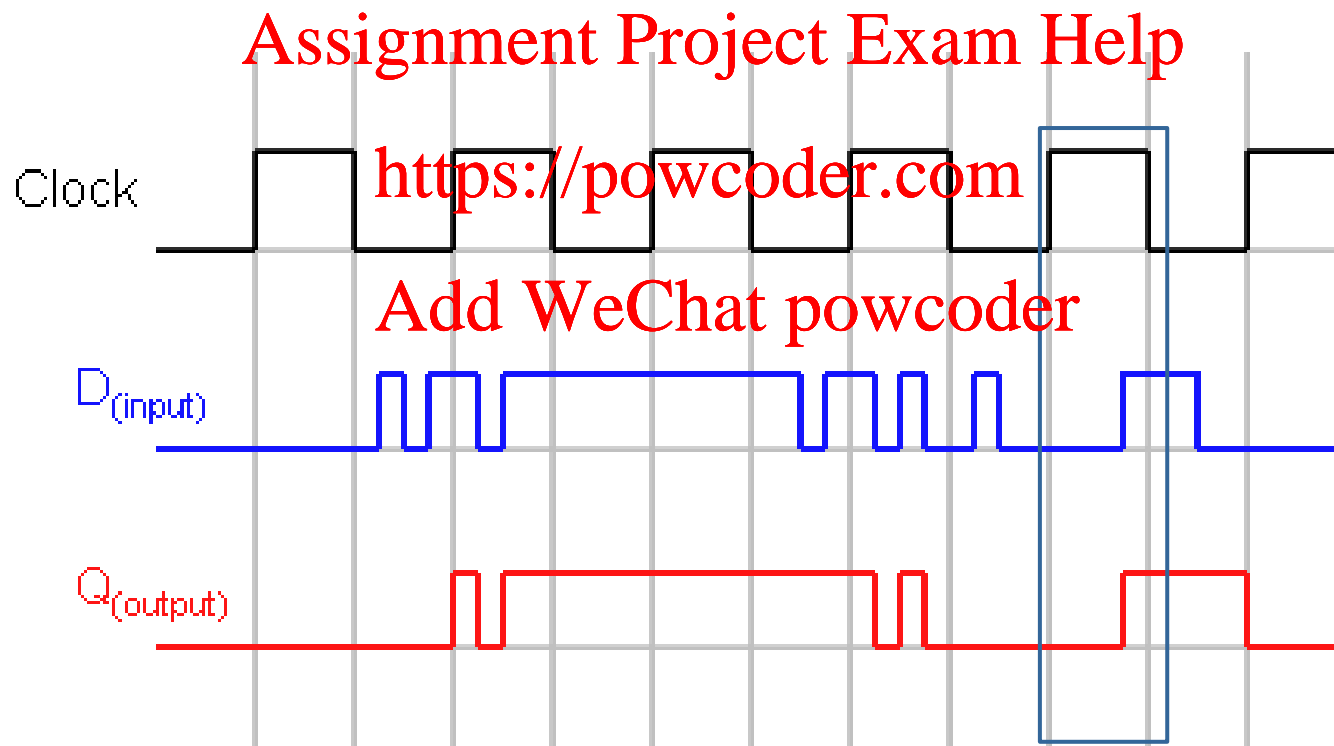- Output is equal to Input when clk is high.
- Stores last value when clk is low.



Latch

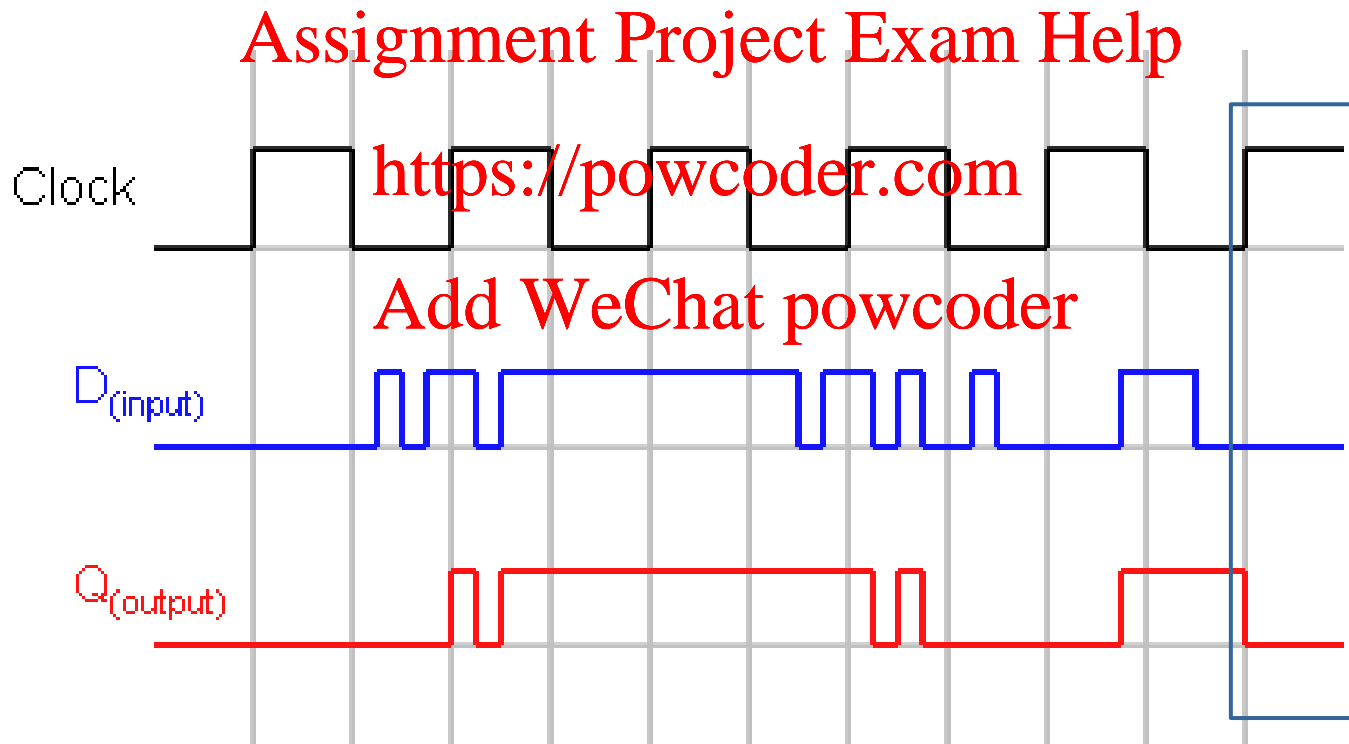- Output is equal to Input when clk is high.
- Stores last value when clk is low.



D Flip-Flops

Memory device

- Can be positive **edge** triggered or negative **edge** triggered (by a clock usually abbreviated by clk)


Assignment Project Exam Help

- Different types: RS, JK
- Inputs/Outputs:

<https://powcoder.com>

- ◆ D: input signal
- ◆ clk: Clock signal
- ◆ en: if 0 Q holds its value, if 1, Q becomes D at clk edge.
- ◆ rst: if 1 then Q becomes 0
- ◆ Q: output signal


Add WeChat powcoder

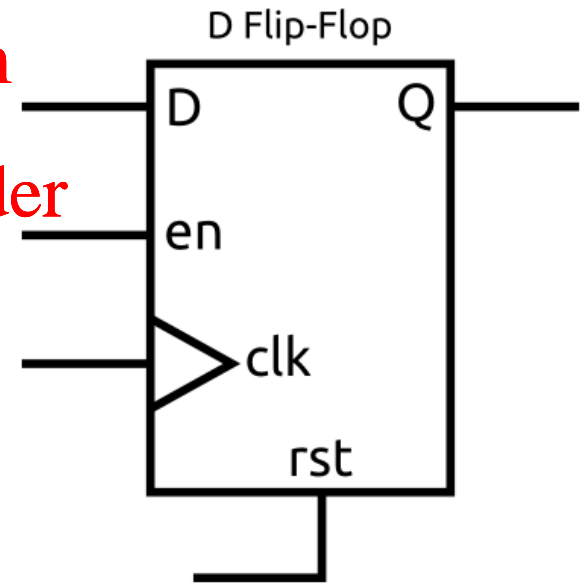

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge (0 -> 1).
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = 1/period


Assignment Project Exam Help

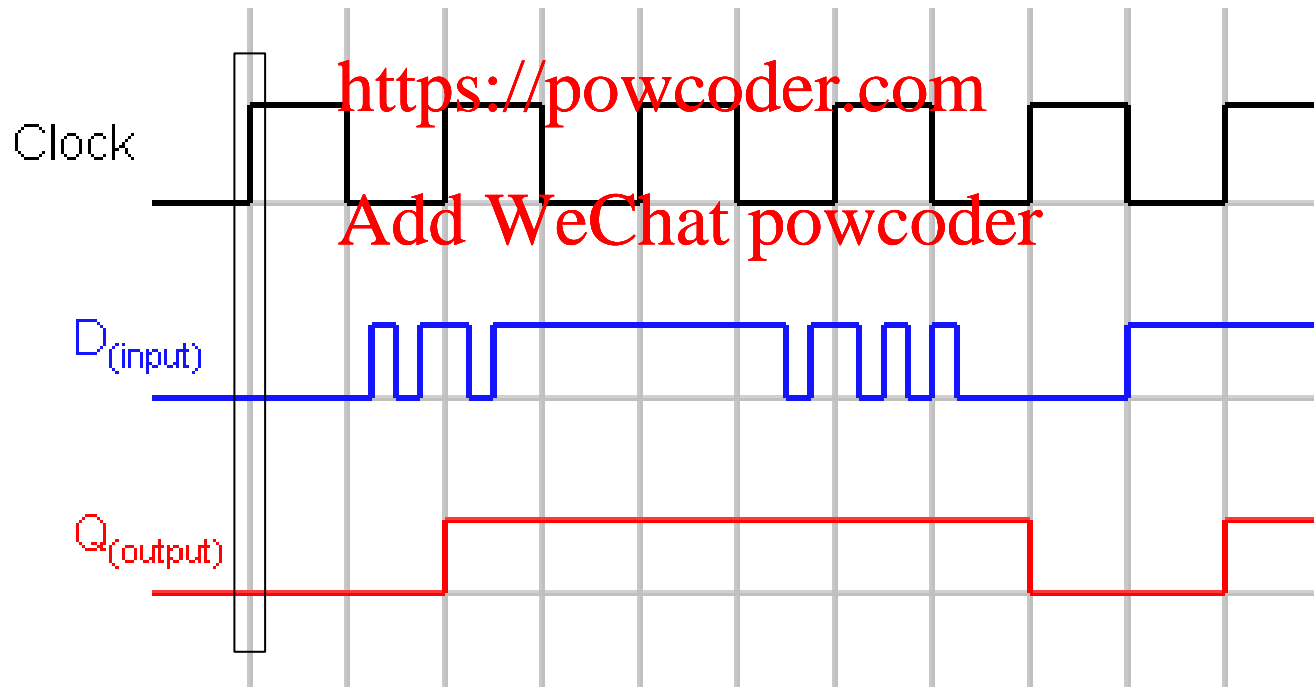

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge (0 -> 1).
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = 1/period


Assignment Project Exam Help

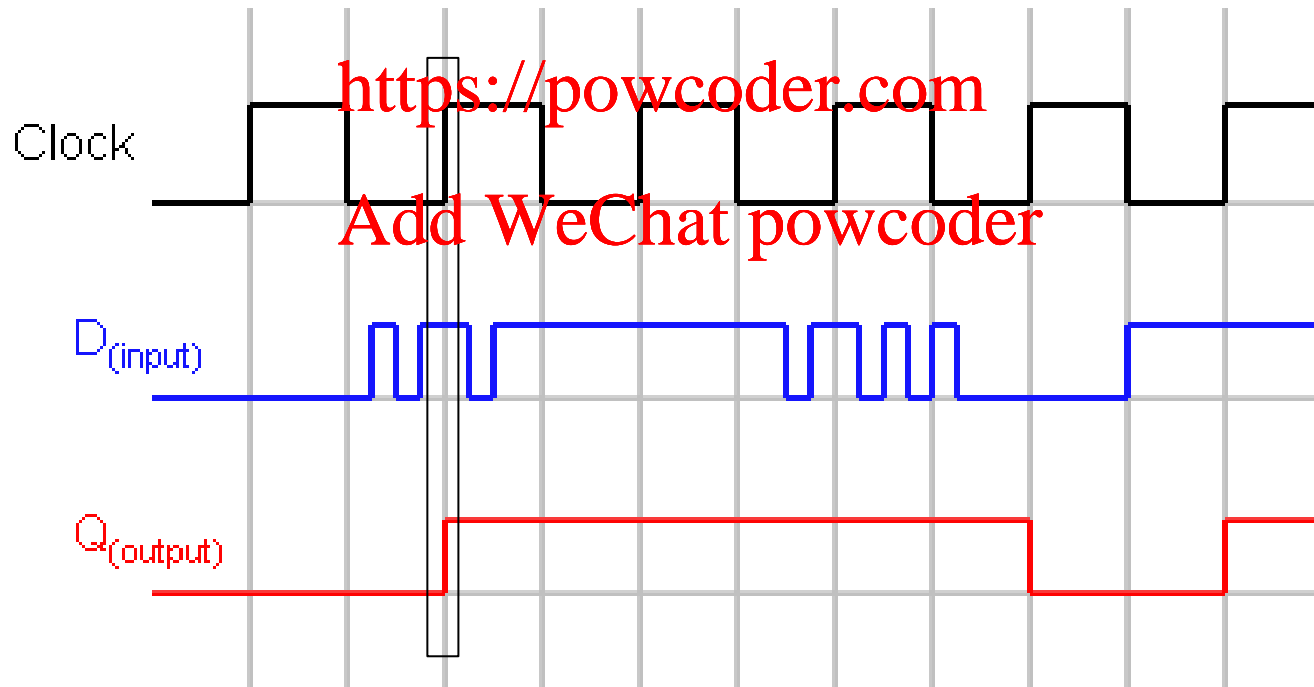

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$


Assignment Project Exam Help

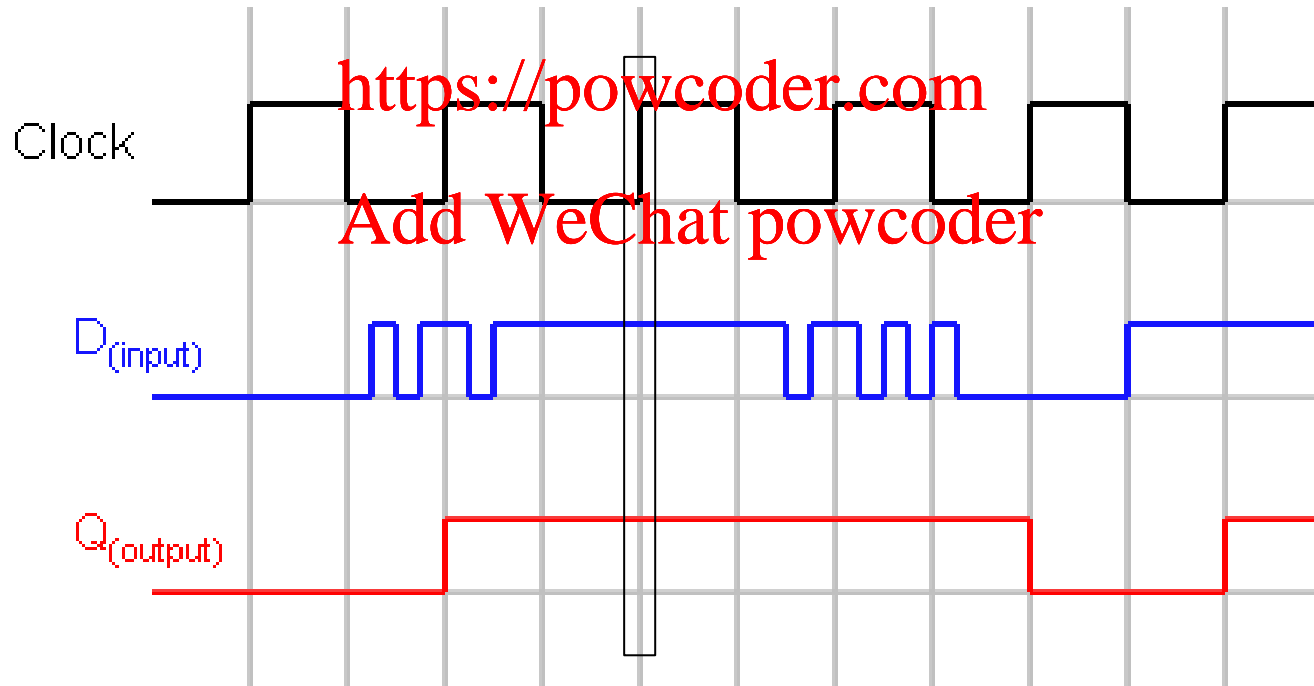

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$


Assignment Project Exam Help

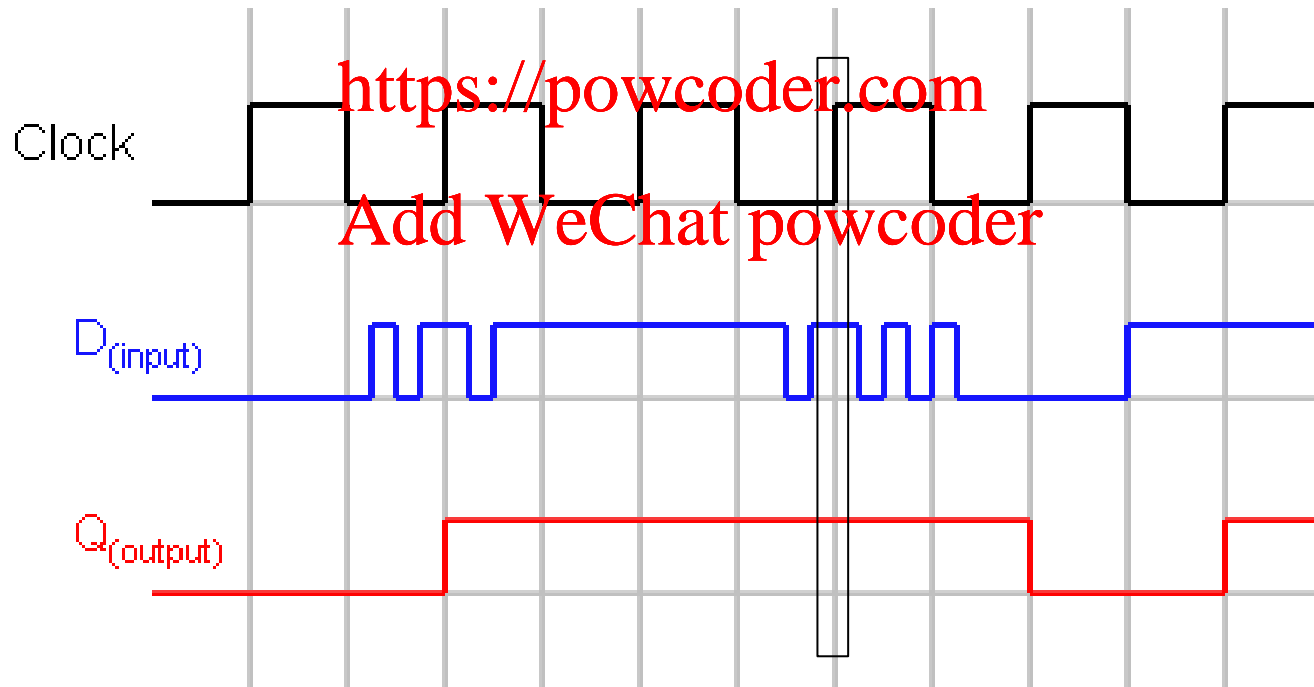

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$


Assignment Project Exam Help

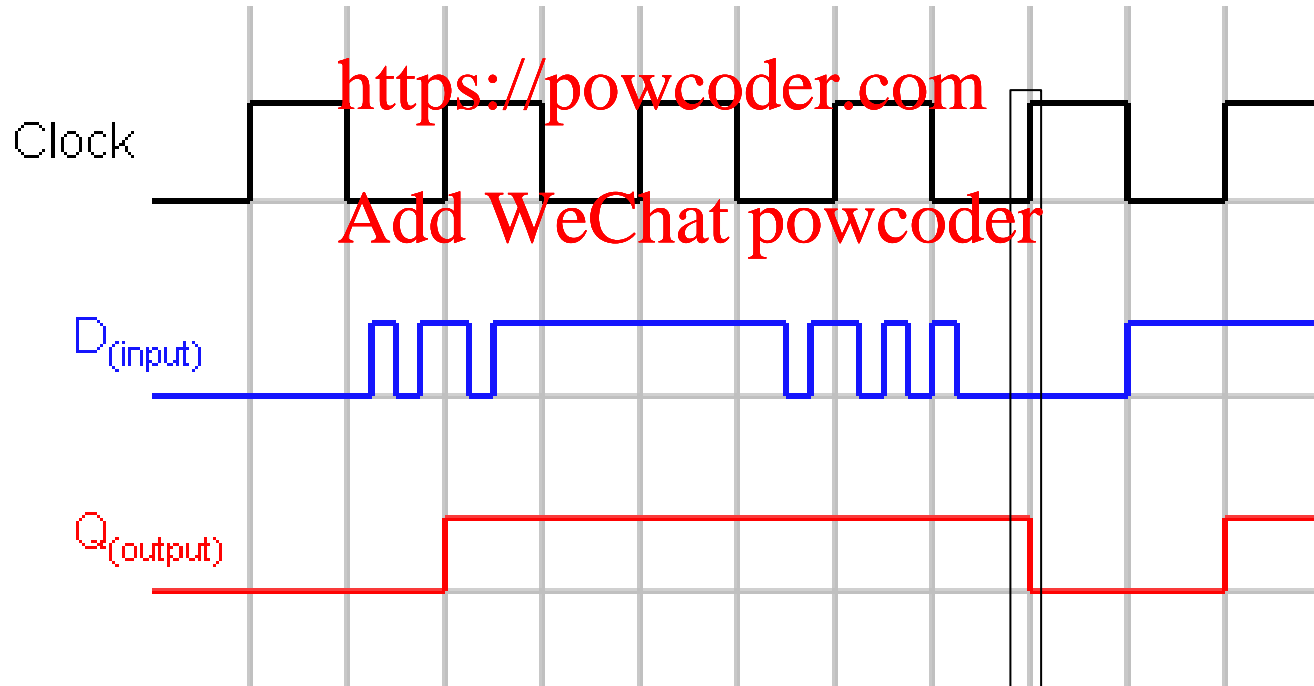

D flip-flop(positive-edge) timing diagram

- Q becomes D at positive clk edge.
 - ◆ Stores value until next positive clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$

Assignment Project Exam Help

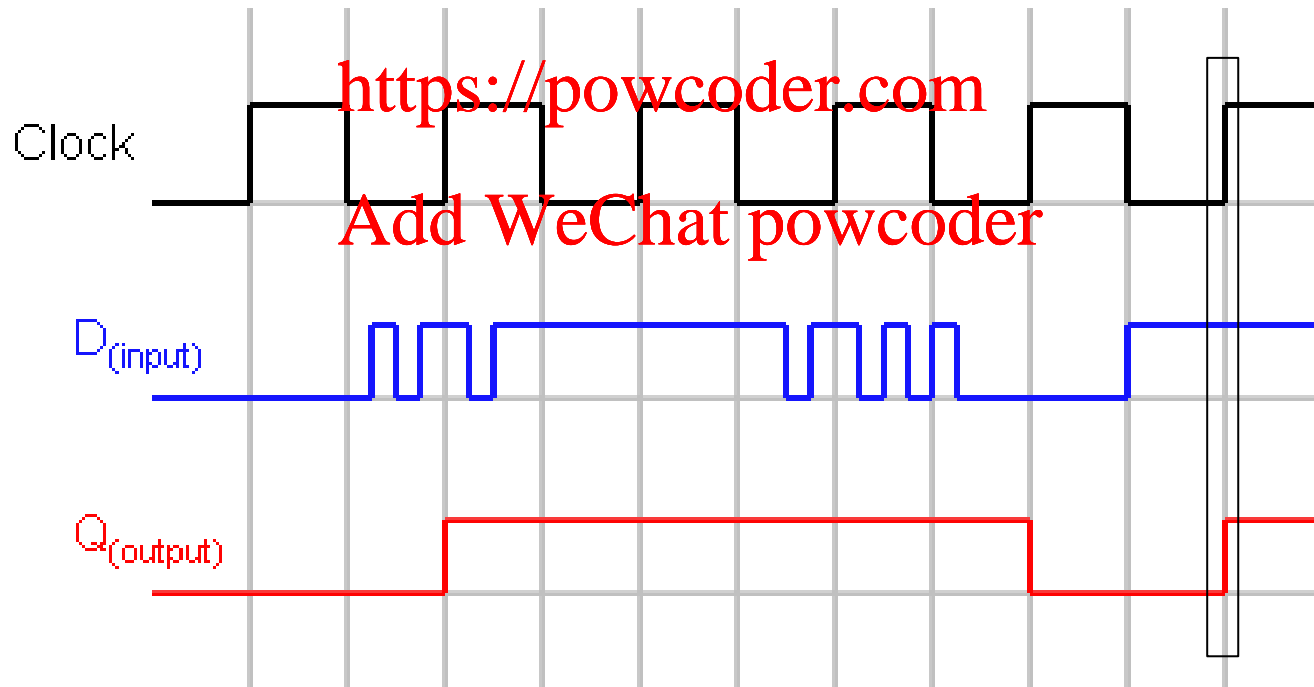

D flip-flop(negative-edge) timing diagram

- Q becomes D at negative clk edge.
 - ◆ Stores value until next negative clk edge.
- clk oscillates between 0 and 1
 - ◆ frequency = $1/\text{period}$

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

Setup and Hold Time


- Setup time: Time before clock edge where signal has to be stable
- Hold time: Time after clock edge where signal has to be stable

Assignment Project Exam Help

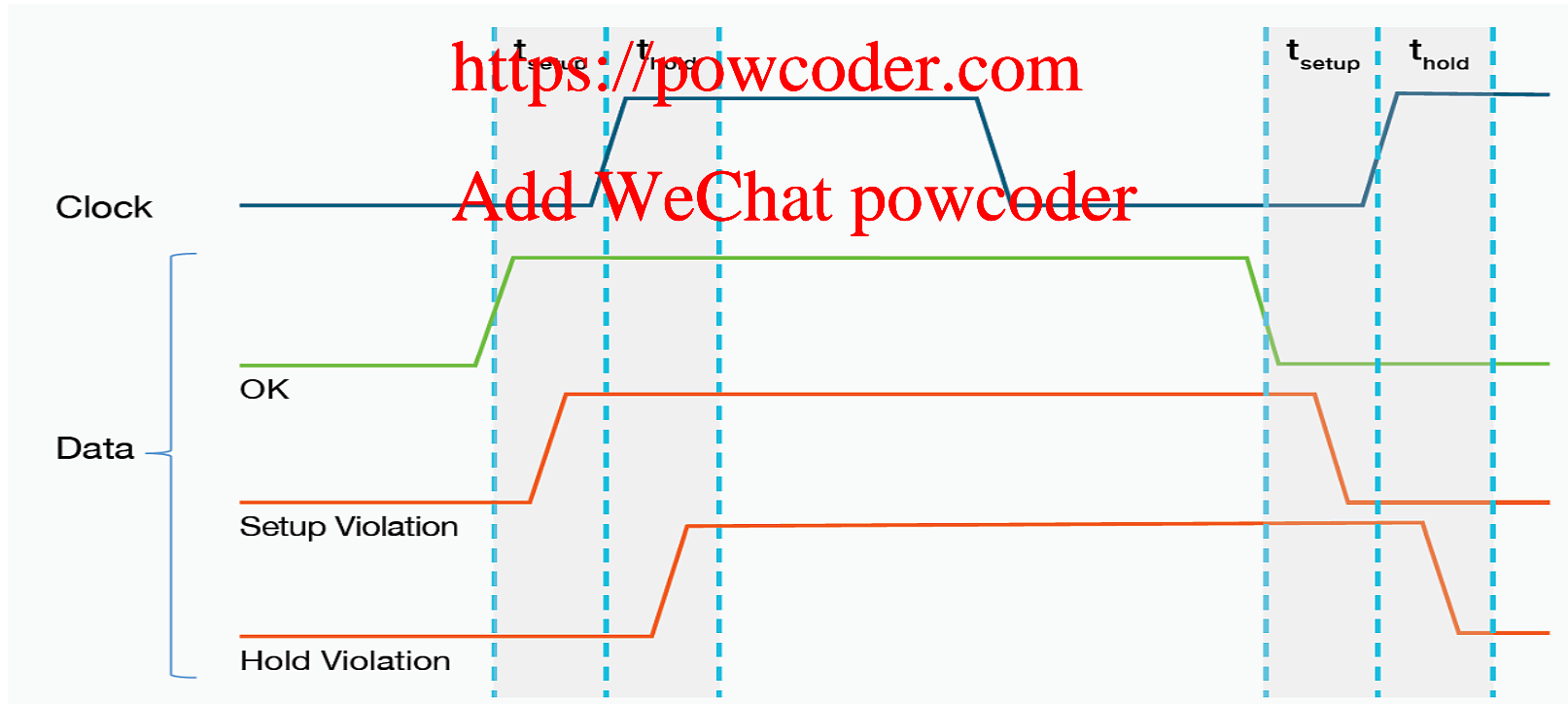


One way to make a Flip-Flop: Two Latches

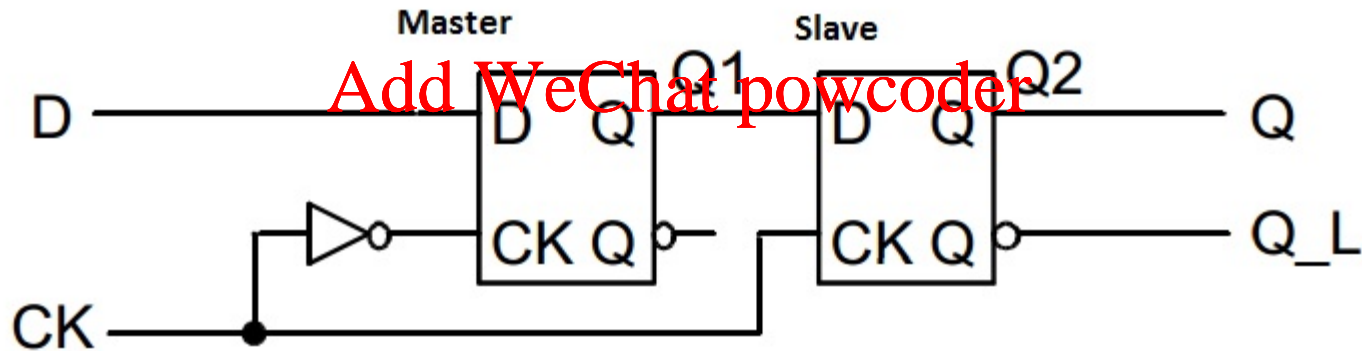- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since it's clk is low.




One way to make a Flip-Flop: Two Latches

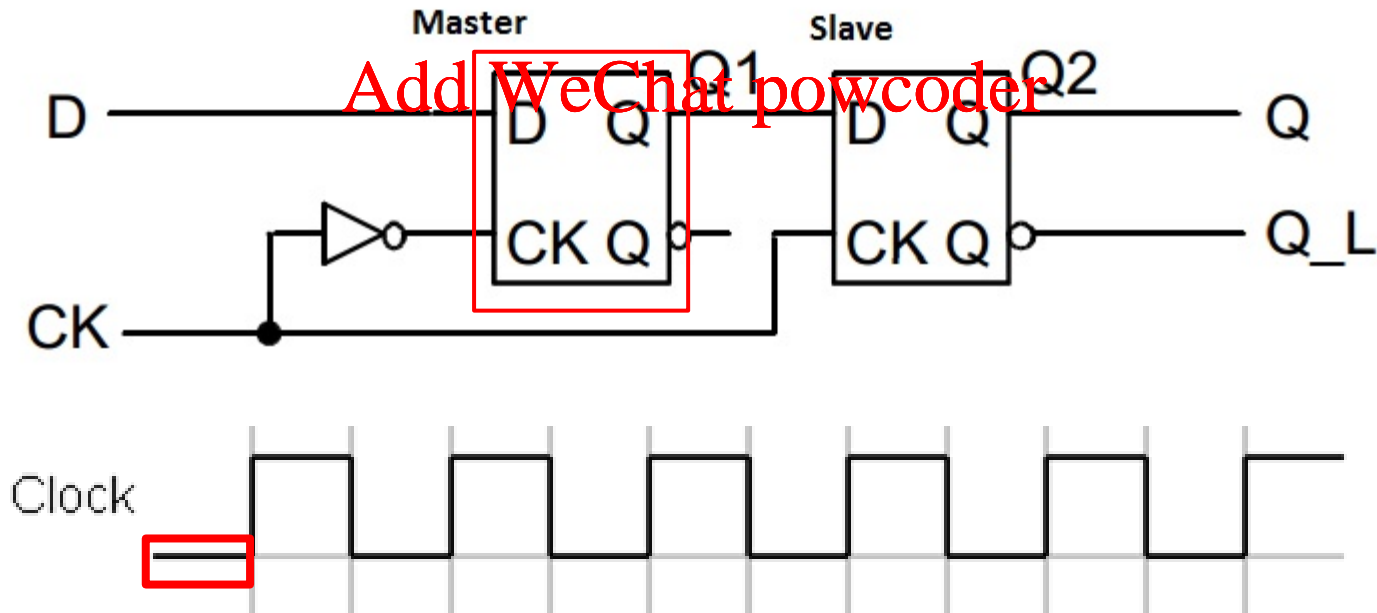- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since its clk is low.




One way to make a Flip-Flop: Two Latches

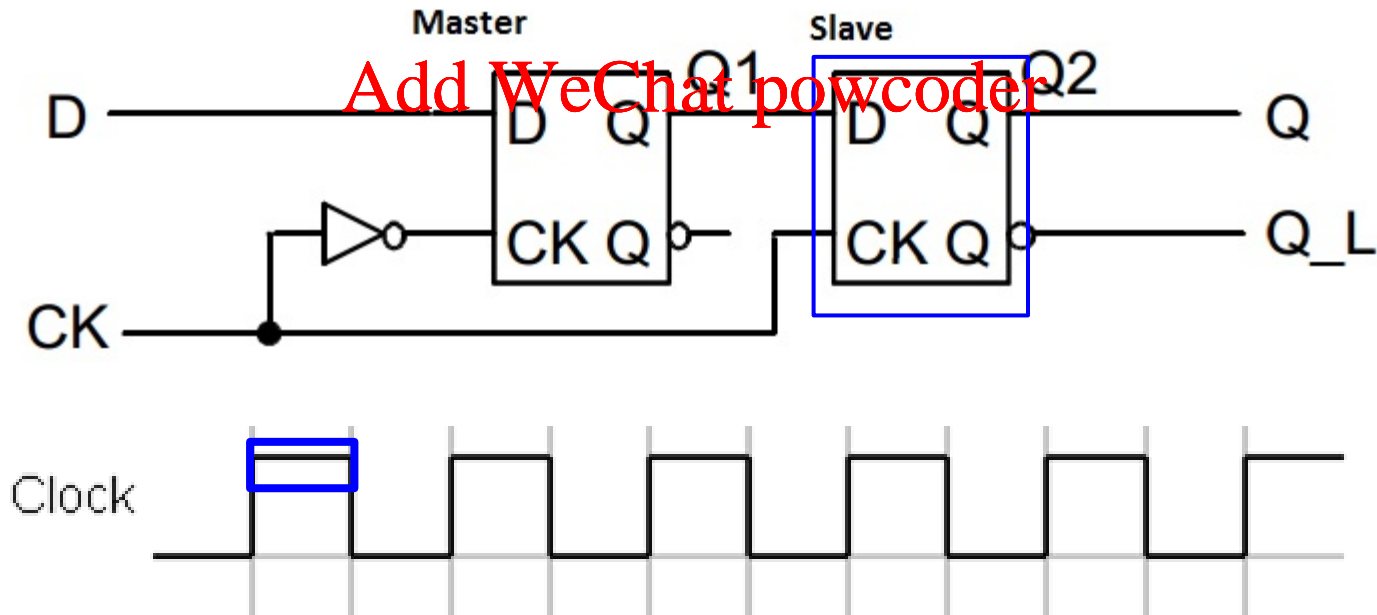- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since it's clk is low.




One way to make a Flip-Flop: Two Latches

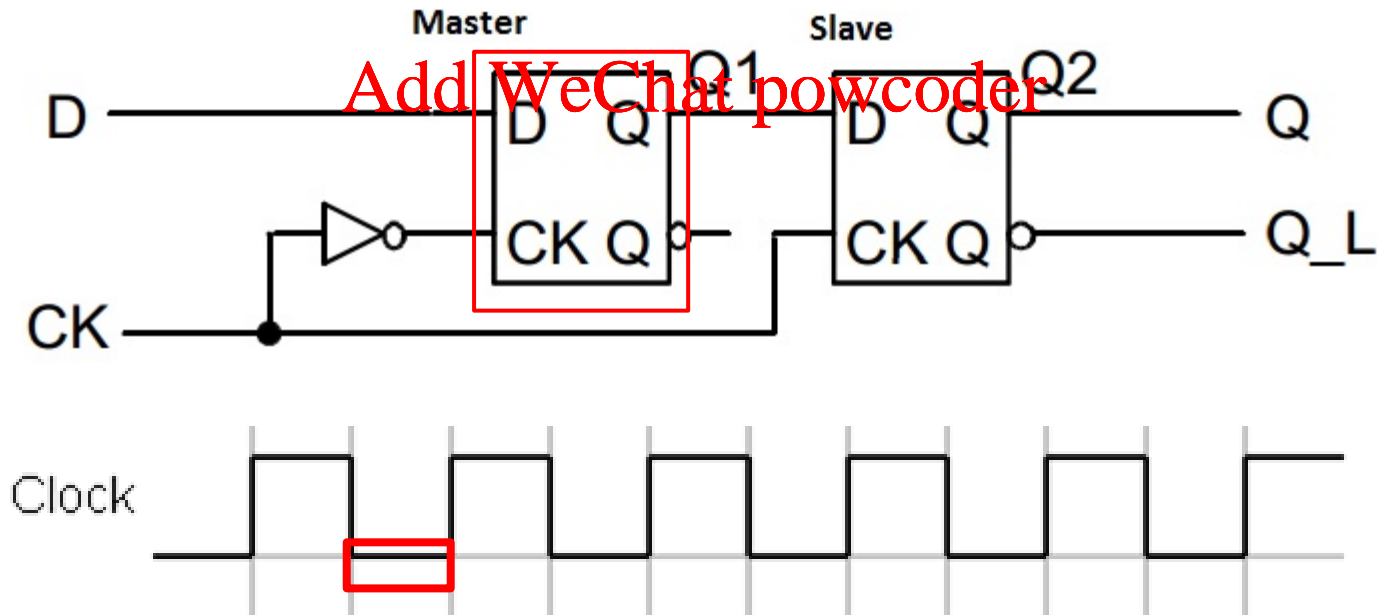- When clk transitions to high, slave captures last value of master which is now stored since its clk is low.
- When clk transitions to low, Master is open again but slave is closed, retaining value



One way to make a Flip-Flop: Two Latches

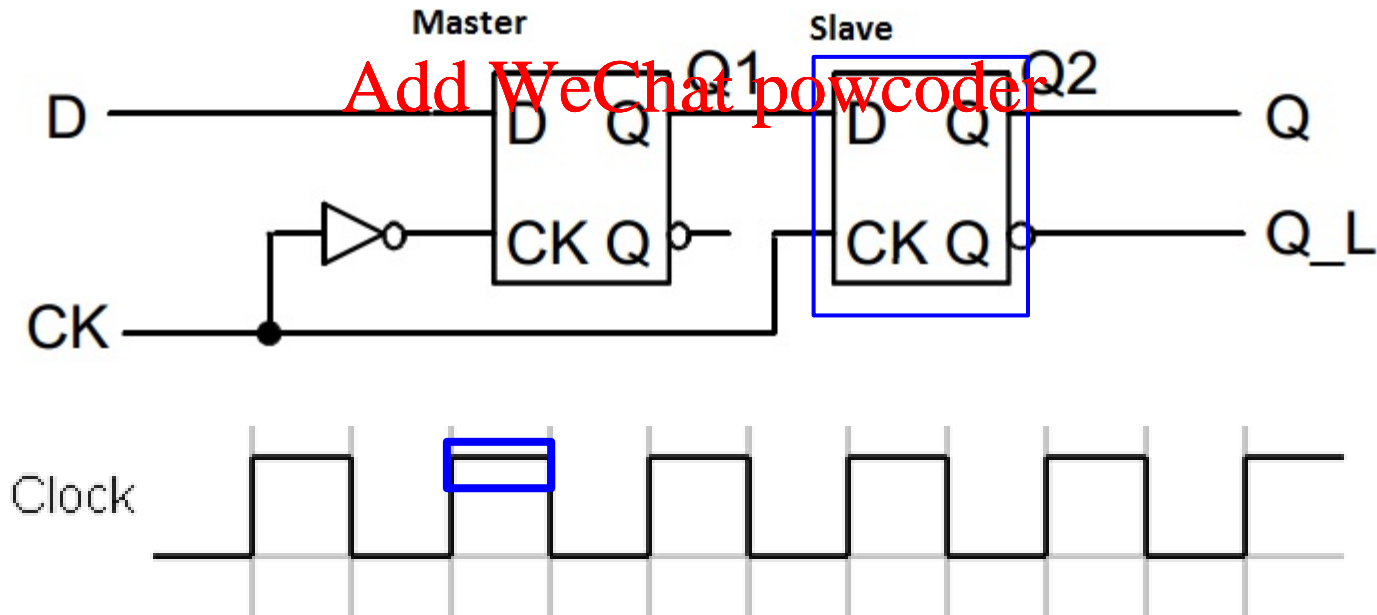- One latch(master) is connected to clk' and the other(slave) to clk (positive triggered).
- When clk transitions to high, slave captures last value of master which is now stored since it's clk is low.



Reset-Set (RS) Latch – or \overline{SR}

- Two inputs: Set and Reset
- Set to 0 one of the two inputs at a time to store a value, S sets, R clears
- The transition to 00 generates an undefined output


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

R-S Latch

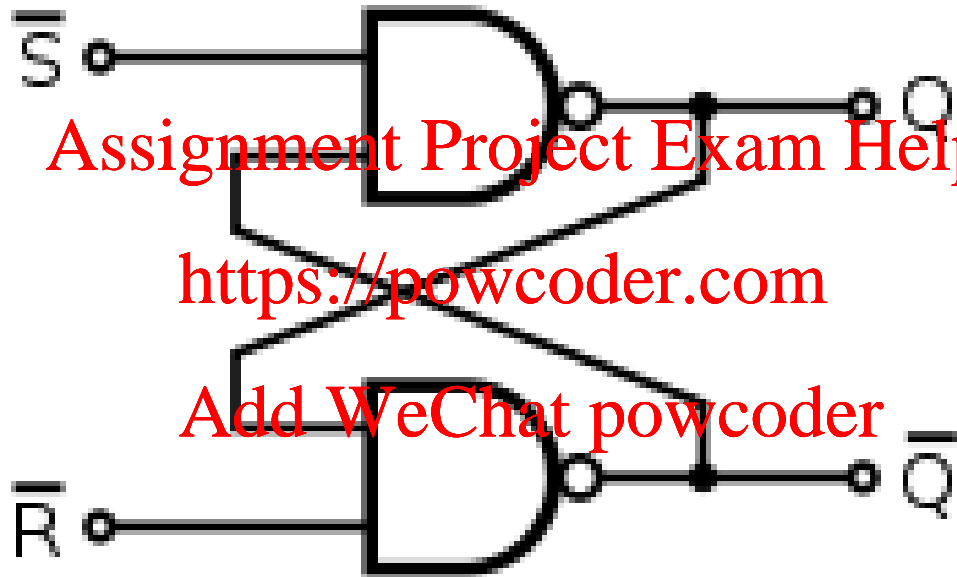


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

R-S Latch Nor Gates

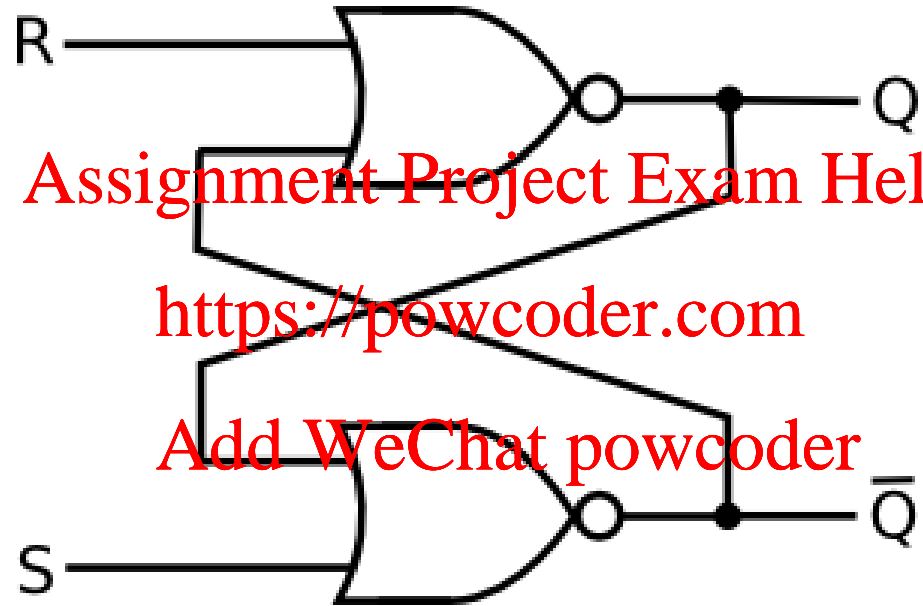


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Four SR Latch States: $S' 0, R' 0$

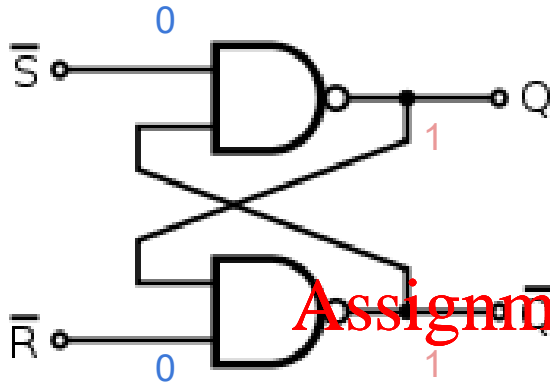


SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Four SR Latch States: $S' 0, R' 1$

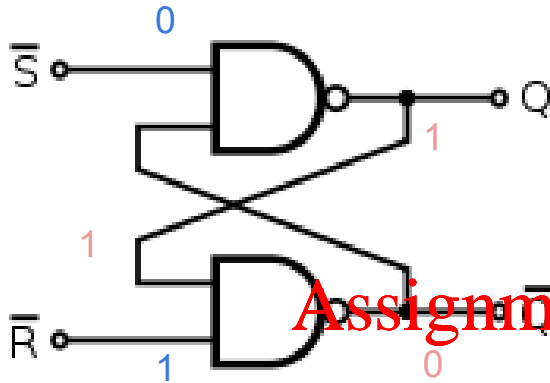


SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Four SR Latch States: $S' 1, R' 0$

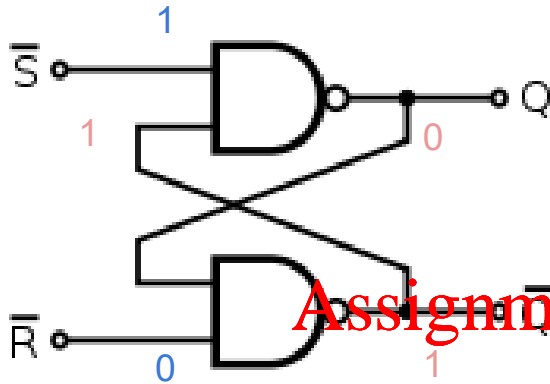


SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

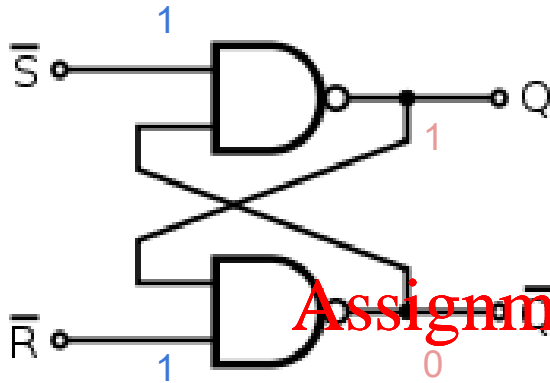Four SR Latch States: $S' = 1, R' = 1$ Memory




SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

$Q = 1, Q' = 0$ Add WeChat powcoder

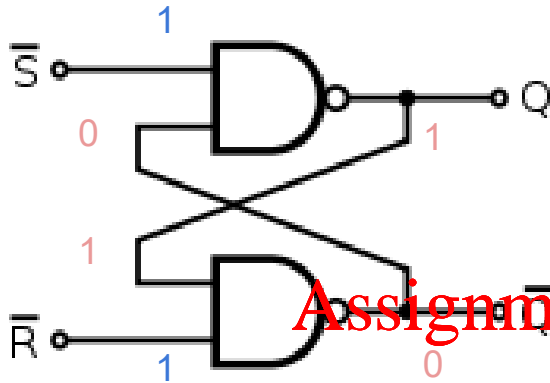Four SR Latch States: $S' = 1, R' = 1$ Memory




SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

$Q = 1, Q' = 0$ Add WeChat powcoder

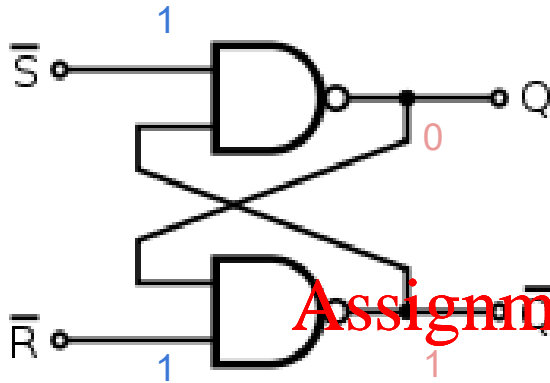Four SR Latch States: $S' = 1, R' = 1$ Memory




SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

$Q = 0, Q' = 1$ Add WeChat powcoder

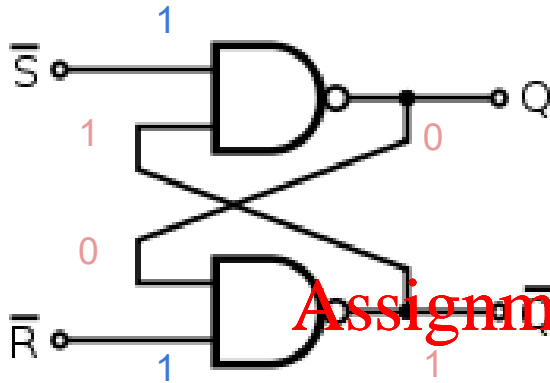Four SR Latch States: $S' = 1, R' = 1$ Memory




SR latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help

<https://powcoder.com>

$Q = 0, Q' = 1$ Add WeChat powcoder

D Latch

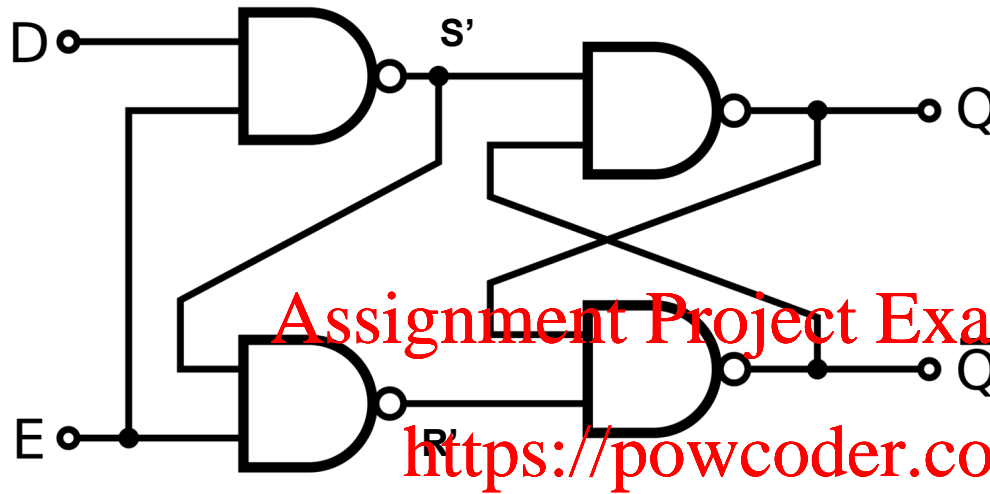

$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

E/clock	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state

D Latch

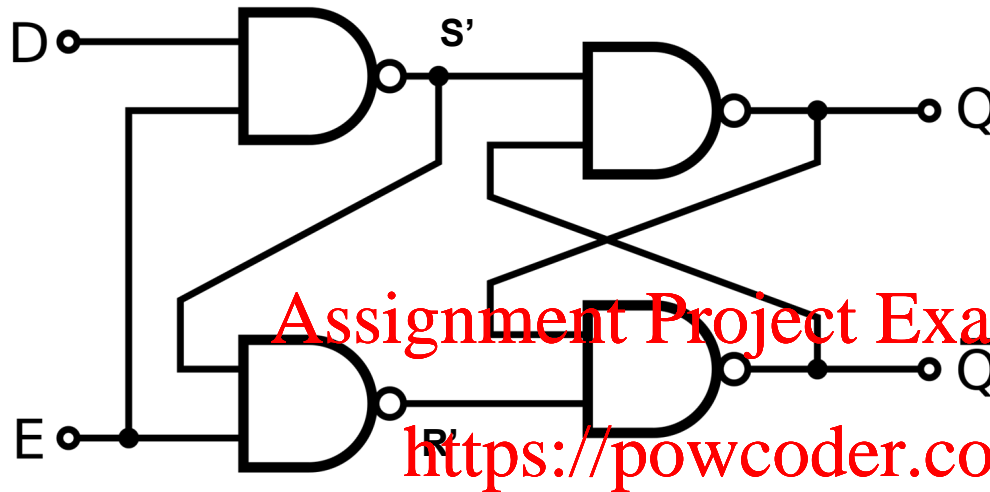


$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Add WeChat powcoder

E/clock	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state
0	1	1	1	Q	Q'	Keep state

D Latch

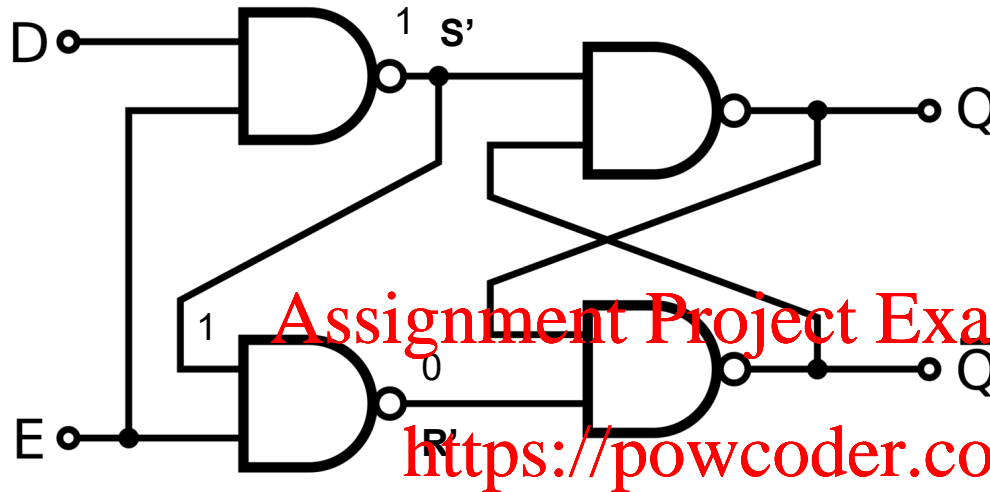

$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

E/clock	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state
0	1	1	1	Q	Q'	Keep state
1	0	0	1	0	1	D = Q

D Latch

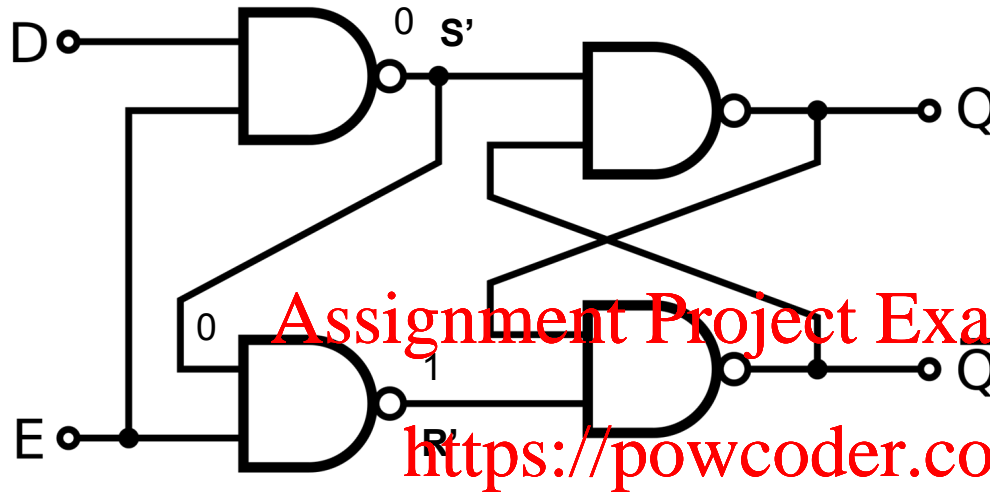

$\overline{S}\overline{R}$ latch operation		
\overline{S}	\overline{R}	Action
0	0	Restricted combination
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep state

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder



E/clock	D	R'	S'	Q	Q'	Comment
0	0	1	1	Q	Q'	Keep state
0	1	1	1	Q	Q'	Keep state
1	0	0	1	0	1	$D = Q$
1	1	1	0	1	0	$D = Q$

Register

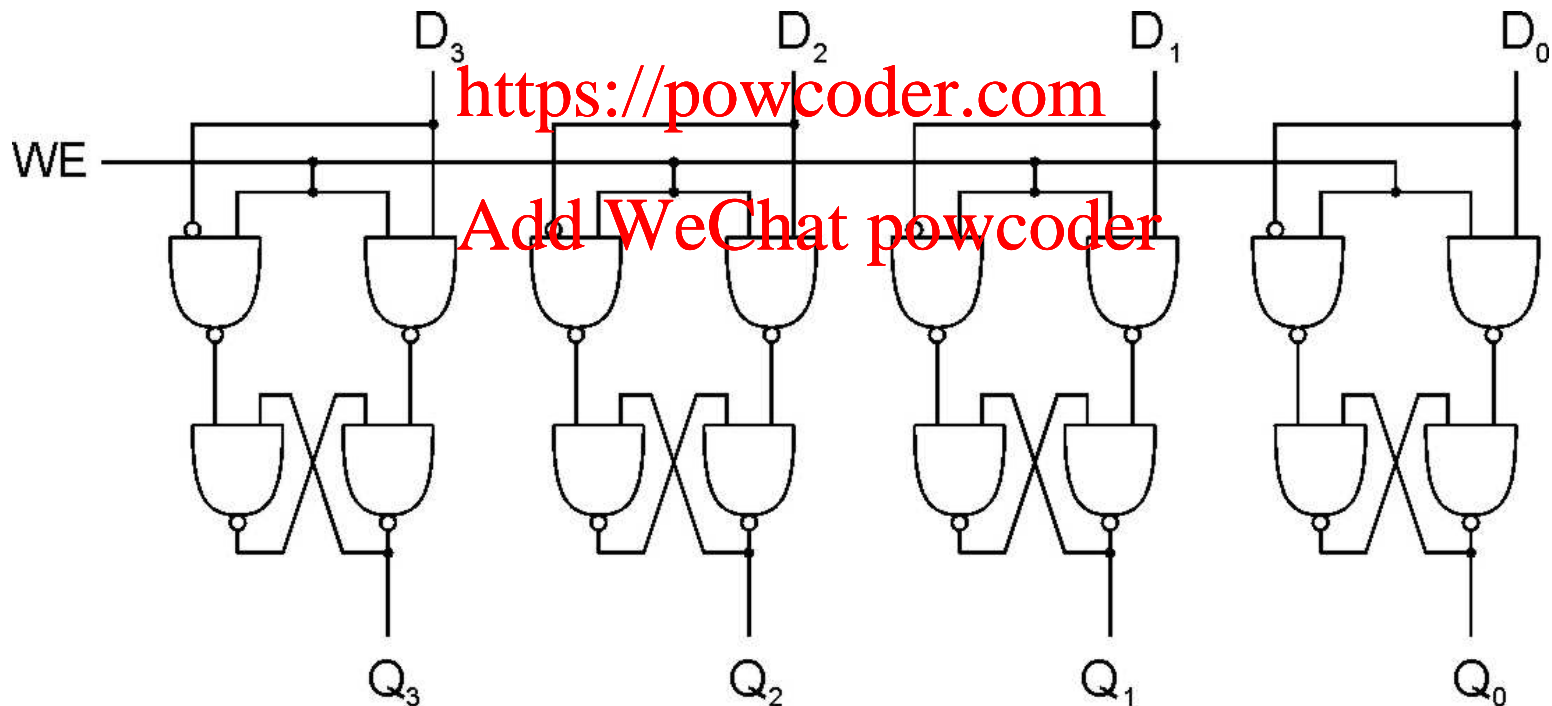- A register stores a multi-bit value
- Common WE which latches the n-bit value



Other types of memory...

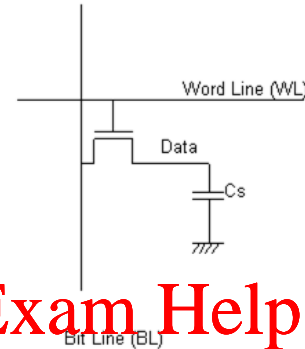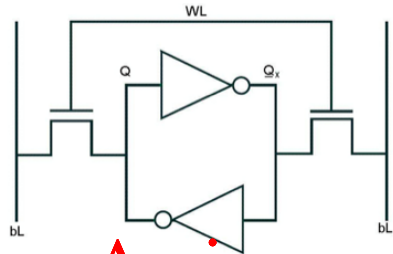

Assignment Project Exam Help


SRAM

(on-chip usually)

DRAM

(off-chip usually)

Add WeChat powcoder

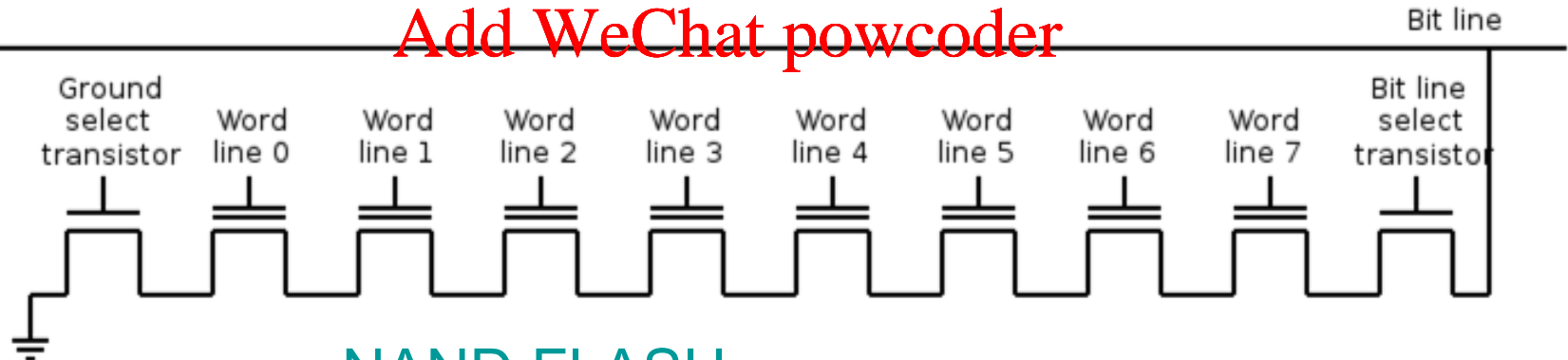

NAND FLASH

(on or off-chip, non-volatile)

Memory

Now that we know how to store bits,
we can build a memory – a logical $k \times m$ array of stored bits.

Assignment Project Exam Help

<https://powcoder.com>

Address Space:


number of locations
(usually a power of 2)

Add WeChat powcoder


$k = 2^n$
locations

Addressability:

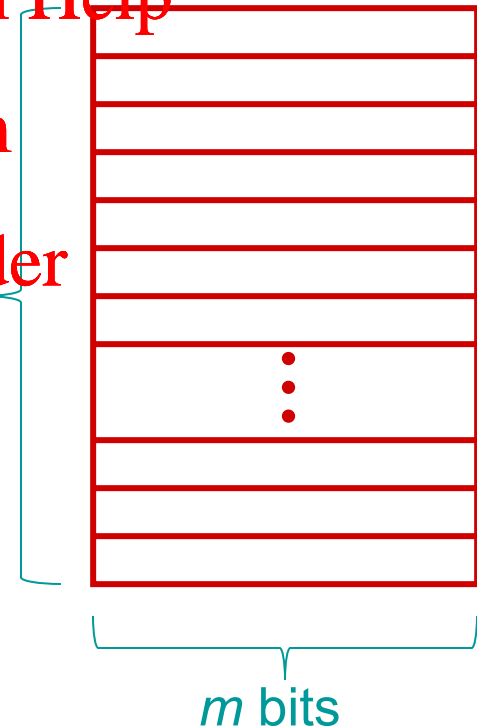
number of bits per location
(e.g., byte-addressable)



$2^2 \times 3$ Memory

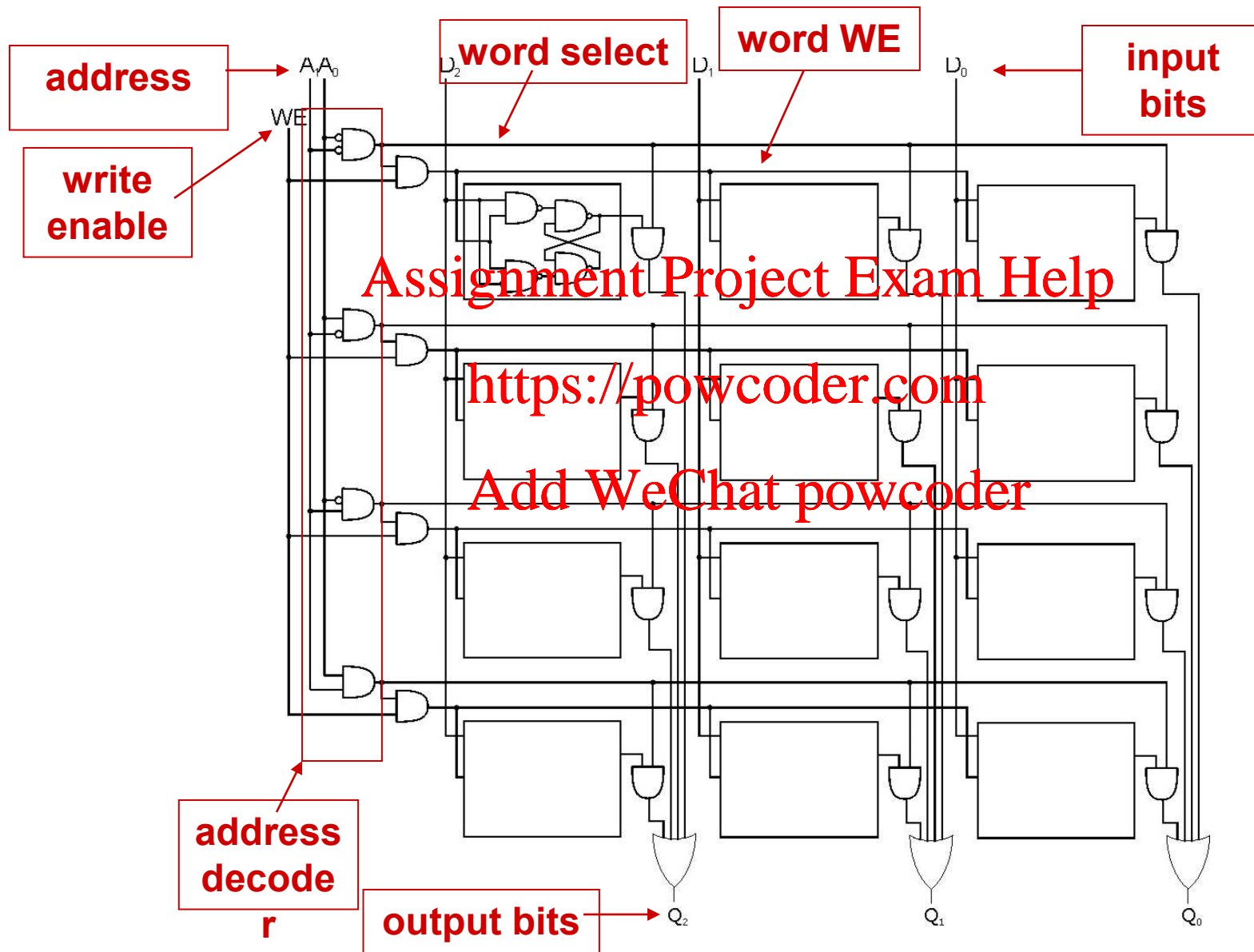

Let's Build a Computer

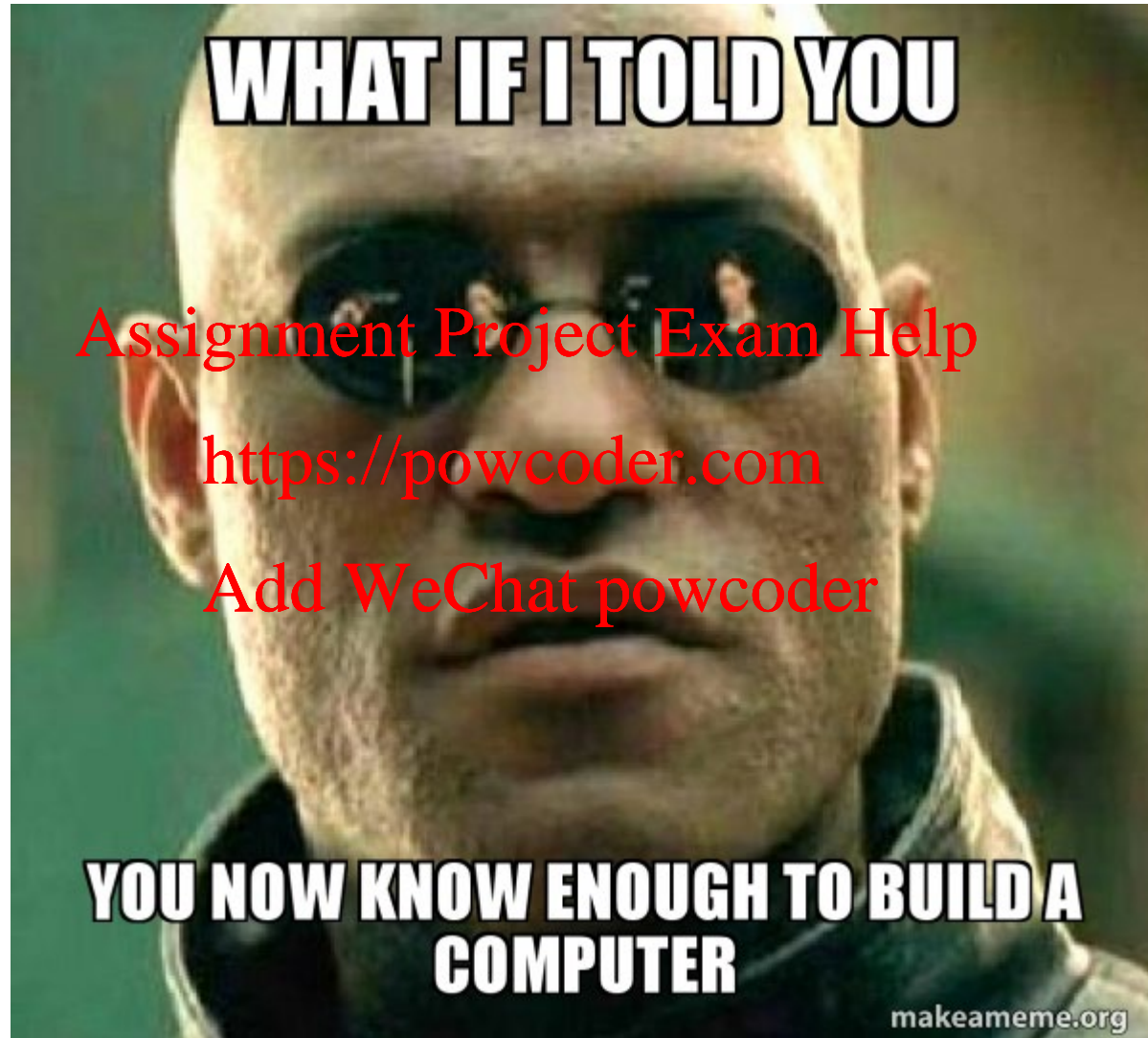

WHAT IF I TOLD YOU

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder

**YOU NOW KNOW ENOUGH TO BUILD A
COMPUTER**

makeameme.org

Basic Computer

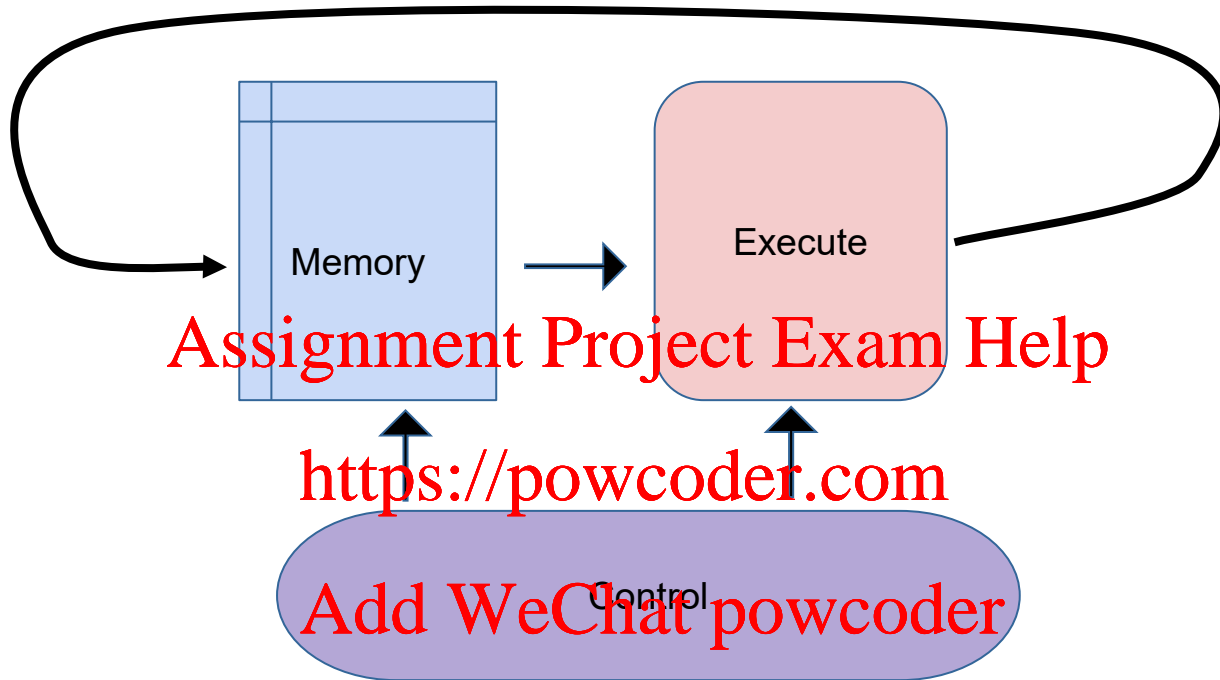

Memory: Could be Flip Flops, SRAM/DRAM, Flash etc

Execute: Combinational Logic (Adder, Shifter, Rotation etc)

Control: Finite State Machine (combination of sequential and combinational logic circuits)

Combinational Logic

<https://powcoder.com>

~~Add WeChat powcoder~~

State Machine

