

Abstraction & Digital Logic: From Transistors to Gates

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Lab 1 – DUE TUESDAY 1/19 11:59pm

- Lab 1 due in 1.5 weeks, released tomorrow
 1. Must commit/push to git server
 2. **Submit Commit ID in Google form**
- Uses MIML (MultiMedia Logic)
 - We will talk about transistors to build gates today
 - Lab will use gates to build logic functions
 - You should be reading Section 3 of the ZyBook (or equivalent of other books) as on schedule

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



Start going through Zybooks textbook

- We will first cover a little bit of Chapter 3
- Today's lecture will mirror 3.1,3.2
- Start doing the participation activities!

Assignment Project Exam Help

PARTICIPATION ACTIVITY 3.1.3: Voltage, current, and resistance.

1) Increasing voltage does what to current?

☒ Increases
☐ Decreases
☐ Doesn't change

Correct
Greater potential means more flow.

<https://powcoder.com>

Add WeChat powcoder



Problem Transformation - levels of abstraction


The desired behavior:
the application

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

The building blocks:
electronic devices

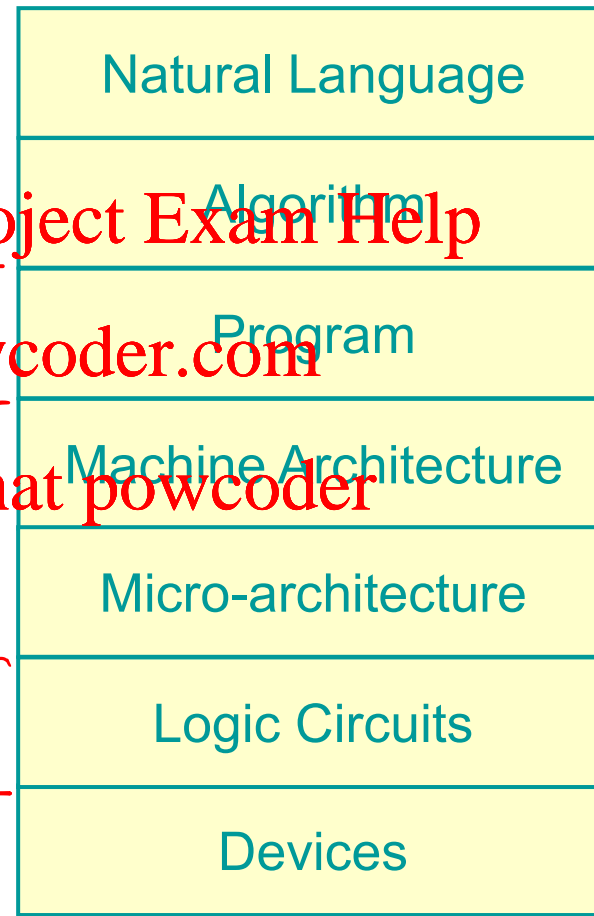


Physics
Materials



Levels of Abstraction

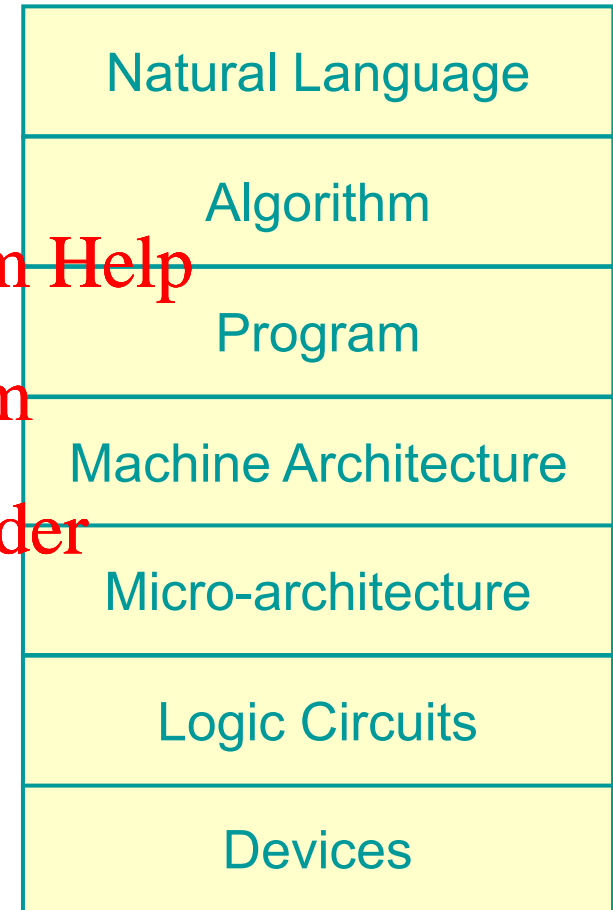- ◆ These levels do not necessarily correspond to discrete components, but to well defined standard interfaces.
- ◆ Standard interfaces provide
 - ★ portability
 - ★ third party software/hardware
 - ★ wider usage
- ◆ These levels are to some extent arbitrary - there are other ways to draw the lines.



Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder



The Program Level

- ◆ Most computers run a management program called the *operating system* (OS).

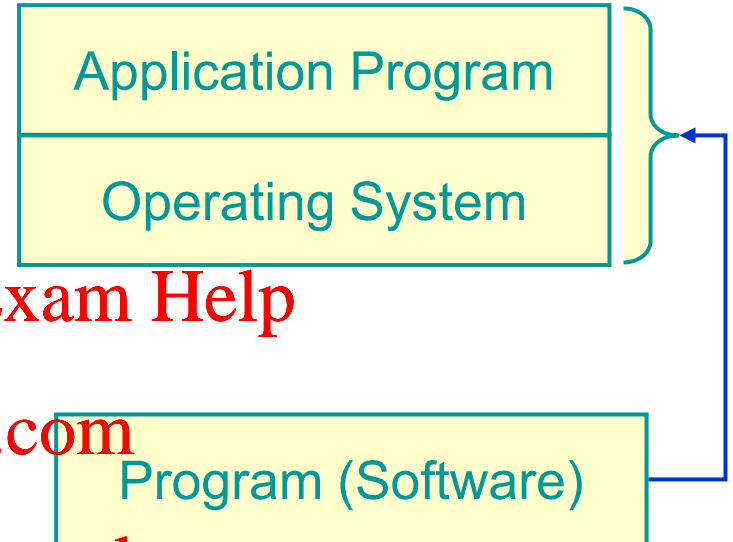- ◆ Application programs interface to the machine architecture via the OS.



<https://powcoder.com>

Add WeChat powcoder

| | |
|--------------|--------------|
| <u>git</u> | This lecture |
| <u>shell</u> | PowerPoint |
| <u>Linux</u> | Windows 10 |

Data

Application Program

Operating System



Course Outline - What is Next?

- The building blocks of computers: logic gates
- How to represent information
- The basic algorithm: the von Neumann model
- MIPS structure
- Programming the machine: assembly language
- A higher-level language: (Some) C

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



The Transistor: building block of computers

- Microprocessors contain many transistors
 - ◆ 15-Core Xeon Ivy Bridge-EX (2014): 4310 million
 - ◆ 10-Core Xeon Westmere-EX (2011): 2600 million
 - ◆ Six-Core Core i7 (2010): 1170 million
 - ◆ AMD 6-core Opteron (2009): 904 million
 - ◆ Intel Core i7 Quad (2008): 731 million
 - ◆ Intel Core 2 Duo (2006): 291 million
 - ◆ IBM/Apple PowerPC G5 (2003): 58 million
 - ◆ Intel Pentium 4 (2000): 42 million
 - ◆ IBM PowerPC 750FX (2002): 38 million
 - ◆ Intel 4004 (1971): 2300

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



The Transistor: Past and Present




Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

Buy



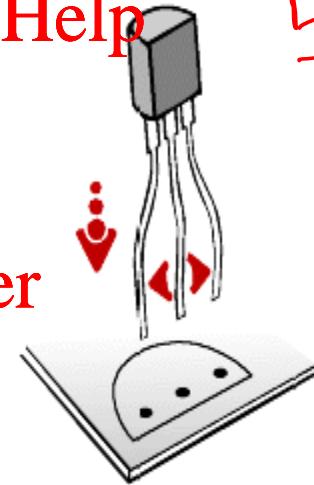


Integrated
Circuit



What Is a Transistor?

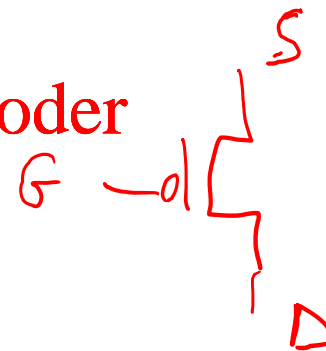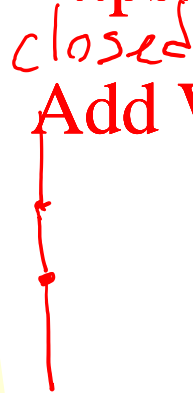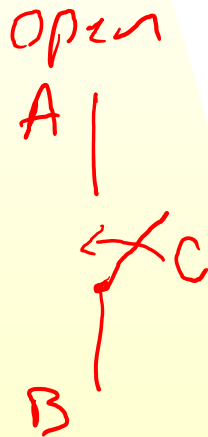- A switch, which can close between the source and the drain
- Changing the voltage of the gate lets you change the current flow between the source and drain (closing or opening the switch)



<https://powcoder.com>

Add WeChat powcoder




Neuron- Transistor analogy

100 billion neurons

Neuroscientists have become used to a number of “facts” about the human brain: It has **100 billion neurons** and 10- to 50-fold more glial cells; it is the largest-than-expected for its body among primates and mammals in general, and therefore the most cognitively able; it consumes an outstanding 20% of the total body ... Jun 26, 2012

www.pnas.org › content › Supplement_1

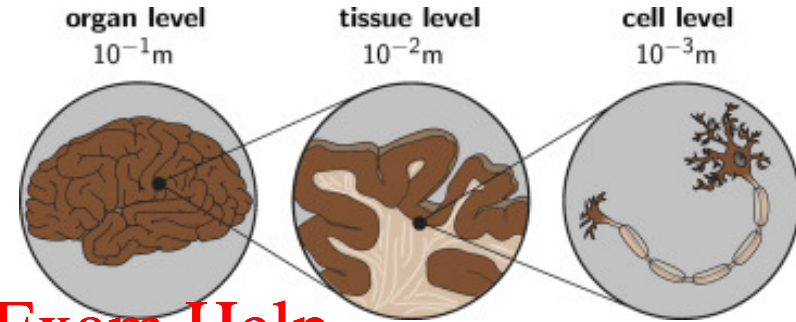The remarkable, yet not extraordinary, human brain as a ...




Assignment Project Exam Help

Register transfer level (RTL)




<https://powcoder.com>

Add WeChat powcoder

Transistor level

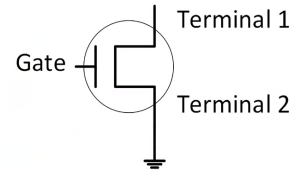

Gate level

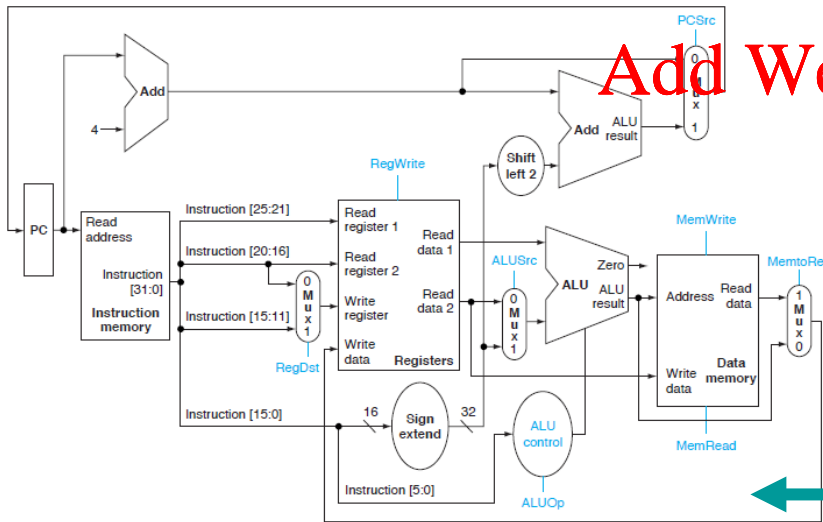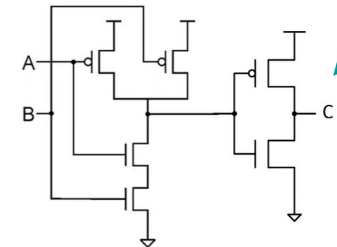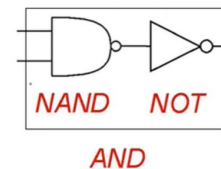

What is a transistor?

- Logically, each transistor is used as a switch
- Combined to implement logic functions
 - ◆ AND, OR, NOT
- Combined to build higher-level structures
 - ◆ Adder, multiplexer, decoder, register, ...
- Combined to build a processor
 - ◆ ARM, Core 2 Duo, i7 9700k, etc

Assignment Project Exam Help


<https://powcoder.com>

Add WeChat powcoder



Simple switch circuit

■ ECE 101

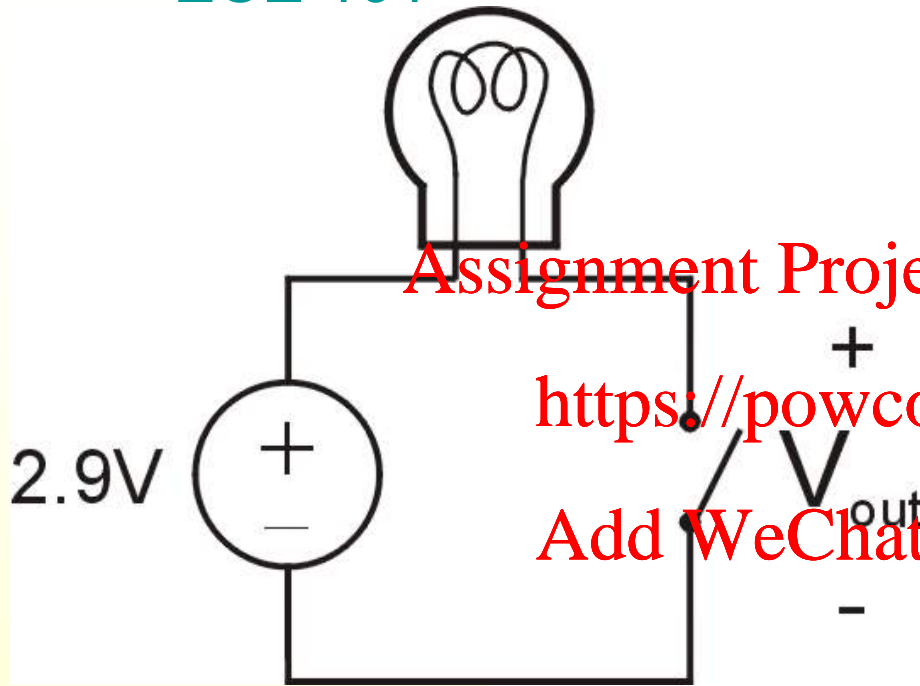

Switch open:

- ◆ No current through circuit
- ◆ Light is off
- ◆ V_{out} is +2.9V

Switch closed:

- ◆ Short circuit across switch
- ◆ Current flows
- ◆ Light is on
- ◆ V_{out} is 0V

Switch-based circuits can easily represent two states: on/off, open/closed, voltage/no voltage.



Assignment Project Exam Help

1. <https://powcoder.com> CMOS Logic Operation

Add WeChat powcoder



Assignment Project Exam Help

<https://powcoder.com>


Add WeChat powcoder




| |
|------------------------------|
| Task - Problem Statement |
| Algorithm |
| Program |
| Instruction Set Architecture |
| Microarchitecture |
| Logic Gates |
| Devices |

NMOS

PMOS



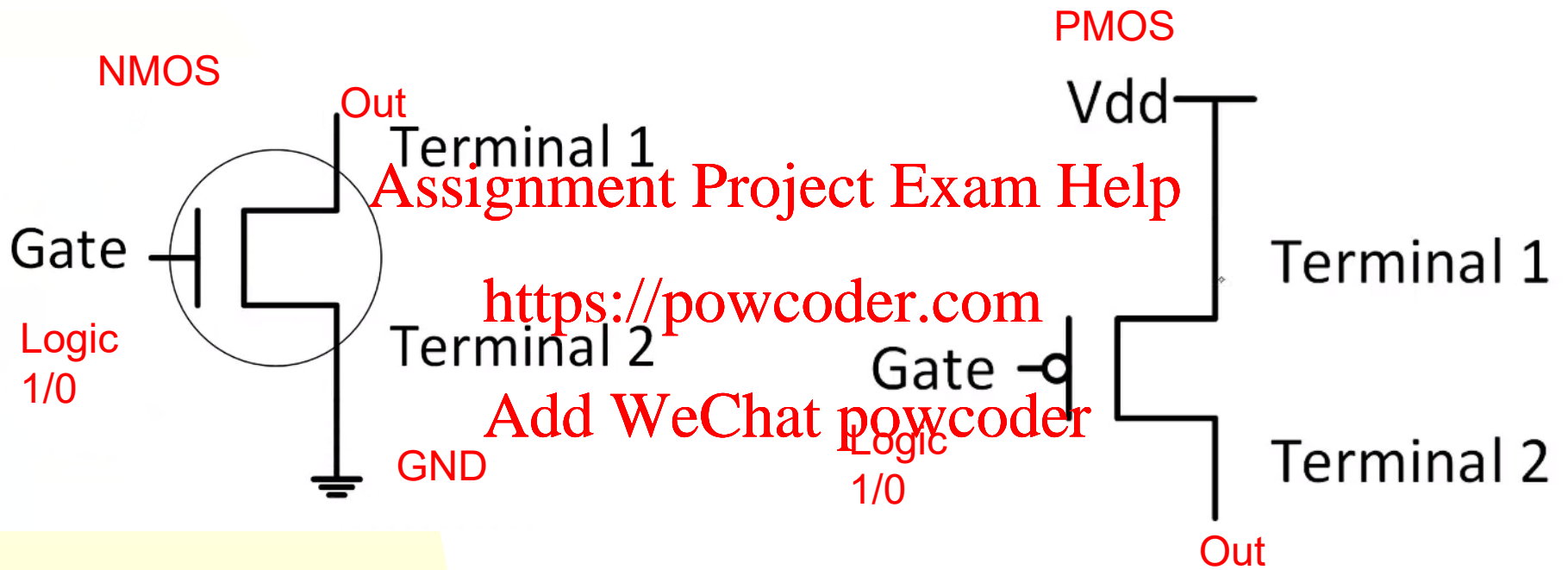

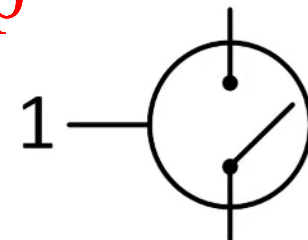
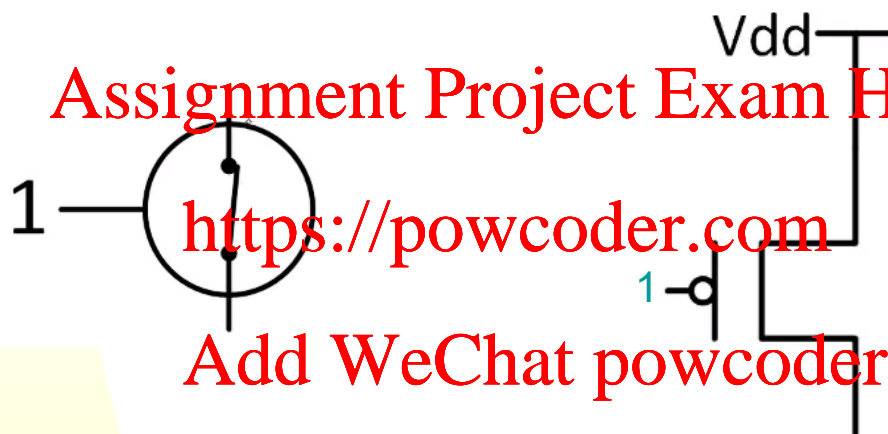
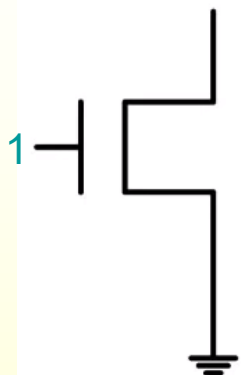


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder



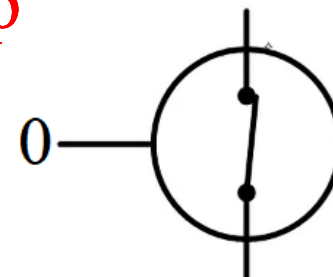
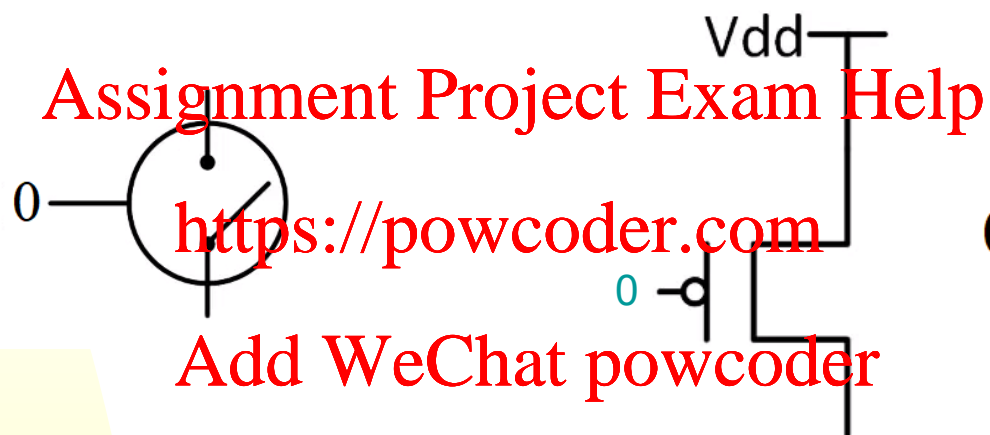
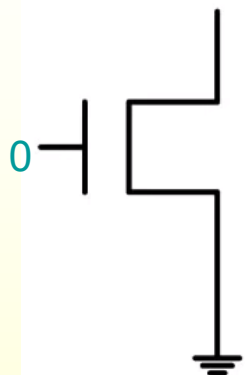


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder




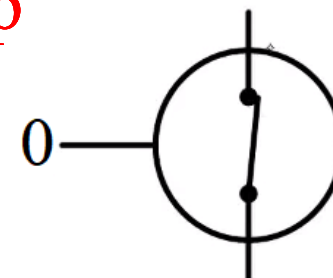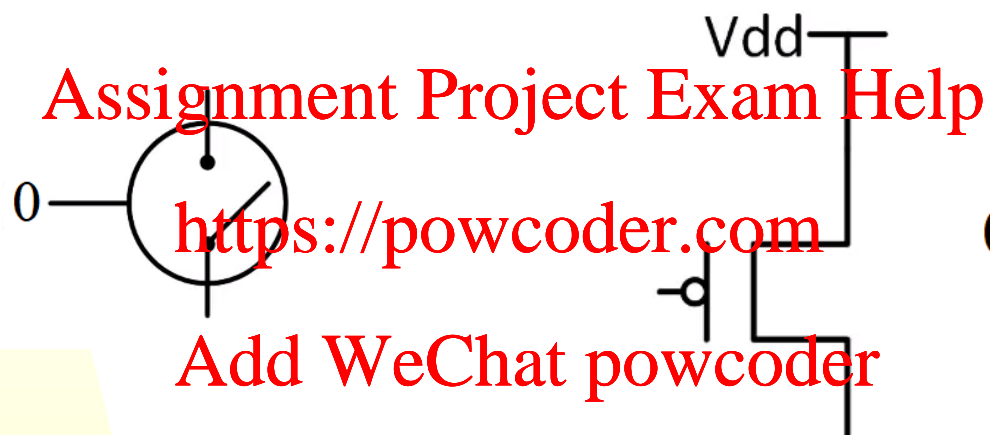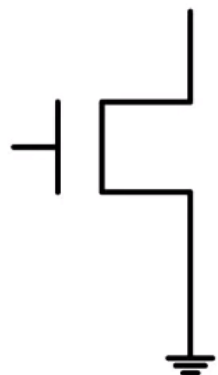



Out=
 V_{dd}

Complementary MOS (CMOS)



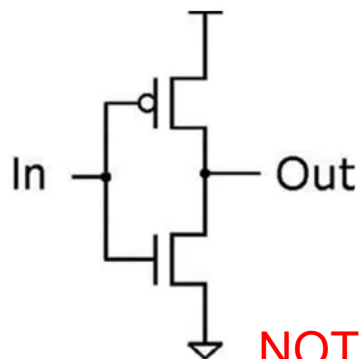

NOT
gate
(Inverter)

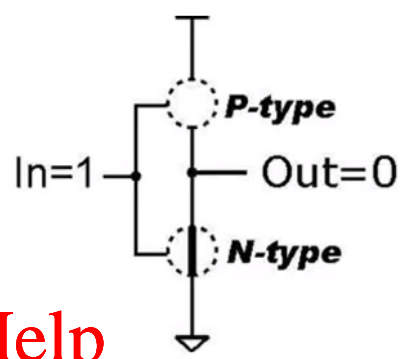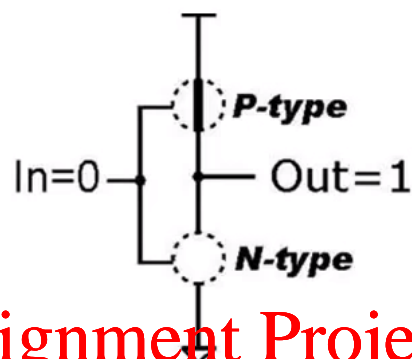

Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

| In | Out |
|-----------------|-----------------|
| 0 V (Logic 0) | Vdd V (Logic 1) |
| Vdd V (Logic 1) | 0 V (Logic 0) |





Assignment Project Exam Help


<https://powcoder.com>


Add WeChat powcoder

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

NAND gate

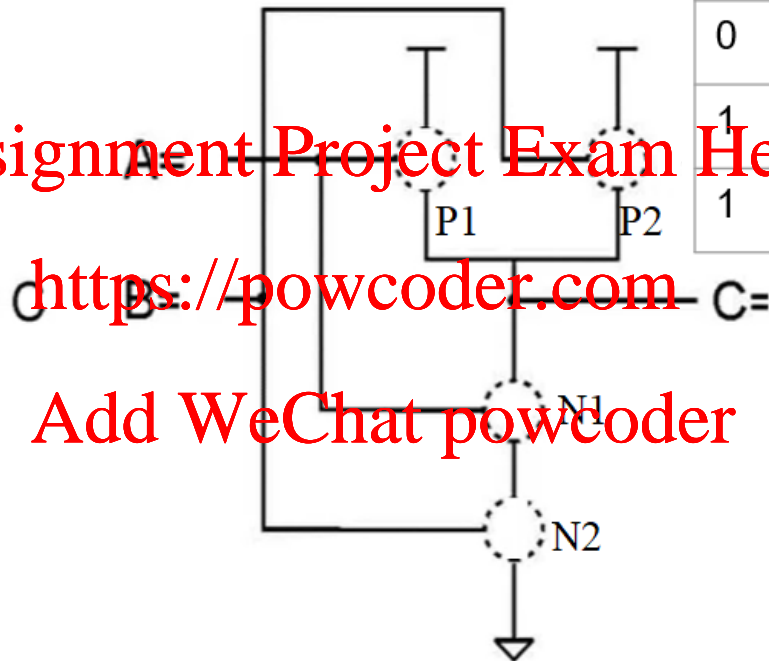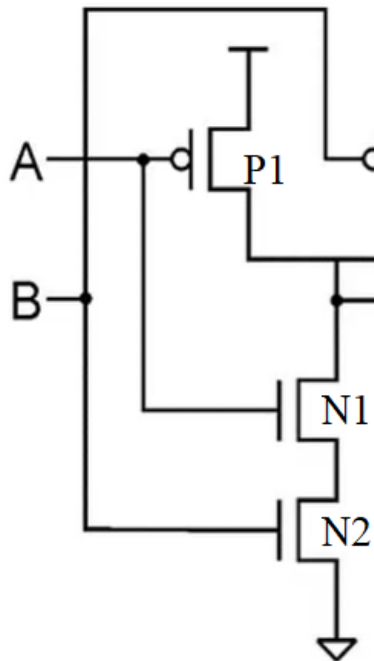

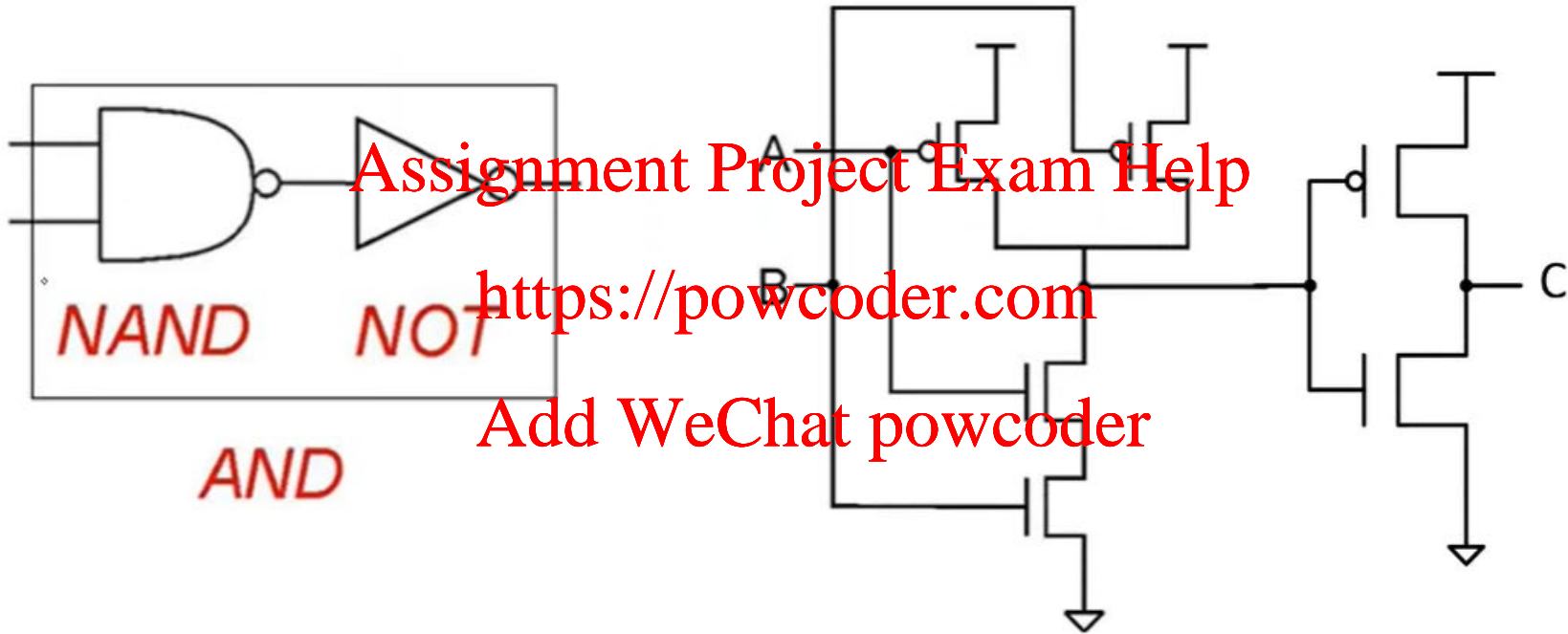

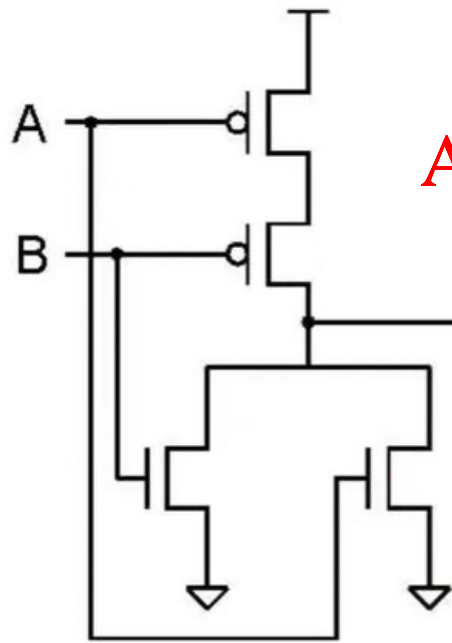



Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

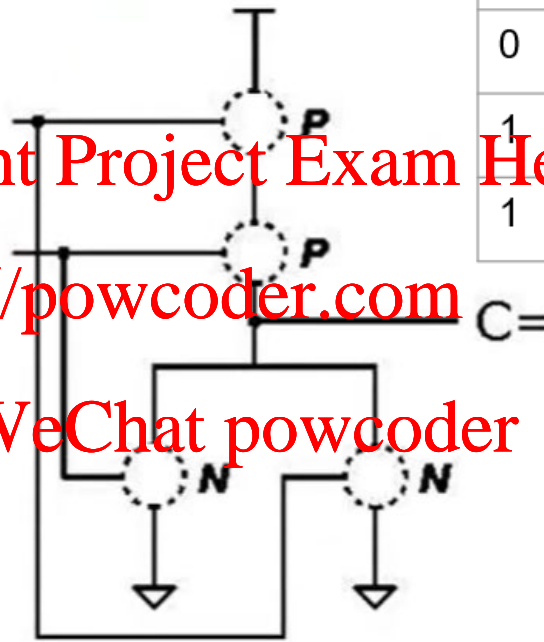


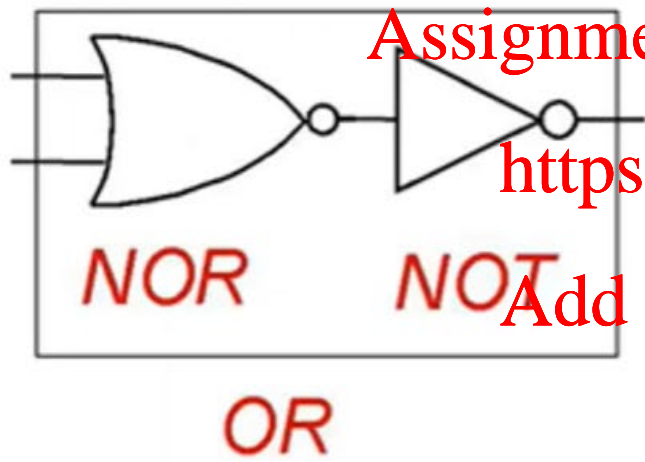


Assignment Project Exam Help

<https://powcoder.com>

Add WeChat powcoder

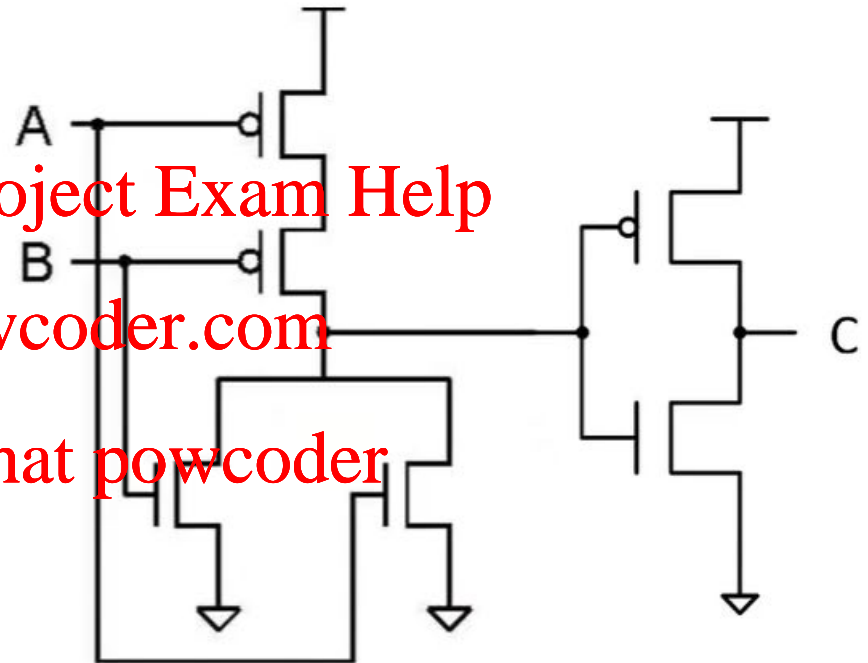

A general CMOS circuit

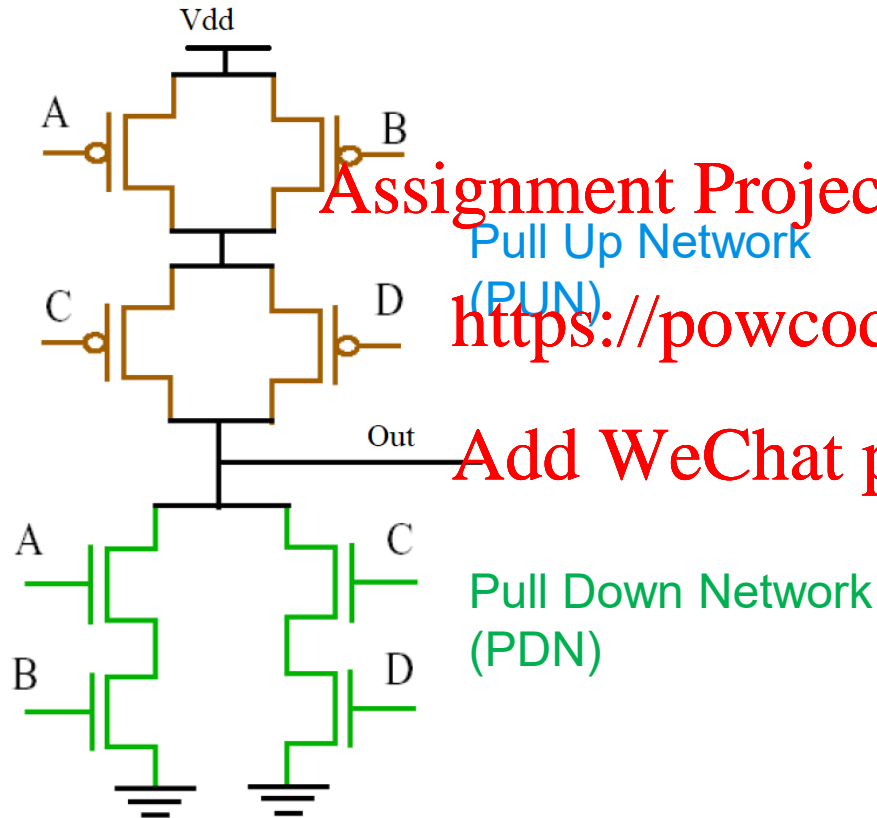

Q. How to determine Out without solving for entire truth table???

A. Follow Output path through either the PUN (towards Vdd) or the PDN (towards gnd)

PDN approach: Under what conditions does Out have a direct path to gnd??


Out = 0, (when A AND B ON)
OR (when C AND D ON)

$$\text{Out} = (AB + CD)'$$



Combinational Logic

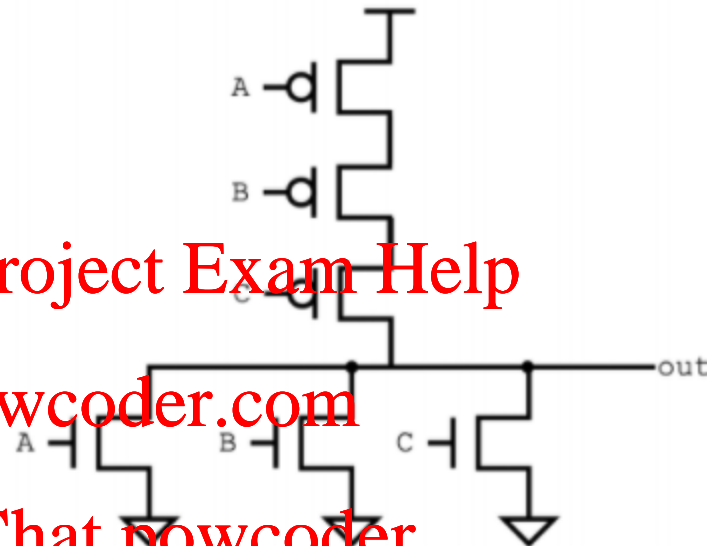7. The following CMOS diagram represents which logic gate?



- ☐ A. NAND
- ☐ B. NOR
- ☐ C. AND
- ☐ D. OR
- ☐ E. Answer not listed.

